

# QST

A MAGAZINE DEVOTED EXCLUSIVELY TO THE WIRELESS AMATEUR



JULY 1921

20 CENTS



OFFICIAL ORGAN OF THE AMERICAN RADIO RELAY LEAGUE, INC.

# For Your Information

We are pleased to reproduce the Radio Corporation's

CHARACTERISTICS OF RADIOTRONS (VACUUM TUBES) FOR  
DETECTION, AMPLIFICATION AND POWER WORK

|                            | Detector         | Amplifier   | Power Tube       | Power Tube      | Power Tube       |
|----------------------------|------------------|---|------------------|-----------------|------------------|
|                            | UV-200           | UV-201  | UV-202           | UV-203          | UV-204           |
| Price                      | \$5.00           | \$6.50  | \$8.00           | \$30.00         | \$110.00         |
| Dimensions (overall)       | 1 3/4" x 4 1/8"  | 1 3/4" x 4 1/8"                                     | 2 1/8" x 5"      | 2" x 7 1/2"     | 5" x 14 1/2"     |
| Base                       | 4 Prong Standard | 4 Prong Standard                                    | 4 Prong Standard | 4 Prong Special | Special Mounting |
| Voltage of Filament Source | 6V.              | 6V.   | 10V.             | 12V.            | 15V.             |
| Filament Terminal Voltage  | 5 to 5.4V.       | 5 to 5.4V.  | 7.5V.            | 10V.            | 12V.             |
| Filament Current           | 1.1 amp.         | 1. amp.   | 2.35 amp.        | 6.5 amp.        | 15 amp.          |
| Plate Voltage              | 15 to 22.5V.     | 40 to 100V.   | 350V. normal     | 1000V. normal   | 2000V. normal    |
| Plate Current              |                  |   | .045 amp.        | .15 amp         | .25 amp.         |
| Output Impedance           | 10,000 ohms      | 21,000 ohms at 40 Volts<br>14,000 ohms at 100 volts | 5000 ohms        |                 |                  |
| Amplification Constant     | 7                | 8   | 8                | 10              | 25               |
| Watts Output               |                  |   | 5 normal         | 50 normal       | 250 normal       |

Clip this page out and save it for future reference.

## THIS NEW APPARATUS WILL INTEREST YOU

As promised last month, we are the first to offer the Radio Corporation's new apparatus for experimental use. Place your order now, with Atlantic. Both our stores have a complete stock of this new equipment and will fill your orders promptly.

|  |        |
|--|--------|
| Radiotron U.V. 200, a gas-content detector, specially designed for amateur use ..... | \$5.00 |
| Radiotron U.V. 201, an exceptional "Pilotron" type amplifier .....                   | 6.50   |
| Radiotron U.V. 202, a 5 watt transmitter for C.W. work .....                         | 8.00   |
| Radiotron U.V. 203, a 50 watt transmitter for high powered C.W. work ..              | 30.00  |
| Radiotron U.V. 204, a 250 watt transmitter for experimental C.W. ....                | 110.00 |
| R. C. Standard Rheostat, Model P.R. 535, for Radiotron 201, 202, and 203 ..          | 3.00   |
| R. C. Standard "A" Battery Potentiometer, Model P.R. 536, for receiving ..           | 2.00   |
| R. C. Standard Rheostat, Model P.T. 537, for Radiotron 203 and 204 ....              | 10.00  |
| 20 Watt Kenetron Rectifier Valve, Model U.V. 216 .....                               | 7.50   |
| 150 Watt Kenetron Rectifier Valve, Model U.V. 217 .....                              | 26.50  |
| R. C. Standard porcelain socket Model U.R. 542, for Radiotron 200, 201 and 202 ..... | 1.00   |

|   |      |
|---|------|
| R. C. Standard Bakelite socket, for Radiotron 200, 201 and 202 .....                                      | 1.50 |
| R. C. Special Bakelite socket for Radiotron U.V. 203 .....  | 4.25 |
| R. C. Standard porcelain socket Model U.T. 541, for Radiotron U.V. 203 ....                               | 2.50 |
| R. C. Standard end mountings for Radiotron U.V. 204, per pair .....                                       | 2.00 |
| (Model U.T. 501 for filament end, Model U.T. 504 for plate end.)  |      |
| R. C. Inter-tube tone frequency amplifying transformer, Model U.V. 712, for Radiotrons 200 and 201 .....  | 7.00 |
| R. C. Standard grid leak, mounting and unit .....   | 1.25 |
| R. C. Standard grid leak, mounting .....  | .50  |
| R. C. Standard grid leak unit (24 values, 1/2 to 6 megohms) .....   | .75  |
| R. C. Special 5000 ohm, Size M grid leak, with midtap at 3500 ohms, for use with Radiotron U.V. 202 ..... | 1.10 |
| R. C. Special 5000 ohm, Size B grid leak, with midtap at 2500 ohms, for use with Radiotron U.V. 203 ..... | 1.65 |

Please include sufficient postage on all mail orders.  
Bulletin 14, gladly sent on request to any reader of QST.

# Atlantic Radio Company, Inc.

88 Broad Street  
Boston, 9 Mass.

Branch--15 Temple Street  
Portland, Maine





"This mark  
your guarantee"

ALBANY, N. Y.  
Shotton Radio Mfg. Co.  
8 Market St.

ASHEVILLE, N. C.  
Hi-Grade Wireless Instru-  
ment Co.

ATLANTIC CITY, N. J.  
Paramount Radio Supply  
Arkansas & Pacific Sts.

BOSTON, MASS.  
Atlantic Radio Co.  
88 Broad St.

BROOKLYN, N. Y.  
Kelly & Phillips,  
312 Flatbush Ave.

CHICAGO, ILL.  
Chicago Radio Lab.  
1316 Carmen Ave.

EUREKA, ILL.  
Klaus Radio Co.  
Branch, Peoria, Ill.

KANSAS CITY, MO.  
McCreary Radio Supply  
4th and Delaware Sts.

McKEESPORT, PA.  
K. & L. Electric Co.  
427 Olive Street

NEW BRUNSWICK  
NEW JERSEY  
Geo. N. DeLaplaine  
306 George St. and  
8th & Magnolia Sts.

NEW ORLEANS, LA.  
Rose Radio Supply,  
604 Gravier St.

NEWARK, N. J.  
A. H. Corwin & Co.  
4 West Park St.

OMAHA, NEBRASKA  
O-B Radio Supply Co.  
406 Brown Building.

PHILADELPHIA, PENN.  
Philadelphia School of  
Wireless Telegraphy  
Broad and Cherry Sts.

PITTSBURGH, PENN.  
Radio Electric Co.,  
3807 Fifth Ave.

PLAINFIELD, N. J.  
Paul R. Collier,  
154 E. Front St.

PORTLAND, ME.  
Atlantic Radio Co.,  
15 Temple St.

PROVIDENCE, R. I.  
Rhode Island Elec. Equip.  
Co.  
45 Washington St.

SCRANTON, PENN.  
Shotton Radio Mfg. Co.  
P. O. Box 3  
Branch, 8 Kingsbury St.  
Jamestown, N. Y.

SEATTLE, WASH.  
Northwest Radio Service  
609 Fourth Ave.

WASHINGTON, D. C.  
Eastern Radio & Elec-  
tric Company,  
1405 Florida Avenue.

WICHITA, KAN.  
The Coaradio Co.  
1725 Fairmount Ave.

Canadian  
BIENVILLE, QUEBEC.  
Canadian Radio Mfg. Co.  
MONTREAL, QUEBEC.  
J. B. Miller  
136 Vendome Ave. N.D.G.

TORONTO, ONTARIO.  
The Vimy Supply Co.  
667 College St.

# RADISCO

"Your Assurance of Satisfactory Performance"



## RADISCO COILS

To buy Radisco Coils is to invest in permanent sat-  
isfaction at the lowest prices consistent with an  
unvarying standard of quality.

Radisco Coils, mounted and unmounted, in ranges  
to meet every known wave length, are available at  
the nearest Radisco agency listed below. They  
range in price from 70 cents to \$2.65. Larger  
sizes wound with 20/38 Litz at a moderate increase.  
Three of the larger sizes are also furnished with  
three taps, to give a wider wave length range.  
There is surely some Radisco Coil that will exactly  
fill your need. And remember, the universal wind-  
ing that has stood the test of time will make good  
for you, also.

*Note: If you mount your own coils, Radisco coil  
mountings are made to fit without bending or filing.*

*Price 80 cents each, by mail or at all  
Radisco Agencies.*

**RADIO DISTRIBUTING COMPANY  
NEWARK, NEW JERSEY**

# RADISCO

"Your Assurance of Satisfactory Performance"

# Increase the receiving range of your station *gradually*-- with ABC sectional UNITS!

You can start with the *ABC* receiving cabinet, add on a VT detector and as many stages of amplification as you want, *at any time*, yet never discard a nickel's worth of apparatus as you go along!



WHEN YOU start to build your receiving station, keep in mind the gradual development of your range. Avoid buying a lot of miscellaneous apparatus, much of which may be useless when you want to improve your set. Buy equipment that will be just as efficient a year from now, when you want to add to it, as it is today! You can do this by concentrating on *ABC* sectional receiving UNITS.



## *The Sectional Principle*

*ABC* sectional UNITS were purposely designed to work together and to save you money when you want to add to your set. The first cabinet is the Radio Receiver, a completely equipped crystal detector station. And altho this Unit is highly efficient and complete in itself, here is the important part of the *ABC* system: Whenever you want to increase your range, you simply

hook the next cabinet (the *ABC* Combined VT Detector and One-Step Amplifier), directly onto the receiver and proceed. It takes about as long to do it as to say it, and you haven't discarded a nickel's worth of equipment. There's no tinkering, no adjusting to be done. Your new set works perfectly from the start. The Units are designed for each other, and the standardized methods of production makes it certain that every new combination of Units, as you go along, *will* make a smooth-working efficient outfit.

IN PLACE of the *ABC* Combined VT Detector and One-Step Amplifier UNIT, you may add on these Units separately. But we strongly recommend the Combination Unit because it gives you (with the proper coils) sufficient range and sensitivity to pick up any known type of sending station, code or phone, on any known wave length.


OTHER CABINETS of the series are the *ABC* Two-Step Amplifier UNIT and the *ABC* "CEARION", a loud speaker that hooks right on to any previous combination of Units without any additional batteries or extra equipment.


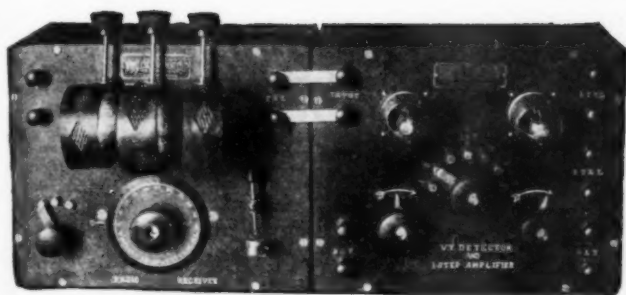
## *The ABC Receiving UNIT*

THE FIRST cabinet, the receiver itself, comes to you equipped with three *ABC* coils, an *ABC* 41 plate variable condenser, a tested

**ABC UNITS**  
*Standardized Radio*  
*Sectional Receiving*



THE FIRST TWO UNITS OF THE ABC SERIES.

The combination shown here is the ABC Receiving UNIT and the ABC Combined VT Detector and One-Step Amplifier UNIT. This set is highly recommended for receiving all classes of signals on all known wave lengths. A One or Two-Step Amplifier or the ABC Clarion may be added at any time. Price of the Receiving Cabinet complete, \$24.50. Price of the Combined VT Detector and One-Step, \$37.50 (without tubes and batteries). This entire outfit, including aerial, phones, tubes and batteries may be secured for about \$84.00, a price never previously approached for guaranteed, high quality radio apparatus.

crystal detector, a switch for varying the wave length range, etc. The panel is a special impregnated fibre, highly polished, and carefully fitted to the handsome Kodak-finish cabinet. The price is \$24.50.

FOR THOSE who want it, there is also provided the ABC Completion Package to go with this Unit. The Completion Package contains phones, aerial, insulators, ground clamp; in fact all the equipment needed to set a complete working station in two hours. This package is an unusually good buy at \$7.50.



### "Professional Radio Equipment at Amateur Prices"

ABC apparatus is highly standardized and produced by automatic, machine methods, down to the smallest switch point. We took three years to make the design right. Other Units in the same standard design will be ready for you, whenever you want them. And the economies of quantity production in the best equipped radio factory in the world make it possible for us to offer "Professional Radio Equipment at Amateur Prices," and back up every ABC instrument with our unequalled guarantee, "Your money's worth or your money back!"



### Booklets

IN ORDER to explain the ABC sectional UNIT system thoroly, we have prepared a 16-page booklet in two colors, profusely illustrated. It is entitled, "How I Put Up

ALWAYS MENTION Q S T WHEN WRITING TO ADVERTISERS

a Complete Radio Station in Two Hours," a true story written by a young man with no previous radio experience whatever. You will be interested to learn how amazingly simple it is to get results with ABC UNITS. Send 10 cents for Booklet Q7.

FOR AMATEURS who prefer to build their own sets, we offer ABC Standardized Un-assembled Parts, identical with parts used in the UNIT system. The complete ABC line including the UNITS is described and illustrated in our new 2 color catalogue. Gladly mailed for 10 cents in stamps or coin. Request Catalogue CQ7.

The coupon below is for your convenience. Mail it today or write us a letter for the booklet or catalogue, or both.

DEALERS: If you are not now stocking the ABC Line, it will pay you to write for our portfolio, "The ABC Sales Plan in a Nutshell."

WIRELESS EQUIPMENT CO., Inc.  
Newark, New Jersey

WIRELESS EQUIPMENT CO., INC.  
Newark, New Jersey.

☐ I enclose one dime. Send me by return mail your booklet Q7, "How I Put Up a Complete Radio Station in 2 Hours."

☐ I enclose one dime. Send me by return mail your catalogue CQ7, of "Professional Radio Equipment at Amateur Prices."


Name .....

Address .....

City..... State.....



# ASSURANCE

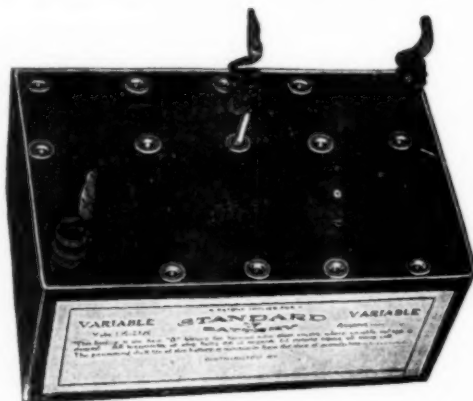

Cast en bloc  
Moisture proof  
Ruggedly Built

Fully Guaranteed  
Long Life  
Silent Performance

When you need a "B" battery and want to feel assured of long life and satisfactory service, buy the guaranteed STANDARD VT BATTERY. Built into the STANDARD VT BATTERY is quality—every STANDARD VT BATTERY is a solid moulded unit of power that will give the service which you expect.

Reasonably priced, these batteries are offered to meet the pockets of all. The next time you are in need of a "B" battery ask your dealer about the STANDARD VT BATTERIES, especially our #7600, which are now in the hands of the most reliable dealers throughout the United States and Canada.

| Number | Description               | Price  |
|--------|---------------------------|--------|
| 7623   | Small type untapped       | \$1.50 |
| 7625   | Large type untapped       | 2.65   |
| 7600   | Large semi-variable type  | 3.00   |
| 7650   | Large type fully variable | 3.50   |

DEALERS—Have you our literature and prices?

## Pacents Electric Company, Inc.

Louis Gerard Pacents, President

SOLE DISTRIBUTORS FOR

Wicony's Complete Line of "Eventual" Apparatus.

Duo-Lateral Coils,

Pacents Universal Plugs,

Sullivan Apparatus,

Standard VT Batteries,

Dubilier Condensers,

Seibt Condensers,

Special Distributors for Brandes Phones

150 Nassau Street,

Telephone  
Beekman 5810

New York City



# QST

## The Official Organ of the A.R.R.L.

VOLUME IV

JULY, 1921

No 12

|                                       |  |     |
|---------------------------------------|--|-----|
| Modulation in Radio Telephony—Part I  | <i>R. A. Heising</i>                   | 7   |
| The Troubles of a Trouble Shooter     | <i>Radiotron Mike</i>                  | 12  |
| Power Factor in Oscillating Circuits  | <i>The Editor &amp; S. E. Anderson</i> | 13  |
| The Ideal Relay Spark Station—Part II | <i>R. C. Denny</i>                     | 18  |
| Spark Reception on Honeycombs—Part I  | <i>Chas. Kingon</i>                    | 21  |
| Radio Market News Service             |  | 24  |
| A Cup for Summer Achievement          |  | 25  |
| First National A.R.R.L. Convention    |  | 26  |
| A Sure-Fire C.W. Circuit              | <i>E. W. Whittier</i>                  | 27  |
| QRX for a New O.W.                    | <i>Irving Vermilya</i>                 | 29  |
| All Set to Perforate QRN              |  | 31  |
| Editorials                            |  | 33  |
| The Operating Department              |  | 35  |
| Calls Heard                           |  | 46  |
| May Station Reports                   |  | 48  |
| Who's Who in Amateur Wireless         |  | 49  |
| Amateur Radio Stations                |  | 50  |
| "Strays"                              |  | 53  |
| With the Affiliated Clubs             |  | 55  |
| Radio Communications by the Amateurs  |  | 57  |
| Classified Advertisements             |  | 116 |
| QST's Index of Advertisers            |  | 119 |

QST is published monthly by The American Radio Relay League, Inc., at Hartford, Conn. Kenneth B. Warner (Secretary, A.R.R.L.), Manager and Editor.  
Subscription price in United States, Possessions, and Canada, \$2.00 per year.  
Foreign, \$2.50. Single Copies, 20 cents.  
Entered as second-class matter May 29, 1919, at the post office of Hartford, Connecticut, under the Act of March 3, 1879.  
Copyright, 1921, by The American Radio Relay League, Inc.  
Title registered at United States Patent Office.

THE AMERICAN RADIO RELAY LEAGUE, Inc.  
HARTFORD, CONN.

# THE AMERICAN RADIO RELAY LEAGUE

"A national non-commercial organization of radio amateurs, bonded for the more effective relaying of friendly messages between their stations, for legislative protection, and for scientific growth."

## OFFICERS

President  
**HIRAM PERCY MAXIM**  
Hartford, Conn.

Vice President  
**CHAS. A. SERVICE, JR.**  
Bala, Pa.

Traffic Manager  
**F. H. SCHNELL**  
1045 Main St.,  
Hartford, Conn.

Treasurer  
**A. A. HEBERT**  
Nutley, N. J.

Secretary  
**K. B. WARNER**  
Hartford, Conn.

## DIRECTORS

**A. E. BESSEY**  
Sunnyvale, Calif.  
**V. F. CAMP**  
Brightwaters, L. I.  
**J. M. CLAYTON**  
Little Rock, Ark.  
**F. M. CORLETT**  
Dallas, Tex.  
**S. KRUSE**  
Washington, D. C.  
**W. T. GRAVELY**  
Danville, Va.

**F. F. HAMILTON**  
Indianapolis  
**A. A. HEBERT**  
Nutley, N. J.  
**HIRAM PERCY MAXIM**  
Hartford, Conn.  
**C. A. SERVICE, JR.**  
Bala, Pa.

**H. L. STANLEY**  
Babylon, L. I.  
**C. H. STEWART**  
St. David's, Pa.  
**K. B. WARNER**  
Hartford, Conn.  
**M. B. WEST**  
Waukegan, Ill.  
**F. H. SCHNELL**  
Hartford, Conn.  
**H. M. ANTHONY**  
Muncie, Ind.

## OPERATING DEPARTMENT

### ATLANTIC DIVISION

Manager  
**Chas. H. Stewart**  
St. David's, Pa.  
Asst. Mgr., Central Sec.  
**C. J. Goette**  
1624 Hamilton Ave.  
Woodhaven, L. I.  
Asst. Mgr., Southern Sec.  
**Edw. B. Duval**  
3909 Cottage Ave.  
Baltimore, Md.

### EAST GULF DIVISION

Manager  
**E. H. Merritt**  
192 W. North Ave.  
Atlanta, Ga.

### CENTRAL DIVISION

Manager  
**R. H. G. Mathews**  
6488 Ravenswood Ave.  
Chicago  
Assistant Manager  
**L. A. Fense**  
2256 W. 24th St.  
Chicago

### ALASKAN DIVISION

Manager  
**Roy Anderson, 7IT**  
P. O. Box 206  
Ketchikan, Alaska

### WEST GULF DIVISION

Manager  
**Frank M. Corlett**  
1101 East Eighth St.  
Dallas, Tex.  
Assistant Manager  
**Raymond L. White**  
900 No. Preston St.  
Ennis, Tex.

### PACIFIC DIVISION

Manager  
**A. E. Bessey**  
Sunnyvale, Calif.  
Assistant Manager  
**E. G. Arnold**  
181 No. 17th St.  
San Jose, Calif.

### ST. LAWRENCE DIVISION

Manager  
**Albert J. Lorimer**  
243 Mackay St.  
Montreal, Que.

### ONTARIO DIVISION

Manager  
**A. H. Keith Russell**  
353 Markham St.  
Toronto, Ont.

### DAKOTA DIVISION

Manager  
**Boyd Phelps**  
3344 First Ave., South  
Minneapolis, Minn.

### NEW ENGLAND DIVISION

Manager  
**Guy R. Entwistle**  
137 Sutherland Road  
Brookline, Mass.

### ROANOKE DIVISION

Manager  
**W. T. Gravelly**  
854 Main St.  
Danville, Va.

### DELTA DIVISION

Manager  
**John M. Clayton**  
1301 Welch St.  
Little Rock, Ark.

### ROCKY MOUNTAIN DIV.

Manager  
**M. S. Andelin**  
Richfield, Utah

### MIDWEST DIVISION

Manager  
**L. A. Benson**  
4942 Wiesehan Ave.  
St. Louis

### NORTHWESTERN DIV.

Acting Manager  
**R. T. Galyean**  
460 Miller St.  
Portland, Ore.

Asst. Mgr., Eastern Sec.  
**H. E. Cutting**  
Box 517,  
Bozeman, Mont.


## ADVISORY TECHNICAL COMMITTEE

**C. S. BALLANTINE**  
**WM. C. BALLARD, Jr.**  
**LEROY M. E. CLAUSING**  
**FRANK CONRAD**  
**LEO C. YOUNG**

**MINTON CRONKHITE**  
**J. H. DELLINGER**  
**C. L. FARRAND**  
**PAUL F. GODLEY**

**L. A. HAZELTINE**  
**C. D. TUSKA**  
**R. H. G. MATHEWS**  
**J. O. SMITH**  
**S. KRUSE**

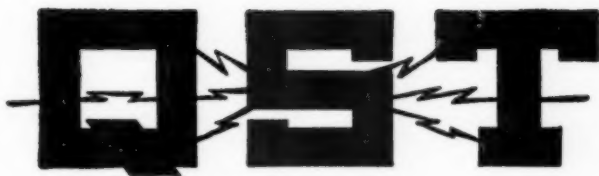Address General Correspondence to Executive Headquarters, Hartford, Conn.



A Magazine Devoted Exclusively to the Radio Amateur

## Modulation in Radio Telephony

By R. A. Heising \*

Presented at Radio Club of America, Columbia University, Feb. 25, 1921.

In Two Parts: Part I.

Here at last is really authoritative information for the amateur on radiophones. Mr. Heising has given the amateurs a splendid paper couched in terms they can understand and we consider it the best article on the subject it has yet been our pleasure to present. Incidentally it should settle once and for all the argument about grid leak vs. constant current modulation.—Editor.

### The Modulated Antenna Current

The average radio amateur on entering the radio telephone field, must bear in mind the fact that he has much to learn to make a satisfactory telephone set that was not necessary for a telegraph set. Also, that because the nature of the signals to be transmitted is different, certain methods of operation and certain requirements which were proper for telegraphy are decidedly improper for telephony. Neglect of these facts and a blind effort to apply to telephony the rules for telegraphy will result in a considerably poorer set than should be the case.

Before discussing any of the systems of modulation, it appears desirable to point out some of the essential facts concerning radio telephony. By doing so, the reason for many modulation circuit connections will be better understood and the finer points which distinguish a poor arrangement from a good one will be appreciated. A study of the form of the antenna current as influenced by a signal will give us many pointers as to the best arrangements for a good circuit.

Human speech, which is the signal to be transmitted in radio telephony, consists of an aggregation of frequencies lying largely between 200 and 2000 cycles per second, having various amplitudes, periods of duration, and transients at the beginning and end, so arranged as to convey information to the listener. To convey the human voice

by radio it is necessary to provide a system which will convey all of these frequencies; that is, it must reproduce each frequency at the receiving end and reproduce it with the proper amplitude in comparison with the others, and reproduce its "transient" or amplitude variation at the beginning and the end, and it must do this for each frequency while doing it for others. This is enormously more difficult than transmitting a telegraph signal. To transmit a telegraph signal it is only necessary to produce some kind of a noise at the receiving station and the signalling is done by varying the duration of this noise. The noise does not have to bear any relation to any noises at the transmitting station but needs only to be something the receiving operator can hear. In telephony, any noise will not do, because the noise to be reproduced must be identical with the noise produced at the transmitting station, it must contain the same frequencies, give them their relative amplitudes, and have them last the proper length of time. The complexity of the signal necessitates a control of the radiated wave not necessary in a telegraph system and it is the control which is such an important part of the radio telephone circuit.

An example of a radio telephone wave is indicated in Figure 1. The carrier wave amplitude is here varied according to the wave form of the signal. The precision of control required to cause the proper antenna current, regardless of the millions of forms the signal may take, is quite evident. This signal on being received and rectified

\* Engineer Research Laboratories of American Telephone & Telegraph Co. and Western Electric Co., Inc.

will reproduce the modulating signal, since the rectified current will be substantially proportional to the high frequency amplitude.

In the discussion of a radio frequency current, it is usual to assume a simple signal as the modulating signal, as most of the necessary information can be secured with that assumption. It is assumed that the signal to be transmitted is a single sine wave of some audio frequency such as 800

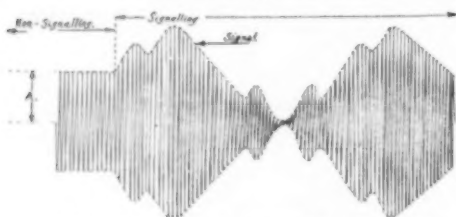


FIG 1 H.F. Wave Modulated by a Speech Signal

cycles. A modulated antenna current carrying this signal is represented in Figure 2. This antenna current is expressed by the equation

$$i = A (1 + K \sin p t) \sin w t \quad (1)$$

In this equation  $\sin w t$  represents the radio frequency wave and  $\sin p t$  the signal frequency wave.  $K$  is known as the modulation constant and is usually expressed in percentage form. When no signal is being transmitted the high frequency amplitude is  $A$  and the constant  $K$  is zero. If a signal of such a loudness as to make  $K$  equal to unity is spoken, the term  $1 + k \sin p t$  varies between values of 0 and 2 depending upon  $\sin p t$  passing through the values  $-1$  and  $+1$  and the amplitude of the high frequency current varies between zero and  $2A$ . That is, the modulation of the current causes it to rise, as well as fall, and it should rise as much above as it falls below. If the system is so constructed that the amplitude does not rise, but is varied downward only, a speech signal will produce a wave of the form shown in Figure 3. In-

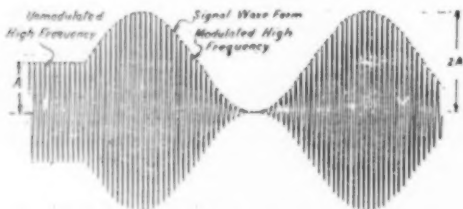


FIG 2 H.F. Wave Modulated by a Single Sine Wave Signal

spection of this indicates that a great distortion is produced. The amplitude should vary so as to follow the dotted signal line, but the failure of the system to cause the current amplitude to rise chops off one-half

of the speech signal and gives an imperfect reproduction at the receiving end. This one-sided or improper modulation is to be avoided if possible.

Those who are acquainted with elements of trigonometry will observe that we can change the form of the equation (1). Such a change does not affect its validity at all but does point out one or two new facts. The equation can be changed to:

$$i = A \sin w t - \frac{AK}{2} \cos (w + p) t + \frac{AK}{2} \cos (w - p) t \quad (2)$$

This equation indicates that a sustained wave, such as shown in Figure 2 and represented by equations (1) and (2), can be said to consist of three frequencies—

The radio carrier frequency  $\frac{w}{2\pi}$  of amplitude  $A$

An upper side frequency  $\frac{w + p}{2\pi}$  of amplitude  $\frac{KA}{2}$

And a lower side frequency  $\frac{w - p}{2\pi}$  of amplitude  $\frac{KA}{2}$

When no signal is being transmitted,  $K = 0$  and the only frequency is the radio carrier frequency with amplitude  $A$ . As soon as the signal begins to modulate the wave,

the side frequencies  $\frac{w + p}{2\pi}$  and  $\frac{w - p}{2\pi}$  of amplitude  $\frac{KA}{2}$  appear while the carrier

remains unchanged. The modulation of the radio wave thus takes the form of the production of side frequencies. At the receiving station, the beats between the carrier frequency and the side frequencies, when rectified, produce the frequency of the transmitted signal.

If the signal to be transmitted consists of many frequencies such as 200, 500, 1200, and 2000 cycles, the frequencies in the antenna will be the carrier frequency  $f$  and the side frequencies  $f + 200$ ,  $f - 200$ ,  $f + 500$ ,  $f - 500$ ,  $f + 1200$ , etc. In telephony, human speech contains frequencies largely between 200 and 2000 cycles so that to transmit speech by radio we must expect to have in the antenna the carrier  $f$  and the side frequencies  $f + (200 \text{ to } 2000)$  and  $f - (200 \text{ to } 2000)$ . That is, if we use a carrier of 50,000 cycles there will occur in the antenna the frequencies—



The carrier 50,000 cycles  
 Lower side frequencies between 48,000 and 49,800  
 Upper side frequencies between 50,200 and 52,000  
 giving us a band 4,000 cycles wide necessary for the transmission of speech.

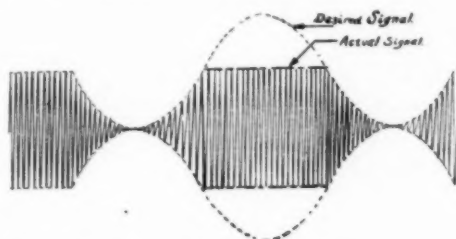


FIG. 3 An improperly Modulated Wave

Having described in detail the important features of a radio telephone wave, we are now in a position to point out a few facts of vital interest to an amateur. In radio telegraphy, it is customary to tune and adjust the set for the maximum antenna current that it is possible to obtain. Signalling is then done by making and breaking the circuit causing the antenna current to fall to zero in the spaces and rise to the maximum in the dots and dashes. The greater the antenna current, the greater is the VARIATION in the current when signalling. The VARIATION in the current is what is desired and the maximum antenna current is tuned for only because the change in current between that value and zero gives the greatest VARIATION. The VARIATION in the current while signalling is thus the factor which determines the loudness of the received signal. In telephony the VARIATION in the antenna current while signalling is also the determining factor as regards loudness of signal or distance to be reached, but the amateur must remember that the determination of the maximum VARIATION is not so easily done as in the case of telegraphy. The antenna current is not merely reduced to zero in spaces and then returned to the normal value, but it varies through all possible values from zero to TWICE THE NON-SIGNALLING VALUE. In telephony the current is either zero or maximum. In telephony it has a certain non-signalling value ( $A$  in equation 1 and Figure 2) and takes all possible values between 0 and twice the non-signalling value ( $2A$  in equation 1) and the apparatus must be capable of producing any possible value between these limits. Therefore the amateur is warned that when he tunes his set up for the non-signalling value  $A$ , he must see that the system that he uses has some variable in

it which when operated upon by the speech will make the set give  $2A$  in the antenna. Failure to remember this will result in producing one-sided modulation as shown in Figure 3.

In telegraphy, it is possible to determine with the antenna ammeter alone the VARIATION in antenna current while signalling. When the key is open the current is zero, when it is closed the current is a maximum. In telephony, unfortunately for the amateur, there is no simple apparatus to tell what the variation is, or to tell him when he is getting complete modulation. There are, however, two indicators which will give an operator some idea of his degree of modulation. The first is the variation in the reading of the antenna ammeter. When a wave is completely modulated by a symmetrical signal in a properly adjusted set, the antenna ammeter reading increases by about 22½%. (To be exact, the reading is  $\sqrt{1.5}$  times the non-signalling value). This must not be taken as an infallible guide as it is not easy to get a set adjusted so as to make this indicator worth much. A badly distorted wave will give a reading variation of even greater than this amount. Judgment should not be passed upon this evidence alone. The second indicator is the quality of the received signal. The signal from a set which tends to "over-modulate" has a peculiar sound often described as "tinny". It sounds like the voice of a person holding a sheet of paper against the lips. It is caused by the over-modulating action

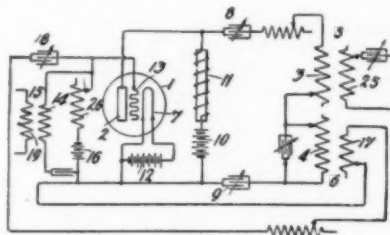


FIG 4 Colpitts System

cutting off the peaks of certain loud signal waves. The identification of this kind of distortion can be learned by observation. The amateur must not let his imagination get the better of him and confuse microphone distortion or other noises and distortions with this over-modulation distortion as many do. He should learn to identify the sound under conditions that will not give him the wrong impression of its character. This indicator is the only cheap indicator of complete modulation at present available to the amateur. It is much more reliable than the antenna ammeter method,

but indicates only over-modulation. It will be found, however, to be useful.

Having discussed the nature of a modulated antenna current, we are now in position to discuss some of the systems which produce it.

#### Colpitts System

Among the systems of modulation which may be of interest may be mentioned Colpitts' system shown in Figure 4 and a modification of it, the Logwood system shown in Figure 5. This system is

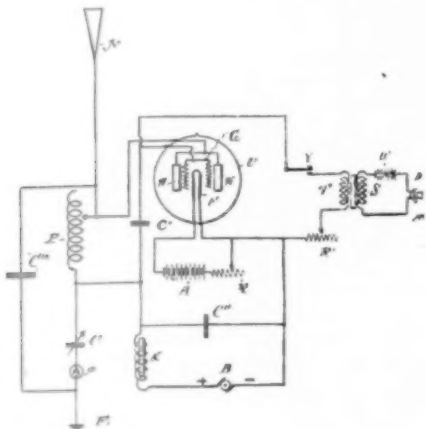


FIG 5 Logwood's Circuit

primarily an oscillator upon the grid of which the speech signal is impressed. In this circuit the grid acts as control member for the amplitude of the oscillation. However, as the grid is also used for controlling the current through the tube while oscillating, it is compelled to perform two different functions simultaneously and unless the circuit is very carefully adjusted, it fails in either one or the other. Usually the amateur will adjust the oscillator to get the most power into the antenna and then impress the signal upon the grid expecting perfect operation as easily as is secured in telegraphy by opening and closing the key. Such, however, is not what results. This system gives about 20% modulation, which is quite poor. To adjust this circuit to give complete modulation requires much more complicated apparatus that the amateur is likely to possess, and there is added the fact that the adjustment is not only difficult to obtain, but is difficult to maintain. The efficiency of such an arrangement is not very high. For an amateur who wishes to secure good range the system is not advised. If, however, one is merely interested in something which will talk a short

distance, it is one of the easiest systems to construct.

#### Van der Bijl System

A system which we have used in many of our experiments is shown in Figure 6 and is known as the Van der Bijl system. It falls under a classification of systems known as "amplifier systems" in which a small amount of power is modulated and then the modulated current is amplified into the antenna. The modulation is done in this circuit by means of a tube in which we make use of its curved characteristic. In Figure 6 will be observed a small high frequency voltage with the time axis running downward, which is impressed upon the grid and whose position on the characteristic curve is varied by the signal to be transmitted. The varying slope of the characteristic curve causes the high frequency current in the plate circuit to change, depending upon what part of the characteristic curve this small voltage wave operates. If it operates around the point marked B, it produces the amplitude indicated directly to the right of the letter B. If it operates around the point marked C, it produces a much greater amplitude as is indicated to the right of that letter. If the signal should slide this wave down to the point A, practically no alternating space current occurs. We thus have the phenomenon of being able to get any alternating space current we desire by merely sliding the high frequency input up and down the curve. If we use the signal to slide this small input up and down, the amplitude produced in the plate circuit is such that a line drawn through the peaks (the envelope of the peaks, so to speak) is the wave form of the signal desired. Having once secured a small amount of modulated high frequency current, it is only necessary to amplify it up to the

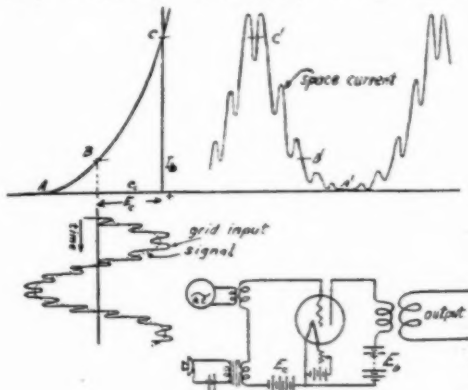


FIG 6 Van der Bijl's System

desired power and put it on the antenna.

This type of system, though fairly simple, is not as good as some to be described later. It is however, as good and as efficient as any other amplifier sys-

tem.  $E_c$  of figure 13) finding the values at which he gets maximum current and minimum current in the antenna. After having determined these values, he should set the negative voltage at about the value half-

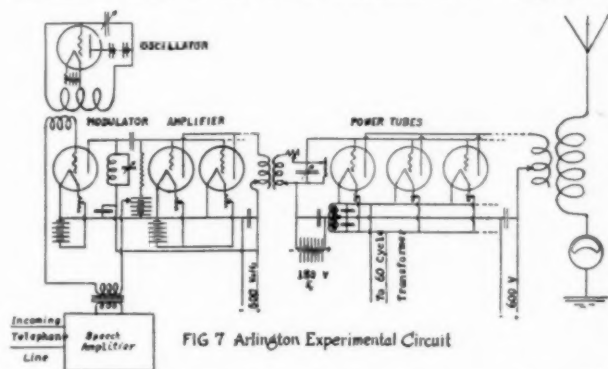


FIG 7 Arlington Experimental Circuit

tem. That is, it is as good as any system in which a small amount of power is modulated by some means and then amplified to the desired point. The efficiency in these systems is determined by the efficiency of the amplifier and has very little connection with modulating arrangement itself.

The circuit which we used in our test at Arlington, 1915, is given in Figure 7. The average amateur should be able to pick out the oscillator, modulator and amplifiers in this circuit without much trouble.

#### Modulating Amplifier System

A modified form of the Van der Bijl system is that indicated in Figure 8. It is known as the "modulating amplifier" system. It differs in detail from the previous arrangement in that the high frequency wave impressed upon the grid is equal to or much larger than the signal wave, instead of being much smaller, and in that the modulator not only modulates, but amplifies and delivers the modulated high frequency current directly to the antenna. This system should be of some interest to an amateur because it is one he can quite easily construct. It requires, however, two or more tubes. One of the tubes must be used to generate the high frequency oscillations, while the other is used as the modulating amplifier. These tubes may be of different sizes; the one generating the high frequency oscillations does not have to be over 1/10 the power rating of the modulating amplifier tube. If the tubes are of very large size, it may be necessary to use a speech amplifier between the microphone and the modulating amplifier.

In a system of this kind, it is desirable to have a high frequency amplitude several times the signal frequency amplitude. The experimenter should vary the negative voltage ( $E_c$  of Figure 8 or

$E_c$  of figure 13) finding the values at which he gets maximum current and minimum current in the antenna. After having determined these values, he should set the negative voltage at about the value half-way between these limits, the value being that which will give  $\frac{1}{2}$  the maximum antenna current. The circuit it then properly adjusted for speech since the non-signalling value is  $\frac{1}{2}$  the maximum possible. He must not feel that he is cheating himself out of some power when he reduces the antenna current to half the maximum, because he is not. The speech signal coming in and being impressed will momentarily oppose the battery at times and cause the power to rise to the maximum, and at

other times will momentarily aid the battery, causing the power to decrease to zero. He has a value about which the antenna current can both increase and decrease by the mere changing of the potential of the grid. This gives him a circuit adjustment which will produce an antenna current as indicated in Figure 1 or Figure 2. It can rise to a higher value as well as decrease to a lower value by a mere potential change which in this case is his grid potential, and he can get a properly modulated, if not a completely modulated, antenna current. The natural inclination of the amateur is to leave the value of  $E_c$  such as to give him the maximum antenna current. If he does this, he can only secure an improperly modulated current such as in Figure 3. His signal impressed from the transmitter and the transformer has alternating potentials which in some instances aid the battery

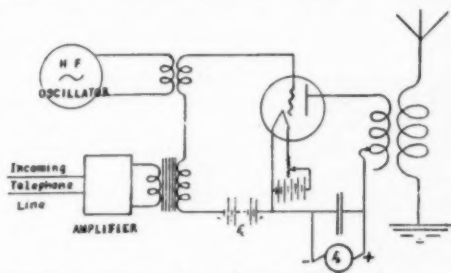


FIG 8 Modulating Amplifier Circuit

$E_c$ , and other instances oppose it. At those instances where it aids the grid battery and makes the grid become more negative, the antenna current will be modulated in a downward direction. But in those instances when it opposes the grid battery and reduces the grid potential it should raise the antenna current. If he does not

make the non-signalling antenna current half the maximum by increasing the negative grid battery he will be operating about the point of maximum antenna current and nothing he can do on the grid can ever make the current any greater. Since his speech signal contains equal amounts of

his negative grid voltage to such a value, as mentioned previously, as will allow the incoming speech signal to oppose the battery and increase the antenna current at times as well as to aid it and decrease it at other times.

A set of curves such as a person would get from a modulating amplifier is indicated in Figure 9. The curve for antenna current ( $I_a$ ) was secured by slowly varying the negative grid potential and taking readings of the antenna current at the same time. As we approach the value of 100 volts on the grid, it is seen that the antenna current is rising so slowly that it is not desirable to go any farther in that direction. In fact, for most work, it is better not to go to a smaller value than 200 volts. This is marked by the letter Z. Half way between this value and that value W at which the antenna current is reduced to zero is marked the value X which is the amount of negative voltage we would apply to the grid when not signalling. If now, we produce by means of a microphone and transformer the simple signal indicated with the time axis running downward, we can cause the potential of the grid to vary. The potential of the grid is the sum of the constant negative potential 280 volts and the varying signal potential, and the grid's potential will range between the points W and Z, causing the high frequency antenna circuit to vary between the maximum and minimum values.

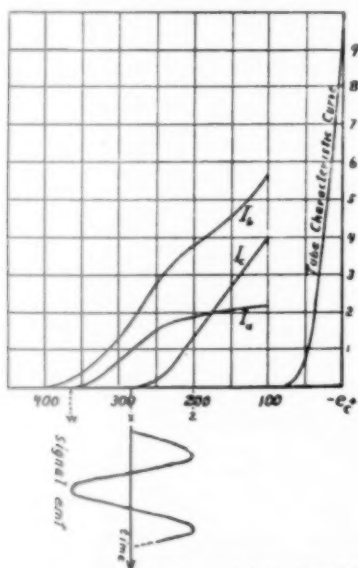


FIG. 9 Behavior curves for the Modulating Amplifier

positive and negative potentials which alternately aid and oppose the battery, he will get modulation only for that half of the signal which aids the battery, giving him the identical improperly modulated signal represented in Figure 3. To secure the complete radio signal, he must increase

(Part II, in our next issue, will deal with the constant current system and master oscillators, and concludes with circuits, specifications and constants of systems particularly suited to amateur use. If you're at all interested in radiotelephony, don't miss it.—Ed.)

## The Troubles of a Trouble Shooter

By Radiotron Mike

PHILLIP ALGERNON FITZDOODLE was an Inquisitive Youth with a Homely Mug who got mixed up with a Farmers' Line telephone company because he needed a pair of shoes and Some Other Things. It was for this reason that he became a Sticker and in due time secured a fair knowledge of Dry Batteries and Pony Insulators. One day he felt a sudden urge to gain Distinction and he applied for a job of Trouble Shooter with a Big City Exchange where he found Higher Poles to climb and More Trouble to shoot for about the Same Money. This grieved him and he looked about for some One to share his Troubles with him. After he had received his Seventh Check he met a Baby Doll. In a short time they were Married and went to

live on the Third Floor. Phillip thought that his troubles had greatly Diminished but such was not to be the case.

One day a Squeak Box Pounder interested Phillip with a flow of Wireless Lingo and in a few hours he was talking about spark-gaps, oscillation transformers, radio calls, amplifiers, loose couplers and rheostats. The Wireless Bug had nibbled him and Bit Hard. Of course Phillip thought he would be Satisfied with 'most any kind of a set but such was not to be in the life of Phillip Algernon Fitzdoodle.

The Local Relay League was on the job. Soon an Amateur who was short of Cash but long of Wind appeared in the Scenery with a Home Made Set which he would gladly Sacrifice at a 1914 Figure because his Pa and Ma were going to move to



California. Opportunity had surely taken Phillip's door to Wirelessness off its hinges. He eyed the Outfit like a little Sod Buster does his first Pin Wheel and managed to scrape up enough Cash to call the Static Collector his very own. It looked like he was soon to become the sole owner of a Beautiful Collection of Junk but such was not to be.



Fitzdoodle's next problem was to get the Sweetest Girl to permit him to install Signor Marconi's Invention in the kitchen. So taking a chew of Ever Sweet and with his Rotary gaining in speed he started homeward looking like a Moving Van. When Phillip arrived at the Proper Address the Sweetest Girl met him on the First

Flight with an Icy Stare. She thought he had robbed a Freight Train and the Wild Look in his eyes indicated to her that the Authorities were hot on his trail. Of course her fears were without a Ground and she was only Up In The Air. Phillip told her what had happened from the time the bug had Sampled him until it had socked in its stinger to the hilt. He explained that by hooking up the instruments Properly which he understood Perfectly that both could hear the zippety zips of wireless operators many meters away. The only meters she knew anything about were Gas Meters and they were very expensive. She thought that all meters were alike. Phillip received the Coolest Reception that had ever been held in his Honor. He knew that the Great Out Of Doors was very much crowded in his neighborhood and that His Landlady would land on him if he attempted to erect an aerial in her Roof Garden. So he promised his Unknown Factor everything that he could not deliver from a High Powered flivver to a Seal Skin coat next winter but she would not budge. Phillip Algernon Fitzdoodle who had been Master of the Apartment was now an Unwilling Slave to a Beautiful Blue Eyes who was often too lazy to punch holes in her own dough-nuts. This could not continue with Phillip Algernon Fitzdoodle.

As Phillip sat looking out of the window wondering what he could do to make his Bitter Sweet oscillate the telephone bell rang. The Voice of a member of the Local Relay League said that he had heard Phillip was interested in Wireless and invited him to call and "Listen In" on a Real

(Concluded on page 17)

## Power Factor in Oscillating Circuits

**F**EW articles in QST have started so much deep thinking and so much violent discussion as the "Wherefores" of Mr. M. B. West in February's QST. We published a few communications on the subject in the April number but they were merely the advance guard of an army of letters of such proportions that we just had to stack them up in the corner until we had a holiday to dig into them and see what all the shooting was about.

We acknowledge particularly interesting communications from Messrs. S. E. Anderson, Brooklyn; M. B. West, Waukegan, Ill.; E. W. Stone, San Francisco; John K. Andrews, Pittsfield, Mass.; Fred. Winkler, Jr., New York; J. A. Morris, New Britain, Conn.; F. F. Hamilton, Indianapolis; and E. L. Powell, Washington, D. C. Chief

discussion has centered on the question of power factor in oscillating circuits—certainly a thing that every radio man *ought* to know about—and we have been enjoying the spectacle of two about equal groups of well-versed men, most of them engineers, taking diametrically opposite views of a vital subject, one side insisting that power factor in an oscillating circuit can be nothing other than unity, while the other side just as strongly contests that it is zero. Now textbooks define the matter pretty well, but all of these men are intelligent, so it isn't likely that we would find half of them just uninformed—the matter isn't nearly that simple. The trouble is largely in that half of the time they aren't talking about the same thing! Surprising, however, is the confusion regarding fundamental A.C. theory and

definitions, and wonderful have been some of the combinations of vector diagrams for parallel resonance circuits accompanying formulae for series circuits, and vice versa, and great has been the dispute! All over the country there have been signs of activity, and, as we know from experience, if there's anything that will drive a man looney it's to attempt to review A.C. theory at one sitting—or even in a week. But cobwebs have been brushed off the old textbooks, "slip-sticks" broken out to light of day, headaches acquired with the sudden realization that even simple algebra was a forgotten language; wives, sweethearts and radio sets have been neglected, two chaps have even come to Hartford to argue the matter; and surely much good has come of all of it.

We are not half sure in our own minds that enough light has been shed on the subject but certain things do stand out and should be realized in clearing the air for further discussion of possible practical improvements in circuit arrangement:

(1) The theory of power factor in radio frequency circuits isn't different from that applying to A.C. power circuits—the well known formulae and practices still hold.

(2) The closed oscillating circuit of a spark transmitter is a series circuit, not a parallel circuit, and such a series circuit has but one "current" flowing thru it.

(3) In such an oscillating circuit the capacitive reactance volts are numerically equal to and opposite in polarity to the inductive reactance volts, whereby the two

reactances cancel. The only remaining voltage drop occurring is that across the apparent resistance of the circuit, which voltage (supposing a perfect condenser without phase displacement) is always exactly *in phase* with the current. The power factor is therefore *unity*, not zero.

(4) It is true that there are large voltages across both the inductance and capacity but they exactly offset each other at resonance and the true power is found by multiplying the current (there is but one current in a series circuit) by the voltage *across the circuit* (not across either inductance or capacity). No amazing values of watts will then be found.

(5) This should not be confused with the fact that there truly is a phase angle of 90 degrees between the current and the voltage across either inductance or capacity. It is this phase difference that has sent so many good men on the wrong track, but it has no bearing on the power factor of the circuit as a whole which must be computed on the resultant voltage across the circuit as a whole and not on that across any one part of it.

(6) We could discourse somewhat similarly upon a parallel circuit, where again the power factor at the resonant frequency is always close to unity and cannot be otherwise.

With which we take pleasure in presenting the following article which by correcting any misimpressions concerning the fundamental *theory* will, we trust, settle the dust for further discussions relating to improved *design*.

## Some of the Wherefores of Radio

By S. E. Anderson

WE all remember the articles by Mr. M. B. West in the February number of QST, in which he frankly invited discussion of a number of the perplexing everyday problems of radio. The opening salvo of this discussion appeared in the April number, and certainly emphasized the fact that there are a number of things in this great game of ours that it will pay us to stop and think about.

I am writing this article in order to throw what light I may on some of these problems, which I have endeavored to discuss in the light of my own experience, tho I wish it thoroughly understood that I am laying no claim to infallibility. The larger part of the discussion has been concerned with that elusive young scamp, power factor. I think our chief trouble has been that we are a bit afraid of it, just because we are dealing with a few more cycles than most of the text books talk about.

To touch briefly on the other points of Mr. West's article, his first question is, "Why is there an optimum wave length

for any given antenna?" The letter, if not the spirit, of Mr. Stone's explanation in the April QST is, I think, entirely correct. We have a number of factors involved, some increasing with wave length, and some, notably the radiation resistance, being much smaller for the longer wave lengths, and the point at which the sum of these various factors is a minimum is the best operating wavelength. But I most certainly agree with Mr. West that in view of the extremely varied conditions under which amateur antennae are erected it is almost impossible to calculate this optimum wave length in advance. From the waves one hears on the air, it is generally more than two hundred meters!

I will not attempt to discuss the apparent greater efficiency, measured in miles per watt, of C.W. apparatus. I must admit that I have never been entirely satisfied with the usual explanations offered, but I have none that are any better, and the factors involved are so numerous that it

could well form the subject matter for a series of articles by someone with experience in the C.W. field.

Now let us look at this matter of power factor, avoiding mathematics as much as possible, but not being afraid to use it where it will help. I have of necessity assumed that we are all either familiar with the proof of the fundamental relations which I state or else we don't care anything about this proof. These relations, in the final analysis, can be developed only by the use of The Calculus, for which I am sure we all have, to say the least, the most wholesome respect.

It can be safely assumed, I think, that we are all familiar with the fact, as explained in Mr. West's article, that with

the voltage across the condenser,  $\frac{I}{\omega C}$ .

The vector sum of these three potentials is the total impressed voltage, represented by vector E. In general this voltage will not be in phase with the current, the cosine of the angle  $\theta$  between them being called the power factor, and it may be shown that the power is

$$W = I^2 R = EI \cos \theta \quad (2)$$

Now it is obvious from equation (1)

that if we make  $\omega L$  equal to  $\frac{1}{\omega C}$ , the

current will be a maximum and equal to  $\frac{E}{R}$ ,

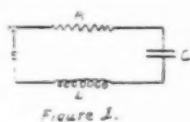


Figure 1.

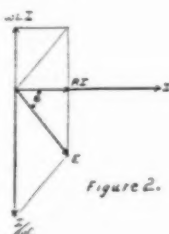


Figure 2.

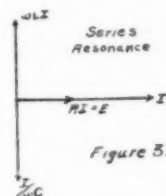


Figure 3.

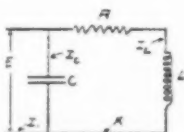


Figure 4.

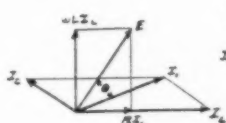


Figure 5.

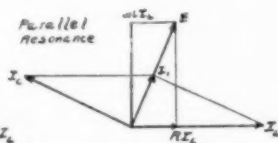


Figure 6.

alternating current the current flowing through an inductance lags behind the voltage across it, while the voltage across a condenser lags behind the current flowing through it. If we have a simple series circuit as shown in figure 1, consisting of a resistance of R ohms, an inductance of L henries, and a capacity of C farads, and apply to the circuit a sinusoidal E.M.F. whose effective value is E volts, and whose angular velocity is  $\omega$  radians per second, where  $\omega$  is  $2\pi$  times the frequency in cycles per second, it may be shown that the effective value of the current through the circuit will be

$$I = \frac{E}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad (1)$$

A vector diagram will be most helpful in our discussion, and one is shown in figure 2. Starting with the current I, we draw the vector representing it, and in phase with it the vector RI, the voltage across the resistance. 90° ahead of the current is the voltage across the inductance,  $\omega LI$ , and 90° behind the current is

and the vector diagram will be of the form shown in figure 3, the current and voltage now being in phase and the power factor unity.

Let us now consider the case of parallel resonance, in which we have an inductance, resistance, and capacity connected as shown in figure 4, the constants being represented and measured in the same manner as for equation (1). With a sinusoidal E.M.F. applied at E, the current through the condenser will be

$$I_c = -\omega CE \quad (3)$$

and the current through the inductance and resistance will be

$$I_L = \frac{E}{\sqrt{R^2 + \omega^2 L^2}} \quad (4)$$

The vector sum of these two currents is the total current, or

$$I = E \sqrt{(\omega C - \frac{\omega L}{R^2 + \omega^2 L^2})^2 + (\frac{R}{R^2 + \omega^2 L^2})^2} \quad (5)$$

The vector diagram of this circuit is shown in figure 5. Starting with the current through the inductance,  $I_L$ , we draw the vector representing it, and in phase with it the vector  $RI_L$ , the voltage across the resistance.  $90^\circ$  ahead of the current is the voltage across the inductance,  $\omega LI_L$ , and the vector sum of these two potentials is the total impressed voltage,  $E$ . The current through the condenser, represented by vector  $I_C$ , is  $90^\circ$  ahead of this voltage, and the total current,  $I$ , is the vector sum of  $I_C$  and  $I_L$ . In general this will not be in phase with the impressed voltage, and as before the cosine of the angle  $\theta$  between them will be the power factor.

It is apparent from equation (5) that if we make

$$\omega C = \frac{\omega L}{R^2 + \omega^2 L^2}, \text{ the current has its minimum value of } I = \frac{ER}{R^2 + \omega^2 L^2},$$

and will be in phase with the applied E.M.F., while the vector diagram will be of the form shown in figure 6.

It will be noted that in these equations, the effective resistance of the condenser has been neglected, tho not that of the inductance. The losses in any but the poorest paper condensers are negligible for any analysis which does not require extreme precision, but the resistance of many of the large air core coils used in radio work is frequently of considerable magnitude. In many circuits, however, the resistance may be neglected, and if this is true we have the condition that for either

$$\text{series or parallel resonance } \omega L = \frac{1}{\omega C},$$

and at the resonant frequency the voltage across the series circuit is zero and the current is infinite, while with the parallel circuit the voltage across it at resonance is infinite and the current is zero, as is apparent from an examination of the equations.

Now if we take the circuit shown in figure 1 and connect a spark gap at E, we have the typical oscillating circuit of the spark transmitter, which is the same circuit as would be obtained by taking our "parallel resonance" circuit of figure 4 and inserting a spark gap at X. I think this is one point where some of us have been getting off the track. The ordinary spark transmitter circuit looks like a parallel resonance circuit at first glance, but it is apparent, once it is pointed out, that as far as the radio frequencies are concerned it is a series resonant circuit.

When free oscillations occur in such a circuit as is represented in figure 4 with a spark gap at X, there being no external potential applied at E during the period of oscillation, it may be shown that the instantaneous value of the current is

$$i = I_0 e^{-\alpha t} \sin \omega t \quad (6)$$

where  $I_0$  is the initial current,  $\alpha$  is the damping factor, and  $t$  is the time elapsed since the starting of oscillations. Taking  $E_0$  as the initial potential across the condenser, the values of the constants are as follows:

$$I_0 = \omega C E_0, \quad \alpha = \frac{R}{2L}, \quad \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \quad (7)$$

In any oscillating circuit worth mentioning, the ratio of inductance to resistance is large, so the last term of the expression for  $\omega$  is negligible and it may be written

$$\omega = \frac{1}{\sqrt{LC}}, \text{ which is identical with } \omega L = \frac{1}{\omega C},$$

which, from equation 1, is the condition for resonance of the series circuit, or the frequency of a circuit in which there exist free oscillations is the frequency for which the circuit is resonant, or has unity power factor.

To consider this from the practical man's viewpoint, let us assume for the moment that the circuit did not oscillate at the resonant frequency. The impedance of the circuit is a minimum at this frequency, so if it were oscillating at some other frequency we would have the impossible condition of a current flowing in an electric circuit which was less than the maximum possible current. This oscillating circuit is entirely self-contained with nothing external to it to control the frequency, so it will naturally be the frequency which will permit of the maximum current, or the resonant frequency.

In Mr. West's article, referring to his figure 3, I think his error is in not considering the proper voltages and currents when he talks about power factor. We have a simple series circuit, in all parts of which the same current is flowing. The voltage across the inductance is  $90^\circ$  ahead of this current (with zero resistance), and the voltage across the capacity is  $90^\circ$  behind. Mr. West asks us to consider the power factor at some point such as A, but I know he is thinking of the voltage across the circuit, as shown by his arrows, and the current in the circuit, which have no relation to each other at all. The power factor of this circuit at resonance is unity, and the power in the circuit is the product of the current by the voltage AROUND the circuit, which is only the drop across the resistance of the inductance and the spark gap, if present, and is very small. Thus even tho the current may reach enormous values, its product by the proper voltage gives us a reasonable value for the power. If we have a parallel resonant circuit (figure 4 of this article) such as



occurs with tube hookups, its power factor will also be unity. The voltage  $E$  across the circuit will be very high, and although the current through the condenser ( $I_c$ ) and that through the inductance ( $I_L$ ) may be very large, the current through the circuit ( $I$ ) is very small, so multiplying it by the voltage across the circuit does not give us ten kilowatts from a five watt tube.

With these facts in mind it is apparent that we gain nothing directly from such an arrangement as is shown in Mr. West's figure 4. Any transformer functions by virtue of its inductance, and the phase relations in the transformer windings will be the same whether the windings contain one turn or ten.

From exactly the same considerations, the power factor of our antenna circuit will be unity when it is tuned to resonance. I have never studied the theory of the multiple tuned antenna, but I am sure that its increased effectiveness is due to something other than an improvement in power factor, such as the increase of the ratio of inductance to capacity and ohmic resistance, and the better resulting current distribution over the entire length of the antenna.

Mr. Winkler in his discussion gives us a very good picture of the negative power loops which occur when the power factor is not unity. I think his error is in considering an oscillating circuit as a parallel circuit when he drew the vector diagrams, and then considering it as a series circuit when he wrote the equation, while he also seems to lose sight of the fact that when the resistance is small the frequency of a freely oscillating circuit just naturally has to be the frequency for which the circuit is resonant.

Referring to paragraph 3 of Mr. West's discussion in the April number, it might be well to emphasize that we have resonance when the inductive and capacitive reactances are equal, and that the constants of the latter occur in the denominator. We all know that if we want to obtain the same frequency with twice as much inductance, we require only half the capacity, so we have an infinite number of combinations of inductance and capacity for any given frequency, *but only one pair of values of inductive and capacitive reactance*. I think the other points in this paragraph have been covered.

Referring to paragraph 4, Mr. West is perfectly correct in stating that there is always a critical combination of inductance and capacity which gives the best results for any given wave length. The reason for this is our old friend—resistance. *The optimum combination of inductance and capacity for a given wave length is that combination for which the time constant of the inductance is a maximum, when this time constant is defined as the product of*

*the inductance and the angular velocity,*  
 $\frac{\omega L}{R}$   
*divided by the resistance. (Written —).*

The rigorous proof of this fact is somewhat involved, but its truth is obvious. It simply means that the more efficient we are able to make our inductance coils the better our circuits will be, and that we should choose a coil which has the highest possible time constant over the frequency range it is desired to cover. I had convincing proof of this in some recent work with vacuum tube oscillators, in which replacing a coil by another of the same inductance, but with a time constant about four times that of the first resulted in a great increase in output, as well as a much improved wave form and greater stability, the net improvement being much more than proportionate to the increased time constant of the new coil.

In conclusion I wish to say that I have tried to maintain throughout this article the same spirit which prompted Mr. West's original speculations. It is only by thus sharing our problems and opportunities that we can make any real progress. I have covered most of the major points raised, the space does not permit as detailed discussion as the subject deserves. I have tried to avoid mistakes, but as this is impossible, I shall be glad to have them pointed out, and will welcome additional ideas.

#### THE TROUBLES OF A TROUBLE SHOOTER

(Concluded from page 13)

Set. Could Phillip turn down an offer such as this? He could not, and his promise to appear at a certain place at a certain time was rarely ever a Brass Brick.

It would be easy to tell how it all Happened but let us make a Short Story of it. Phillip did induce his Storm and Strife to accompany him and in an hour both were sitting in front of the Bakelite. A few adjustments by Friend Indeed brought in a few zippety zips and another little Twist and the sweet strains of "Carry Me Back To Old Virginny" floated in from KDKA. Phillip handed his Sour Grapes another set of phones and both listened to the Music until they had to be Kicked Out.

The Sweetest Girl has given up her Sewing Table on which rests a Short Wave Set. Over the sink swings a box aerial. A loud speaker dangles from the spot where a picture of Bread Pudding previously decorated the wall. A shelf in the cupboard is devoted to batteries and Mrs. Phillip Algernon Fitzdoodle is again devoted to her husband.

Phillip often comes home with a pocket full of Trouble Tickets and a Grouch but he tunes up a Real Set and floods his Happy Apartment with Music long after he has finished washing the dishes.

## The Ideal Relay Spark Station

By R. C. Denny, 6CS

In Two Parts: Part II.

### The Spark Gap

This is another part of the apparatus that is generally not so well understood. The spark frequency and the quenching are vital factors in the success of the transmitting set. In the great majority of relay stations the rotary spark is used, and it is generally acknowledged to be the best all-around gap. It gives a fairly good smooth tone over a considerable range of voltages and spark frequencies, and besides is quite easily cooled, in fact is self cooled; and may have very good quenching characteristics also.

Synchronous rotaries are indeed the most desirable, but unfortunately are most impossible to get hold of except at considerable expense. Their speed holds in step with the frequency of the supply current, and the sparks may be timed to occur at the most favorable points of the voltage wave. This condition can be very closely approached with a non-synchronous motor in connection with a rotary gap, if certain conditions are observed.

Spark frequencies of from 500 to 600 per second are quite effective, and besides being pleasant to the ear, are generally high enough to work the condenser up to the power rating of the transformer. A rotary for operation on a 60 cycle system, should be equipped with a rotor having a number of studs equal to some sub-multiple of 60, say 12; and be operated at a speed that will give a spark frequency equal to some multiple of the current frequency, say 600. Thus the 120 alternations or waves per second may be divided up equally, and the spark timed, so that no stud is opposite an electrode at the zero point on the wave. A twelve stud rotor would have to run at 3000 RPM to give 600 sparks per second; while the same spark frequency could be obtained by running a 6 stud rotor at 6000 RPM. For a rotary on a 50 cycle system, the same reasoning applies. A spark frequency of 500 is desirable, and may be obtained by running a 10 stud rotor at 3000 RPM or one of 5 studs at 6000 RPM. In the case of the higher speed rotor of fewer studs, the quenching would of course be much improved, which is very desirable. Other combinations of speed and studs will suggest themselves. To be able to time the sparks properly, the stationary electrodes should be mounted on a yoke which may be turned through a few degrees about the shaft, and clamped at any desired position. It is adjusted till the spark gives the very

smoothest tone, and the radiation ammeter should show an increase at this point. (Note 4.)

Needless to say, perhaps, studs and electrodes should be flat and wide, and the gaps set at a very minimum, just sufficient to clear. Furthermore the edges of the studs and electrodes must be exactly parallel, or the sparks will occur at the closest point only and the advantage of the large cross section be lost. Inclosed rotary spark gaps are a luxury, but well worth while. Quenching is better and the

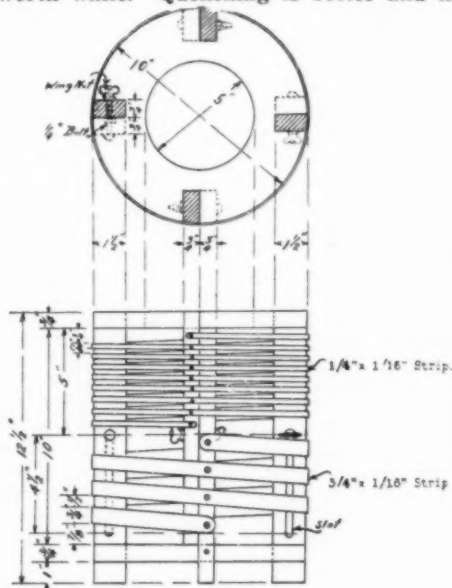


FIG. 5

objectionable noise and light from the spark is entirely overcome. There are so many medium priced rotary gaps on the market that it is hardly worth while to undertake building one, especially since the motor itself is the main item of cost, and would have to be purchased in any event.

### The Oscillation Transformer


This is at least one instrument that can be built and operated by most any amateur. There are in use two general types, the pancake or spiral, and the helical. The latter is probably the better transformer, because it produces a uniform and undistorted magnetic field. The main points to

remember in designing an oscillation transformer are to use large conductors, spaced sufficiently on a good insulating material, in such a manner that the distance or coupling between the two coils is variable.

The drawing shown herewith (Fig. 5) illustrates a very simple yet efficient oscillation transformer, good for 1 KW or more. The frame may be made of 'most any sort of wood, if it is thoroughly dry. There is little or no need of using more than two or three turns in the primary for 200 meter work, while six or eight turns in the secondary will usually be found sufficient. Dead turns are not to be desired, and if any exist after the set has been tuned up, they had better be cut off. Only one of the uprights in each pair need be slotted for the sliding coupling. The bolt in the others may be fixed solidly by countersinking a nut in flush. The metal strip used may be either copper or brass, and fastened to the frames by round head, nickel plated wood screws.
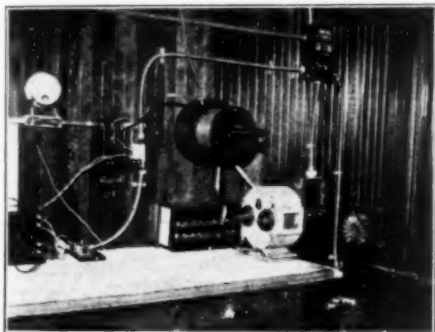
#### The Radiation Meter

This may be a hot-wire ammeter or an instrument of the thermo-couple type, of 0 to 5 amperes scale. However, it is



ARRANGEMENT OF APPARATUS


of hardly enough importance to justify much of an investment. Its chief value is in getting the highest indication when tuning the set up, and whether the reading represents actual amperes or not is a matter of small consequence. After that it is of very little use, and should be cut out of the circuit entirely or shunted with a single-pole single-throw knife switch.

#### The Key

Little need be said about this piece of equipment. Any easily adjusted smooth-working key, of 10 amperes capacity, is sufficient for a 1 KW installation; preferably one in which conducting strips are used to convey the current to the contacts, instead of depending upon the trunnions for that purpose. Fads in keys are rather to be lamented, as there is enough poor sending without them.
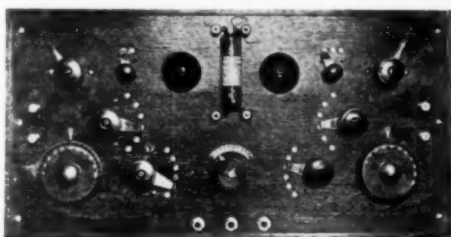
#### Arrangement of the Transmitter

Little need be said in this connection, as amateurs who pretend to be relayers in any sense of the word have a very good understanding of these pre-requisites. However, the accompanying photograph is presented as a good example of the compact arrangement of a transmitting set, which is necessary in order to have very short leads in the closed oscillatory circuit. All conductors of this circuit should be of comparatively large cross-section, to offer little resistance to the high frequency current. It will be noticed that




PANEL ARRANGEMENT OF REGENERATOR

the inclosed rotary is mounted with the pulley over the edge of the table, and the driving motor on the floor. This does away with excessive vibration, and gives more room on the table.
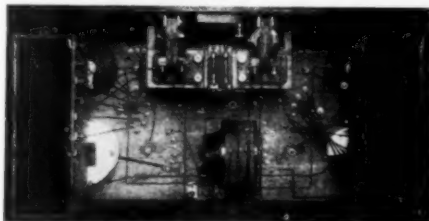
#### Tuning the Transmitter

For the accurate tuning of a set, a calibrated-by-standard wave meter is absolutely necessary. However, as this is an instrument that few amateurs possess, it is often necessary to resort to some approximate method. As most amateurs have some sort of receiving set, more or less sensitive, there is no reason why the receiving set itself should not be used as a wave meter. The amateur is perfectly familiar with tuning in 200 meter stations, and can adjust his circuits to the point where he gets some particularly sharp-tuned 200 meter station best. Then using his receiving set without changing any of the adjustments, as a wave meter, he may tune the transmitting set.



INTERIOR OF SHORT WAVE REGENERATOR

To tune the closed oscillatory circuit, the tuning coil or inductance of the receiving set should be brought into close

inductive relation to the primary of the oscillation transformer. The contacts of a small buzzer should be connected in place of the spark gap, in series with the condenser and primary. On operating the buzzer, this circuit will be excited by the spark at the contacts. The primary tap should then be varied on the oscillation transformer until the spark tunes in sharp at the 200 meter adjustment of the receiving set. In all probability one turn of inductance will be found sufficient, or possibly some fraction of a turn more or less.

The open circuit may be tuned independently of the closed circuit, by cutting the buzzer contacts in the ground lead, and with the tuning coil of the receiving set in close inductive relation to the secondary

meter, or to wind up an inductance and have it calibrated in connection with a variable condenser, borrowed from your receiving set for the time.

#### The Receiving Set

There are an infinite number of hook-up for receiving sets, and it would be folly to attempt to say which is the best. At any rate a short wave regenerative set, with two steps of amplification, is essential to an up-to-date reliable relay station. Whether the variometers or condensers are more effective is still very much a matter of opinion, and very wonderful work has been done on sets of both kinds.

The set described herein and shown in accompanying photographs and drawings has been giving splendid results on an in-

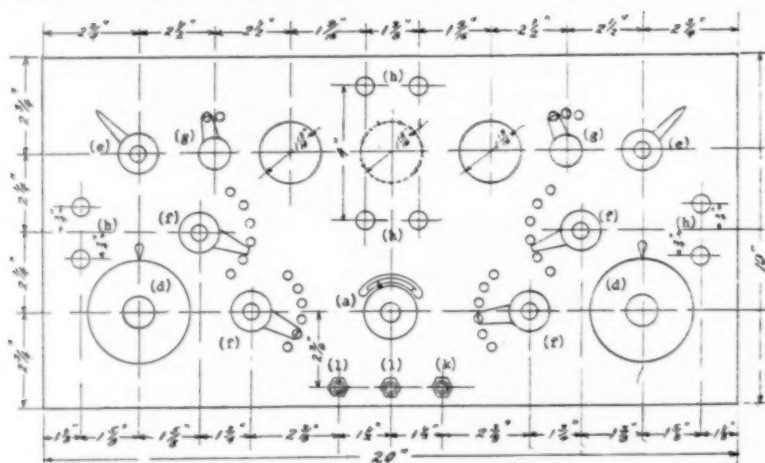


FIG 6

PANEL ARRANGEMENT

of the oscillation transformer and the aerial connected in its place at some point on the secondary. Then without changing the receiving set adjustments from the previous test, the buzzer should be operated and the secondary turns varied, until the spark tunes in sharp at 200 meters as before. Then on placing the primary and secondary in inductive relation, with comparatively loose coupling, and operating the set with the power on, a wave of very nearly 200 meters will be emitted.

Another method would be to simply use one turn in the primary and, operating the set, change the secondary turns, while comparatively closely coupled, until the apparent radiation was at a maximum. One trouble with this method is that the radiation might be so low, due to very little power being used, that a variation of several turns in the secondary might not have an appreciable effect on the indication, although the variation would alter the wave length considerably. The better idea would be to borrow a reliable wave

verted L indoor aerial of average height 15 feet from the ground. In fact, all efficient amateur stations within a thousand miles are heard. It is built up of standard parts bought from different dealers, as indicated in the list. The cabinet is built of mahogany, including the panel, and nicely finished, costing about \$5.50. The symmetrical arrangement of the parts gives the set a very pleasing appearance, and they had just as well be arranged that way as not. Since the tubular audions are no longer on the market, it is suggested that a third hole be put in as indicated by the dotted line, to accommodate a detector tube of the standard base type. The drawings and photos so clearly show the set, inside and out, that detail construction points hardly need be discussed. A full size drawing should be made up first and fastened to the panel, and all the center points transferred to the panel by punch marking. This saves scratching up the finish, as probably would occur in trying to lay out the arrangement (Fig. 6) directly on




the panel. Wiring up the set is the biggest job of all, and requires considerable patience, more than anything else. No. 14 bare copper wire was used in this set, and cut and bent to fit. It makes a very rigid job, and has a neat appearance. When using both amplifiers, the points on the filament switch are simply bridged by the lever arm, which is found to be entirely satisfactory. This set has a remarkable range of selectivity, and is recommended to all who are ambitious to build their own sets. It represents probably the best possible arrangement of the necessary apparatus, at the very minimum cost.

- (k) 1 No. 1421W. Federal Phone Jack.
- (l) 2 No. 1422W Federal Phone Jack.
- (m) 1 No. 1428W Federal Phone Plug.
- (n) 2 No. 226W Federal Amplifying Transformers.
- (o) 2 Marconi VT<sub>2</sub> Amplifying Tubes.
- (p) 2 Marconi Tube Sockets.
- (q) 2 Marconi 2 Megohm Grid Leaks.
- (r) 1 Audiotron Double-Filament Detector Tube.
- (s) 2 Kennedy 45 Volt B-Batteries.
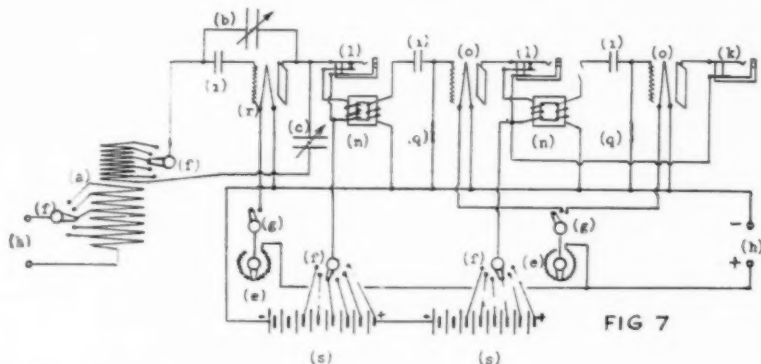
## Comments

Note 4. As a non-synchronous motor cannot be expected to hold in synchronism



The location of the component parts of the set is indicated in the panel layout (Fig. 6) and in the circuit diagram (Fig. 7) by the letters used in the following list:

- (a) 1 Sears-Roebuck SCR-54 Variotuner.
- (b) 1 23-Plate Illinois Variable Condenser, Style No. 1.
- (c) 1 43-Plate Illinois Variable Condenser, Style No. 1.
- (d) 2 Sears-Roebuck Moulded Dials, No. 6A-9349.
- (e) 2 No. 81 Remler Rheostats.
- (f) 4 No. 82BP Remler Control Switches.
- (g) 2 No. 84BP Remler Control Switches.
- (h) 8 Murdock Binding Posts.
- (i) 3 No. 358 Murdock Fixed Condensers.
- (j) 1 Pair No. 55 Murdock 3000 ohm Phones.

any great length of time, the choice of speed described would not prevent electrodes coming into opposition at times when the voltage is too low to jump.

Such speeds "are generally high enough to work the condenser up to the power rating of the transformer", but we must point out that that does not mean greater range, in spite of increased antenna current, because it is the power in *each wave train* that makes the noise at the other end. For that reason we recommend that attention be given methods that put the greatest power in each discharge, such as the use of high voltages and a low spark note, preferably synchronous so as to discharge the condenser at or near peak voltage.—*Editor*.

## Spark Reception on Honeycombs

**By Charles Kinyon**

**I**N the January QST I read with interest the article written by "A Novice" regarding the use of the Honey-Comb coils, also the articles written by Mr. Groves in the January and previous numbers. I noticed "A Novice" requested that other amateurs of less ability than Mr. Groves give their experiences

with the H. C. coils and in accordance with this request I will set down my experience with them and hope the article will be of some value to the craft in general.

I do not claim that I have been able to get any exceptional results and in fact not as good results as Mr Groves has reported and doubtless many other amateurs

Without in the least intimating that Mr. Kinyon's "grey matter is a little less grey", as "A Novice" put it, here is a more or less elementary exposition of tuning honeycombs which we know will be interesting to our readers. Mr. Kinyon confines himself pretty well to the reception of damped signals by the zero-beat method and altho most of us incline to the belief that the true field of the honeycombs is above 600 meters, Mr. Kinyon's article shows what can be accomplished with them in amateur work and, what is important, tells how to do it.—Editor.

have done better also, but I do believe that many amateurs are getting very little out of the H. C. coils in comparison to what could be gotten out of them by careful adjustment along more nearly correct lines. I have heard considerable criticism of the Honey-Comb coils from amateurs in this vicinity and I do not think it is justified by the action of the coils when properly handled. Of course the coils have their defects and in time will doubtless be improved upon but at present I do not know of any better receiving equipment for long waves or for a universal equipment to receive all waves from 150 meters to the highest around 20,000 to 25,000 meters, damped and undamped.

According to all the information I can get Salt Lake City is about the worst place in the world to get radio signals into and out of. It is surrounded on all sides by high mountains and in addition the soil is very sandy and dry a great part of the year. Before the war I had a loose coupler set in Kansas City and was getting pretty fair results with it but when I unpacked it here and set it up I could hardly get the Pacific Coast 600 meter stations on it and even after making several improvements in it results were greatly under what I thought they should be as compared with work in Kansas City. I then got the Honey-Comb coils and from the first got much better results with them than with the loose coupler.

In order that others may have some method of comparing their results with what I have been getting I will give some idea of the range I can receive from and if any one will remember that a station on the coasts or in the middle west should be able to receive from  $1\frac{1}{2}$  times to 2 times the distance with similar equipment I believe they can readily determine if they are getting as good or better results.


Amateur stations are received from the following points fairly regularly: Portland, Oregon, and south along the California coast to San Diego, Calif.; eastward to Roswell, N. M., and Douglas, Ariz., Anthony, Kans., Wichita, Topeka, Omaha, a station or two in Dakota, several stations in Montana. On commercial waves I can get coast stations on 600 meters with no aerial or ground. I frequently hear boats reporting their position 1,500 to 2,000 miles south and west of San Francisco. Undamped waves are received from Alaska, Hawaiian Islands and occasionally Guam and the Philippine Islands, Mexico

City, NBA Panama, eastern coast stations, NSS, WII, WSO, NDD, NAA and at times I have heard POZ, LCM, and MUU but these last are uncertain and are probably only received during favorable conditions. I have a two-step audio-frequency amplifier in service but find that one bulb will bring in any signals that can be read on the amplifiers provided there is no noise about the house to drown out the weak signals.

I am willing to admit that if anyone will be content with a wave length range of 200 to 600 meters or so, the regenerative set of the so-called Paragon type may be superior from the standpoint of quick adjustment, probably has a greater distance range also; however, as far as I have been able to personally compare the Honey-Comb coils with regenerative sets in this territory I seem to be able to hear amateurs as far away with the Honey-Comb coils as the other fellows do with the regenerative sets and also get a tone which I like better.

Most amateurs, I believe, are never satisfied with their sets regardless of what type, kind and amount of equipment they may have. This is probably due to three principal causes; first, the type and size of aerial is governed more by the room available in which to string it and by the supports it is possible to use than by the amateur's actual beliefs of what would be the best type and arrangement from an operating standpoint; next, the average amateur when starting to build his first set knows very little about what kind of apparatus is really best and must depend very largely on reading advertisements and generally buys at least some articles which he later finds to be greatly out-classed and later when he goes to construct a better set the third item, lack of money to buy what he then knows to be best, induces him to re-use certain parts of the old equipment which he hopes will answer the purpose but which he knows will not perform as well as other parts would do. My own set I know suffers to a greater or less extent from these causes. My aerial is not at all what I would consider ideal, either as to shape or location. The best arrangement I could get out of it seemed to be as follows: I have a pole 55 feet high set at one side of the house and the other end of the aerial is supported by a combination electric light and telephone pole which is about 30 feet high but the ground where the pole is set is

about 10 feet higher than the ground where the house pole is set. The aerial itself is of the inverted L type with the flat-top part consisting of 4 No. 14 copper wires spaced 2 feet apart about 60 feet long, with the free end about 35 feet above ground, and the end from which the lead-in comes off is about 50 feet from the ground. The lead-in consists of 4 No. 14 copper wires tied together and fanned out to meet the flat top portion. The ground is connected to the city water pipes and a pipe driven into the ground

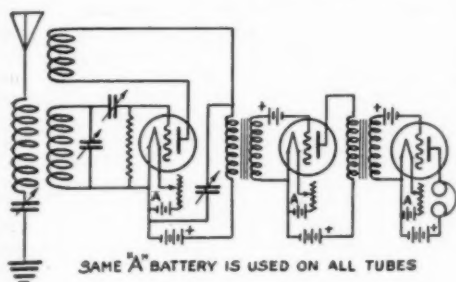

but due to the sandy and dry condition of the ground this proved unsatisfactory for short wavelengths, long wavelengths coming in satisfactorily. This condition was eliminated by burying a single strand of No. 14 copper wire about 4 inches under ground and directly under the aerial. 200 meters then came in satisfactorily but of course more than this would be necessary to fit the aerial for efficient sending.

The receiving set consists of an assortment of H. C. coils from L-25 to L-1500, a Clapp-Eastham variable condenser of .0007 m. f. capacity in the aerial circuit, with a switch to change from series to parallel. (One of the DeForest vernier .0015 m. f. would be preferable and for larger aeriels probably the loading condenser of .003 m. f. could be used to advantage.)

The secondary circuit uses a DeForest grid condenser, capacity unknown but probably close to .0005 m.f.; shunt condenser is a Murdock capacity nearly .001 m. f. but this condenser especially should be of the vernier type as it requires very accurate adjustment to obtain good results on short waves. I am using an old style DeForest tubular bulb purchased before the war as a detector and find it the best bulb I have tried although I have used the Marconi Class I and the Audiotron bulbs successfully. The tickler circuit besides the H. C. coil contains the "B" battery and a telephone jack arranged so that the telephone receivers may be plugged into the detector circuit when desired and when pulled out the jack contacts pick up the primary winding of the Fed-

eral amplifying transformer. At present I am using a variable condenser of about .0007 m. f. capacity around the "B" battery and the telephones or amplifying transformer windings but a condenser having a capacity of .004 or .005 m. f. would be much better. On account of the small condenser in use in this circuit I find it necessary to introduce a small loading coil in series with the H. C. coil in the tickler to enable me to get a satisfactory plate adjustment on the short waves. With a suitable plate condenser I think the circuit would be improved by leaving this loading coil out. I am using a grid leak made of lead pencil marks between binding posts on a piece of fiber. I prefer this leak to the Marconi on account of the ease with which the resistance may be varied to suit conditions.

The first step of the audio-frequency amplifiers uses a Marconi Class II tube connected as usual to the secondary of the transformer with a "C" battery of 1½ volts connected negative side to the grid. No condenser or grid leak is necessary in this circuit. A potentiometer to vary this "C" battery voltage would probably increase the amplification but as yet I have not installed it. The plate circuit uses about 100 volts "B" battery and is hooked up through a telephone jack to enable the telephone receivers or primary of the second Federal transformer to be inserted at will.

The second step is hooked up like the first except that a W. E. Co. VT-2 tube is used and a "C" battery of between 8 and 9 volts. The same "B" battery is used on this step as on the first and is also run through a telephone jack to enable the telephone receivers to be used. I am using the Brandes Navy Type phones although I would prefer the Baldwins if available. The sketch shows the circuit used.

I have been using a method of adjusting, particularly on short waves (200 to 900 or 1000 meters,) which I have never seen explained in print and which seems to me to give good results from the standpoint of selectivity and loudness of signals, also retaining very nearly the natural tone of the spark stations although the detector tube is in full oscillation. When this adjustment is obtained the oscillations in the tube are exactly the same frequency as those in the aerial circuit or of the signal to be received (or if there is some difference in frequency it is so small that the best notes which would be formed by this difference are of such a low frequency as to be inaudible.) For simplicity's sake and also because I know a great many of you will challenge the accuracy of the above statement I will refer to the adjustment as the location of a

(Continued on page 25)

## Radio Market News Service

Beginning April 15, 1921, the radio market news service of the U. S. Bureau of Markets was expanded to include the sending of agricultural market reports by wireless from Washington, D. C., Bellefonte, Pa., St. Louis and Omaha, at stated periods each business day. This increased radio market news service is made possible by the co-operation of the U. S. Post Office Department which, through its Air Mail Radio Service, has offered to send certain agricultural reports to the Bureau of Markets at specified hours from its wireless stations at the cities named.

On December 15, 1920, the Bureau inaugurated an experimental wireless market news service at Washington for the purpose of determining the practicability of sending daily agricultural market reports to farmers by wireless, as previously announced in QST. Reports of prices and conditions of leading fruits and vegetables, live stock and meats, grain, hay and feed, at important national markets were prepared and at 5 p.m. each day were sent by wireless from the U. S. Bureau of Standards' Washington radio station to farmers and other agricultural interests within a 200-mile radius of Washington. The experiment proved successful and the offer of the Post Office Department to send similar reports from some of its wireless stations was gladly accepted. The sending of reports from Washington which had formerly been handled by the Bureau of Standards was transferred to the Post Office Department on April 5.

The schedule for sending reports is as follows: From Omaha a complete report of the Omaha live-stock market will be sent at 11:15 a.m. each day (Central standard time), and at 11:45 a.m. a complete report on the Kansas City live-stock market. At 2:15 p.m. a grain and potato report, giving prices and conditions at the Chicago, Minneapolis, Kansas City and Winnipeg grain markets, and similar information at the Chicago and other potato markets, will be dispatched. At 5 p.m. a daily "Radio Marketgram" will be sent, covering national market conditions on live stock, fruits and vegetables, grain, hay, feed and seed. The reports to be sent from St. Louis are a National Stock Yards live-stock market report at 11 a.m. (Central standard time), a Chicago live-stock market report at 11:30 a.m., a grain and potato report at 2 p.m., and the Radio Marketgram at 7 p.m. From the Washington and Bellefonte stations will be dispatched a Radio Marketgram giving a general daily summary of eastern market prices on live stock and meats, fruits and vegetables, grain, hay, feed and seed, at

5 p.m. and 7 p.m. respectively, (Eastern standard time). The Weather Reports from the local office of the U. S. Weather Bureau will be appended to the forenoon live-stock report. Any changes in the form or time of reports will be announced in advance by radio at the time of sending regular reports.

These reports are intended to be received by amateur radio operators within the territory covered by the 300-mile radius of each of the four wireless stations named. There are some 2,500 licensed wireless operators in the area covered, and the Bureau of Markets hopes that as many of these operators as can conveniently do so will receive the reports and see that they are placed in the hands of farmers and other agricultural interests as soon as possible after the information is received. The morning and early afternoon reports will be sufficiently brief to be transmitted in 10 or 15 minutes each, and the Radio Marketgram will require about 20 minutes. Each operator indicating a desire to receive and distribute the market reports will be supplied with blank forms so that it will be necessary for him simply to fill in (in longhand) the prices, and the brief comments on general market conditions. With one exception, the reports will be transmitted on a wave length of 800 meters at a rate of 15 words per minute. The Washington station will use an 1800 meter wave length. The reports will be opened by the general call signal to all stations (QST) and the call signals of the Post Office Department: WWX for Washington, WWQ for Bellefonte, KDEL for St. Louis and KDEF for Omaha.

Suggested methods of distributing the reports are: Furnish them at once to shippers' associations, county agents, States bureaus of markets, farm bureaus, and other agricultural organizations; deliver them to local newspapers for publication; post them on the bulletin board in the Post Office or elsewhere; and file them with the local telephone exchange so that farmers can get the information by asking the telephone operator for it. Suggestions for improvement of the service will be welcomed. It is desired that all A.R.R.L. members interested in receiving or planning to receive the reports by radio communicate with the U. S. Bureau of Markets.

---

**SAVE YOUR MONEY!**  
**CHICAGO CONVENTION**  
**AUG. 30—SEPT. 3**

---



## A Cup For Summer Achievement

**M**R. Seymour Wemyss Smith of "The Hartford Courant", long a member of the A.R.R.L. and likewise of the Radio Club of Hartford and ardently interested in amateur activity, has presented the A.R.R.L. with the handsome loving cup shown in our illustration, to be awarded by the A.R.R.L. to the amateur performing the most outstanding feat in the interest of Citizen Radio, under rules to be drawn up by us.

Mr. S. Kruse has accepted our invitation to become the chairman of a committee to award the cup. He is now forming his crew, to consist of a well-known and representative amateur from each inspection district, he himself representing the Third. The tentative formation of the committee is as follows: Irving Vermilya, 1ZE; C. J. Goette, 2JU; S. Kruse (Chairman), 3ABI; E. H. Merritt, 4YA; J. M. Clayton, 5ZL; A. E. Bessey, 6ZK; Royal Mumford, 7ZJ; Rev. A. J. Manning, 8ZG; R. H. G. Mathews, 9ZN. It has been decided to make the award on November last of this year for the most outstanding accomplishment between July 1st and November 1st. The summer period was chosen purposely, because an achievement made then will be an accomplishment indeed.

The cup stands 13¼ inches high, is the same in overall width, and with a bowl 9¼ inches diameter. Across the face of it is engraved "National Trophy—American Radio Relay League—In Recognition of Outstanding Achievement in the Interest of Citizen Wireless". On the reverse will be engraved the name of the winner and the circumstances under which the award is made. It is a prize well worth having, for the honor that will go with its possession.

The readers of QST are requested to submit to the Chairman of the Committee, Mr. S. Kruse, 2637 Garfield St., N. W., Washington, D. C., any distinctly meritorious work in the advancement or interest of Amateur Radio that should come to their notice. Any type of work whatever will be considered, whether a feat of operating, construction, design, invention, organization, noteworthy publication, or what not. The achievement must be made between July 1st and November 1st, and all suggestions should be in by November 7th.

Who's going to get it? We'd be mighty proud to have it sitting in our static room, proof to the world that we did something noteworthy in the annals of Amateur Radio. The coming of the contest right in mid-summer means that you'll have to keep on

the job, fellows. Your neighbor will have the edge on you if you don't. We are an organization of Doers and it's going to be no easy matter for the judges to pick a winner, because we're all accustomed, anyway, to work for the advancement of Citizen Wireless. But somebody is going to do something distinctive—something "outstanding". Somebody is going to relay 1100 messages per month right thru summer, or is going to work Japan on a detector tube, or invent something, or put Citizen Wireless to some new use in the



service of the community. We do things that are conspicuous right along, but there's only one cup and the fellow whose accomplishment sticks up head and shoulders above the gang is going to get it, and with it the recognition of service to the game.

So don't dare to give up the set—stick right on the job this summer!

### SPARK RECEPTION ON HONEYCOMBS

(Continued from page 23)

quiet spot between two noisy spots and leave the proof or discrediting of the above theory to some of you who have a more elaborate testing equipment than I have at my disposal. I presume that this method is practically the same thing that Mr. Groves described in QST some time ago but as I understood the article it applied principally to the longer waves and I believe that somehow he missed the corresponding results that could be obtained on the short waves.

(Continued on page 32)

## First National A.R.R.L. Convention

**T**HE First National A.R.R.L. Convention will be held in Chicago August 30th to September 3rd and will be the biggest combined radio show and general good time ever staged. The programs of the various meetings include the very best speakers from all over the country and it is believed that this program is so varied that it will be interesting to everyone. The Convention headquarters will be at the beautiful Edgewater Beach Hotel, situated on the shore of Lake Michigan. This hotel is of the very latest summer resort type and has as its attractions tennis courts, small golf links, swimming and bathing facilities, dancing, private bus service to the downtown district, and a hydroaeroplane taxi service. Registration will be done at this hotel and the offices of the Convention managers will be located there. The Banquet to be held on the final evening of the Convention will be held on the famous beach walk of the Edgewater Beach Hotel and speeches will be delivered from a gondola on the lake by means of loud speakers.

The general meetings, special meetings and manufacturers' exhibit and show will be staged at the Chicago Broadway Armory. This structure is over a block long and a half block wide and is beautifully decorated. The exhibits which will comprise booths furnished by radio manufacturers and dealers all over the country as well as exhibits of the latest Army and Navy equipment will line the walls of this enormous hall. Chair accommodations for over 2,000 are provided in the center of this hall which is provided with a speaker's platform equipped with modern sounding boards. All the big meetings and lectures will be held here, which is a decided advantage to both the Convention delegates and exhibitors as the meetings and exhibits are thus placed close together.

In connection with the meeting and exhibit hall is the well known Butterfly Room which is fitted up as a dance hall and which will be used for executive and traffic department meetings in the daytime. Dancing will be provided in the evening with music furnished by a special orchestra of radio men.

Refreshments will be served in the large lobby adjoining both the exhibit hall and the Butterfly Room.

These details serve to give a very meager idea of the scale on which this biggest of radio conventions is being staged. Every effort is being made to bring together the most notable collection of radio men ever gathered under one roof, and since "all

work and no play makes Jack a dull boy" special amusement is being provided by the various trips throughout the city as well as by the cabaret and banquet nights.

The cabaret night which will be held on the fourth evening of the convention will be devoted entirely to a general good time at which we will "take over" one of Chicago's best dinner and dancing places. Every attempt is being made to take good care of the wives and mothers who may accompany our delegates and special trips are being organized to Marshall Field's and several other of the large department stores, which should prove of interest to these fair visitors. For those who come without OW's, girls will be provided for the banquet. This may sound like an impossibility but we can guarantee at least 500 unattached young ladies who are willing to be talked to about radio.

Special rates are being arranged in connection with the various railroads whereby tickets will be certified at Chicago by the Central Division Manager which will allow of a considerable reduction on the return fare.

Preparations are being made to take care of an attendance of over 2,000 radio men and in addition an attendance of thousands of other interested Chicagoans is expected. Reservations for the Banquet and meetings, which will total \$5.00 per person, may be made with Mr. N. C. Bos, Reservation Manager, 118 N. La Salle St., Chicago, Ill. In addition to accepting reservations for attendance at the Convention, Mr. Bos will be very glad to supply inquirers with full information regarding hotel rates at the various Chicago hotels and will arrange hotel rooms in advance for any who wish such reservations made. Every effort is being made to get these reservations arranged early. The general tendency, however, is against early reservation because of fear that attendance may not be possible. In this connection it should be stated emphatically that any such reservations made now may be cancelled without question at any time up to and including the day before the Convention. Therefore please do not withhold your reservation because of any doubt as the possibility of your attendance.

At the manufacturers' exhibit, the spaces have been divided to allow booths approximately 14 feet square. The available space aside from that allowed for the meetings has been divided into 31 booths, 6 of which will probably be given over to Army and Navy displays and executive quarters. This leaves but 25 open to the first applicants. The Chief Show Director

advises that a number of unsolicited requests for space have already been received. Manufacturers and dealers desirous of obtaining space can obtain a chart of the booths, rates and contracts from Mr. N. E. Wunderlich, Show Director, First National A.R.R.L. Convention and Show, 4533 N. Sawyer Ave., Chicago, Ill. General information regarding the entire feature of the Convention, show, programs, or reservations can be obtained from the Central Division Manager, Mr. R. H. G. Mathews, 6433 Ravenswood Ave., Chicago, Ill.

A skeleton outline of the tentative program follows:

#### August 30th.

Day devoted to meeting arriving delegates, arranging reservations, etc.

7:30 p.m. Business and General Organization Meeting.

#### August 31st

10:30 a.m. Educational Lectures.

1:30 p.m. Central Division Organization Meeting.

3:30 p.m. General Business Meeting for discussion of interference control, time division, traffic regulations, observance of laws, legislative matters, etc.

7:30 p.m. Technical Meeting on spark apparatus.

#### September 1st.

10:30 a.m. Educational Lectures.

1:30 p.m. General Club Organization Meeting.

3:30 p.m. General A.R.R.L. Operating Department Meeting, to take action on matters discussed in general business meeting of preceding day.

7:30 p.m. Technical Meeting on C.W. apparatus.

#### September 2nd.

10:30 a.m. Educational Lectures.

1:00 p.m. Indoor Baseball Game between A.R.R.L. Board of Direction and Chicago Executive Council. Each player will have his call letters printed in large letters on a white placard fastened to his back.

3:00 p.m. A.R.R.L. Board of Direction Meeting.

8:00 p.m. Cabaret—not a meeting but a get-together, free of speeches.

#### September 3d.

10:30 a.m. Hamfest. All the DX men available will describe their stations, etc.

2:00 p.m. Stunt Party, with novel and interesting tests for which valuable prizes will be given.

8:00 p.m. Banquet and Dance at Edgewater Beach Hotel on the famous Beach Walk.

## A Sure-Fire C.W. Circuit

By E. W. Whittier, 1DH\*

**A**FTER trying several C.W. circuits with poor or indifferent results, I happened to run across the hookup shown below, for which credit is due the General Electric Co. The beauty of this circuit is that anyone who can wire up a set correctly can get the maximum output of his tubes with almost no trouble at all. The constants given below have been found to be correct for two UV-202 tubes on several different grounds, aërials, etc.

This article deals mostly with the UV-202 tubes. Since they can be overloaded so easily and safely, we may as well get all we can out of them. The source of plate supply used is an Acme 200 watt C.W. transformer, the output being rectified by an electrolytic rectifier. The output voltage after rectification is between 550-600 V. This means that a high resistance grid leak must be used to keep the grid negative enough to prevent excessive plate current. If the tubes are run on normal plate voltage (350 V.) the grid leak may

be omitted. Using from 550 to 600 volts is liable to cause fireworks inside the stem or seal of the tube, and a safety gap connected from the grid of one of the tubes to the filament is recommended. This gap should be about .015 inch (1/64 inch).

The writer runs his two tubes on this high voltage and uses about 150 M.A. plate current. The power put into the antenna circuit is 30 watts under these conditions. The efficiency of the tubes at this overload is about 33%. The antenna current will vary with the conditions of resistance in the antenna and ground system. Using a 14 ohm antenna system 1.5 amperes can be obtained. With a good counterpoise the resistance may be made as low as 5 or 6 ohms, giving an antenna current of 2.2 to 2.5 amperes with the same plate voltage and current.

The circuit diagram and its accompanying legend show the constants of the various pieces of apparatus and exactly how to connect them up to get results.

The only meter that is absolutely needed is the antenna H.W.A. but it is highly

\*Radio Engineer, Atlantic Radio Co.


desirable to have a filament voltmeter and a plate milliammeter.

The only real critical adjustment on the whole set is the value of  $C_4$ . If the value of this condenser is not right, the grids may be at such a low negative potential that the plate current may become very great. The value of  $C_4$  is different for each change of  $T_1$ .

In setting up this circuit, or any other for that matter, the use of as short connecting wires as can be used is always to be recommended. The condensers  $C_2$ ,  $C_3$ ,

sq. in. per 100 M.A. is about right. When these plates are working properly there are little scintillating sparks running all over the immersed portion. The best way to make up the solution for these rectifiers is to dissolve as much 20 Mule Team Borax as possible in cold distilled water. Allow the surplus borax to settle and fill the tumblers containing the lead and aluminum strips with the clean liquid. As the solution evaporates add only distilled water.

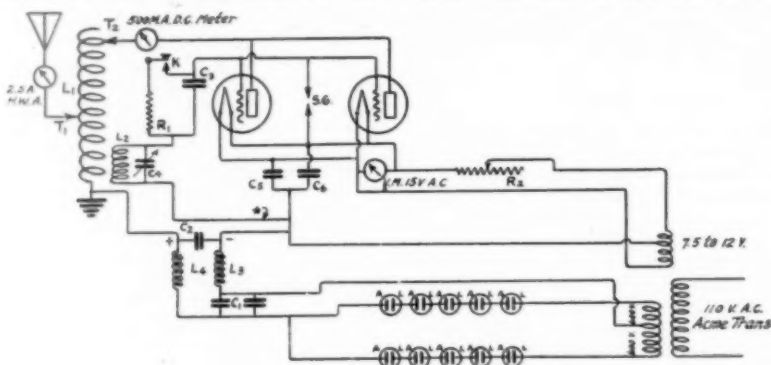It will be noticed that an A.C. voltmeter was used to tell the proper filament



$L_1$ —Antenna inductance 25 turns of large wire or edgewise wound copper ribbon about 5 to 6 inches in dia. Well insulated.

$L_2$ —Grid tickler coil 15 turns bell wire on 3 to 4 inch dia. tube and placed in bottom of  $L_1$ . Wind in the opposite direction to  $L_1$ .

$L_3$ ,  $L_4$ — $1\frac{1}{2}$  henry iron core chokes, 500 M.A. capacity. 150 M.A. will do.

$C_1$ ,  $C_2$ —21-AA Western Elec. Co. 1 mfd. condensers.

$C_3$ —.0005 to .005 mica or air condenser, fixed.

$C_4$ —.0005 to .001 air condenser (variable)

$C_5$ ,  $C_6$ —.001 fixed paper condensers.

$R_1$ —Grid leak resistance 10,000 to 15,000 ohms.

$R_2$ —Rheostat capable of carrying 4.7 amperes. (The rheostat may be done

away with if the voltage of the transformer is just 7.5 V. when the tubes are lighted. When modulating, the filaments need to be a trifle brighter than for telegraphy.

$T_1$ —Tap to vary wave length of antenna circuit.

$T_2$ —Tap to vary power input to plates of tubes (coupling).

V.M.—0-10 or 0-15 voltmeter.

S.G.—Safety gap.

K—Key.

\*Secondary of modulation transformer may be inserted at this point. The secondary of this transformer must be shunted by a .001 condenser or short circuited when using straight C.W. The value of  $C_4$  then will be different when modulating than when using C.W.

and  $C_6$  should be right in the set and not near the transformer or rectifier. These are high frequency by-pass condensers and should be connected by short leads, and be near the oscillatory circuit.

In setting up the electrolytic rectifier, don't use large plates thinking you will get more voltage or current. If the plates are too large or too small the voltage and the completeness of rectification is affected. The author uses aluminum strips  $\frac{1}{4}$ " wide and 3" long and  $\frac{1}{32}$ " thick; these pass 200 M.A. easily. If the plates are wider they should not be immersed so far into the borax solution. A total area of  $\frac{3}{4}$

brilliancy. This method gives several times as great filament life as the use of an ammeter for this purpose.

This same circuit may be used on UV-203 tubes (50 watt) with slight changes in the constants. The grid leak at 750 volts may be omitted. With 1000 V. on the plates of two UV-203 tubes the grid leak is about 250 ohms; for one tube twice that. The condensers on the filter circuit will have to be able to stand 2000 V. at least. Ten tumblers on each side of the 1500 V. secondary winding of the plate voltage transformer are needed.

The author has been using a small set



as described (two UV-202's) and has had no trouble working over 800 miles on straight C.W. With voice modulation about 100 miles is the limit when there is no QRM. I wish to thank those who have so kindly reported the signals from 1DH and stand willing to help those who may be in need of any dope on hooking up a C.W. Set.

(Editor's Note—Circuit students will recognize this hook-up as the favorite diagram of the English engineers in their war-time sets. It appears frequently in Stanley's "Valves and Valve Apparatus".

As to the results it gives, it is far and away the best short wave oscillator we have ever tried. Since the receipt of Mr.

Whittier's paper at the QST office we have tried this circuit at three different stations, one a phone station using two 50-watt tubes in a Colpitts circuit, one a 5-watt set using the Hartley circuit, and the third an experimental circuit using three E tubes. In every case surprising improvement resulted. These three cases are not enough from which to make a general rule but nevertheless we will state that the new circuit gave outputs that averaged more than twice the watts power given by the original circuits, accompanied by the ability to reduce wave length an average of 100 meters in each of the three sets. The 5-watt set used a UV-202 and with the new circuit, using 850 volts a.c. on the plate, 15 watts were put into an antenna of 500 mmfds. capacity on 190 meters! It works—try it.)

## QRX For a New O.W.

By Irving Vermilya, 1ZE

"SQUEEK, scratch, pick, putter, pfoof, spiff awawk—"

"What the hexx is this," thot old 1HAA, as he tuned around trying to get a line on its decrement. "Something new moved into this little old burg of Marion, I'll bet, or else that sixty cycle stuff is running loose up in some tree top."

All quiet, not a peep or scratch, and VN breathed easier. But we speak too soon, for suddenly the air was again rent asunder, worse than ever, with the darnedest scratching and sputtering and up-and-down shimmy tones ever heard. "Sure enough, that's a Ford spark coil or I'm a boob," said VN.

Mad clear thru, he threw the juice on his old stone-crusher and with the bug key gave a quick snappy "QRA?" and listened. Not a scratch to be heard. The usual 2's, 3's and 8's were pounding in but not a sound from the QRM-er. "Just as I thought," said Vermilya; "that bird is sitting there waiting for me to get busy with someone out in Ohio before he murders me with his coil." But after a long period of silence for both the big DX station and the new-born "friend," VN looked in the direction of his message hook and realized there was lots of work to be done. So he started in to clear the hook as quickly as possible.

No more was heard from the new-comer so the night progressed well for DX work. The next day, try as he might, Van could not forget that new noise. Marion is so far from civilization that one coil is a big matter, especially where hundreds of messages are handled each month and a good clear path is essential. Well did 1HAA realize that he already had his hands full

with the continual QRM he gets from the high power station not a mile away from his shack radiating four hundred and fifty amperes. Eventually he got to thinking



Miss Eunice Randall.

that perhaps he had imagined a lot of it, but was certain whoever or whatever it was had a pretty broad band of waves.

Next night as he sat in at his tuner, long before touching his key, sure enough that

was the same old boy at it again. "Scratch, scratch, scratch," on and on it went. "Dog-gone it," said VN, "someone's either going to get a license now or pipe down or I'm going to find the reason why. I'll just take a listen to this and see if old Killjoy will hang himself if I give him plenty of rope." On went the scratch—"Sputt, stitch, futz, buut, fuerer, thup, wee, zipp." "Good

to realize that this little lady probably wanted an answer of some sort, so he put the switch down, and again very slowly: "I am married." The answer came back a-flying this time: that is, the reply was quick even tho the sending was not: "How we suffer, but my heart is not in my hand; I will see you tomorrow night just the same."

"OK have your own way."

Thus ended the conversation and no further scratching was heard. But upset! Say, VN was purely and simply licked. Here he was going to "make" someone get a license and the first thing he knew a little girl had come along and he had passed out like a little boy sent to bed without his supper. "Darn her anyway. Gee she's fresh, telling me she is going to see me tomorrow night. I'll be darned if she will. I'm going out to a dance tomorrow night and I'll lock this old coop up tighter than a drum."



The Y.L. at 1XE.

night," thot VN, what are we coming to?"

Finally all died down again and once more Van put the juice on the old sink gap, and then just ... — ... — and a listen. "That ought to do for bait," thought he. Much to his surprise he heard a very crippled call: "1HAA 1HAA ER."

"There now, for the love of mud, we do know that he wants to call himself 'ER' ". So back he went after Mr. ER. He realized it would be useless to give this newcomer a show of speed for surely it would not be appreciated, so he spelled out as slowly as ever he sent, "Who is ER please."

A long silence, and then, soft and sweet this time, just the simple word "What?" So again: "Who are you please?" "There, that ought to fetch him," Van thought. And sure enough, like a long slow funeral procession came the following:

"This is a little girl in Mattapoisett and I will see you tomorrow night."

"Wow, said Vermilya to himself. "This is the little innocent chick I've been wanting to hang or kill or something. Wonder if she knows I'm married." A million other thoughts ran thru his mind but he began

Not daring to mention his experience on the air to a soul, next night VN went off to a dance in a neighboring town. Many of his friends were there; all seemed quiet and everthing was going along in fine shape; the music was good and so were the dancers. Now in these small country places strangers are easily spotted, and it wasn't long before Van noticed two very tall people enter the hall—a fellow and a girl, looking much like brother and sister. But as they stopped to speak to Brad Cleveland, an old friend of Van's, he decided they belonged there and that he had just never noticed them before. A little while later VN was sitting alongside of Brad and in the course of the conversation he asked Brad who that tall couple was that had come in a short while before. You could have knocked him over with a feather when he was told that their name was Randall and that the girl was in the wireless business somewhere up Boston way. "Holy smoke," thot VN, "I'll bet my last nickel that that's the one I had on the air!" Here she came, making foot-prints over their way and up jumped Brad saying "Vermilya, I want you to meet Miss Eunice Randall. She is deeply interested in wireless and works up in the American Radio & Research Laboratories at Medford Hill-side." VN tried his best to say something but the best he could do was a sound that resembled "MO." "No," said Miss Randall, "you won't need your direction finder now; you can put it away. I have found you and met you as I promised I would do last night. I've heard about enough about 1HAA without knowing him, especially when you consider that my home is in Mattapoisett, only about five miles from your station. While I don't live there dur-

ing the week, I manage to get down week-ends once in a while. I am working up in the Amrad place as drafft lady and now, to be truthful with you, I want to learn the code and theory of radio so I can be 'one of the boys'."

"Look here, Miss Randall, if you are in earnest and really want to learn the code and all about radio from one end to the other, I will help you all I can. But if you just want an adventure you're going to be plain Outta Luck. Now which is it?"

"I tell you I am really interested and if you had seen me shinning up a tree putting my aerial in place you would believe me a lady of my word."

"Very well," said VN, "I'll give you a note to a good friend of mine who runs a radio school in Boston, where you can learn in a good thoro manner all the ins and outs of radio, as well as code. You're going to have a mighty hard struggle, I can warn you, and being a girl your trials will be many and hard, but I want you to know I admire your grit and nerve and I can see right now that you are going to succeed. When you come out, bring a first grade commercial license with you and then if you're not too busy let me know how you liked it all and whether you think that after getting that far and being thoroly bitten by the little radio bug you will ever waste any more time thinking of the things that most other girls think about. You're one in a hundred for the pick you are taking and I want to wish you success. But meanwhile please don't open up on that squeak box again until you can handle at least fifteen words

per minute. By that time you will be an honest dyed-in-the-wool O. W., and believe me if you make good I'll see that you have a station that will put Mattapoissett on the map."

"Gosh," thot Vn, "she isn't so bad after all. In fact I'll have to take my hat off to her. She has the proper spirit for a real honest to goodness shemale radio bug. Other districts have had the honor of boasting an O.W. long enough, by heck; we're going to have one of our own up here now."

So watch your step, boys, for already she is on the job at 1XE every night they have the radiophone concerts—yes, she's the assistant operator at 1XE. And on three other nights a week she's plugging away at code at a Boston school where reports say she is already doing better than some of the fellows that have been there six weeks longer than she. And it won't be long now before you'll hear another real DX station on the air and the operator is going to be Miss Eunice Randall.

As a word of warning, don't try to flirt with her, for she hasn't time and besides, as she has already asserted, she "does not carry her heart in her hand." Treat her as one of us, a sister operator. If you can lend her encouragement by all means do so as she's the jolliest girl you ever want to meet or talk with over the air. But don't expect to find a "little" girl, for Miss Randall is over six feet tall.

Three cheers for the new First District O.W.!

## All Set to Perforate QRN!

### A Miasummer Party to which Everyone is Invited

**W**E are off, and we are loaded for bear and lordhelpus if we don't knock Old Man Static full of holes in our static-puncturing contest on the night of July 19th.

This was announced in June QST, page 21. Come on and unpack your receivers, you fellows who have closed up for the summer; dust 'em off and give our A.R.R.L. a lift. We need you, OM. We need everyone if we are to be successful in the undertaking. This is the first time such a contest has been attempted in mid-summer, and we want to prove that relaying can be done with C.W. thru QRN, and we are calling upon you men who can copy thru static. There will be a hole in static all right and C.W. will puncture some more holes—copy thru them. The scheme is to have pairs of transmitters broadcast messages as per the following schedule on

July 19th. Each pair of transmitters will consist of the most powerful C.W. and spark in each division of the A.R.R.L. Each transmitter will broadcast a different message at ten words per minute and each message will be sent twice.



It is a well known fact that it is rather hard to pick up the C.W. signals, so on July 16th each of the transmitters will QRL at exactly the same time and exactly the same wave as shown on the schedule. This will give all of you a chance to tune

for the different transmitters and make notes of the settings of your receiving equipment. In this way it will not be necessary for you to "hunt" for the transmitters on July 19th, because you can be reasonably sure of finding the stations on the same adjustments. There will be 38 transmitters, 18 C.W. and 20 spark, scattered all over the United States and Canada, and if you have any kind of receiver at all and can copy thru QRN, you ought to make some good records. (Undoubtedly there will be many stations heard over great distances where they have not been heard before. We will have authentic proof if new records are made and due credit will be given the receiving operator for his part in copying.) All transmitters have been instructed to start

messages travel in order to be received at your station. Therefore it will be necessary for you to note the distances of the transmitters from your station on each message. After all the transmitters have finished the broadcast, add the total mileage of the C.W. stations and the total mileage of the spark stations. Then add these two figures which will give you a grand total. Mail your copies to the American Radio Relay League, 1045 Main St., Hartford, Conn., so as to reach this office not later than July 26th.

If you are not interested in the contest, please have a heart and keep your transmitter silent during the transmitting period so the thousands of other amateurs can copy. We will have QRN, and we can but put holes in that, but please let us have your co-operation in a way that will reduce QRM to the very minimum, and

**Schedule of Transmitters for the Static-Puncturing Contest, July 16th and 19th.**  
Eastern Standard Time, P.M.

| Division       | C.W. | Wave | Time  | Spark | Wave | Time  |
|----------------|------|------|-------|-------|------|-------|
| Ontario        | 9AL* | 250  | 8:46  | 3BP*  | 200  | 8:50  |
| New England    | 1AE  | 275  | 8:54  | 1ZE   | 250  | 8:58  |
| New England    | 1TS  | 275  | 9:02  | 1AW   | 200  | 9:06  |
| Atlantic       | 2ZL  | 275  | 9:10  | 2JU   | 200  | 9:14  |
| Atlantic       | 3AAO | 280  | 9:18  | 3XF   | 375  | 9:22  |
| Roanoke        | 8ZW  | 325  | 9:26  | 8SP   | 200  | 9:30  |
| East Gulf      | 4GL  | 220  | 9:34  | 4XC   | 375  | 9:38  |
| Delta          | —    | —    | —     | 5ZP   | 250  | 9:42  |
| Delta          | —    | —    | —     | 5ZL   | 300  | 9:46  |
| Midwest        | 9HT  | 200  | 9:50  | 9OE   | 200  | 10:02 |
| Midwest        | 9ZB  | 375  | 10:06 | 9LC   | 200  | 10:10 |
| Central        | 8IB  | 200  | 10:14 | 9ZN   | 375  | 10:18 |
| Central        | 8DE  | 210  | 10:22 | 8ZL   | 375  | 10:26 |
| Dakota         | 9XI  | 360  | 10:30 | 9ZX   | 375  | 10:34 |
| West Gulf      | 5ZA  | 375  | 10:38 | 5ZX   | 375  | 10:42 |
| West Gulf      | 5ZW  | 375  | 10:46 | 5ZC   | 375  | 10:50 |
| Rocky Mountain | 6WV  | 375  | 10:54 | 6JT   | 200  | 10:58 |
| Pacific        | 6ZX  | 375  | 11:02 | 6OH   | 200  | 11:06 |
| Pacific        | 6EN  | 200  | 11:10 | 6ZO   | 375  | 11:14 |
| Northwestern   | 7XF  | 250  | 11:18 | 7DA   | 200  | 11:22 |

\*Canadian

promptly on schedule, and not to start 5 seconds before or 5 seconds after the scheduled time and not to overlap by even 1 second. The schedule is on Eastern Standard Time. Now your part will be to copy—copy any part or all of every message from every C.W. and spark station. You must have the signature of two people who witness the actual reception of the messages and these signatures must appear on the original copy that is sent to this office for verification. Remember that you will be given due credit for any part of any message that you copy, so do not feel discouraged if you do not get a perfect copy—send in what you do copy. While accuracy and completeness of copy will be considered in computing the percentages, the main feature in determining the winner is based on the grand total of air line miles over which distances the

accept our thanks for your efforts in asking others to do the same.

## SPARK RECEPTION ON HONEYCOMBS

(Continued from page 25)

[Editor's Note—What Mr. Kinyon uses is "zero beat frequency." The tube is really in full oscillation but at the same frequency as the incoming signals, so that no beat note is produced. In such adjustment the full benefit of heterodyne amplification is received on spark signals and without distortion of the musical note. It is well worth the somewhat critical adjustment necessary to secure it.

In the concluding installment of this article, in our next issue, Mr. Kinyon will tell just how he adjusts his equipment for best results.]



# EDITORIALS

## de AMERICAN RADIO RELAY LEAGUE



### What We Want in Radio Law

THE scheme of the two radio bills introduced in the House by Congressman White and in the Senate by Senator Kellogg at the instance of the Department of Commerce is to get away from outlining operating regulations in the law and instead provide a law that will establish an administrative organization and facilities for publishing regulations from time to time, so that the regulations can be changed as progress in the art demands without the necessity of framing a new law every few years. As we stated in these columns last month, our Board of Direction after a careful consideration of the case feels that the province of the amateur ought to be specified in the law. Some folks, we suppose, will think we are highly inconsistent in asking for what offhand seems to be a request for direct discrimination in our favor. But is it? We do not think so.

These bills would provide for the government of all classes of stations by regulations promulgated as occasion required, by the Secretary of Commerce. Now the present Secretary and the present Commissioner of Navigation and the present Chief Radio Inspector are all friendly towards the amateur and know his value, and we haven't any doubt that administration of such a law by them would be entirely satisfactory to us amateurs. But they won't be in office always, and we ask you to just imagine a Daniels as head of the department looking after us! We wouldn't be safe, and as now is the time to express ourselves for future years we are doing so. While we amateurs are well organized for looking after our interests in general, we are not financially equipped to wage a continual defensive against powerful commercial or political interests that might want to invade our little domain for some purpose of theirs. We feel very strongly that the only reason we have been unmolested in past years is that the law has very definitely said that there shall be amateurs and that their wave shall be up to 200 meters. As a class we are not prepared to combat big interests perpetually and our only safeguard is to get our future written into the law. And as we pointed out last month, commercial companies won't put good money into installations to use waves near the amateur's as long as there

is possibility that the latter may be changed to interfere with them; yet the intensive development of radio demands that use be made of all waves, so that definitely specifying ours in the law should stabilize the commercial use of nearby waves. An exception to this end in the case of the amateur would not be terribly inconsistent, since we are at about one end of the waves of value so that we could be put to one side and the use of all other waves left to regulation without disrupting the scheme.

And it's vital that no drastic change be made in our allocation. Our apparatus is extremely highly specialized and would be made virtual junk if we were suddenly given a wave length appreciably different from our present. And our investment in equipment runs up into many millions of dollars.

We have another thing in our favor in the very consideration of what wave lengths we should ask for. The Department of Commerce had a committee last year consisting of representatives from every radio interest in the country and they gave consideration to what wave length the amateur should have in new law. The old basis wouldn't do, for the navy want a wave under ours for chaser boats, and yet we couldn't be put up too high because the ship-to-shore telephone service wants waves around 300. They had many meetings but eventually a tenable basis was arrived at, with every interest agreeing that they would be satisfied if such waves were assigned the amateur. Broadly speaking they are 180 to 220 meters for spark, and 180 to 250 for C.W. If an unwise administration should assign waves other than the above to us amateurs as long as present conditions in the art maintain, they would certainly be stepping on the toes of one or more strong interests, yet the above wave lengths form a basis that has been mutually agreed to. And with the Navy below us and the A.T.&T. above us, both clamoring for more room, believe us we would like to see our wave length written into the law so that there would be no question about it.

These, then, are the reasons why we are asking our friends, the Department of Commerce, to amend their new bills to except the amateur and write his place into the law in black and white.

### What We Are.

THE A.R.R.L. used to be just a little handful of ardent enthusiasts, but that was long ago and now we are a big national organization, recognized as the standard-bearers wherever amateur affairs are concerned. Recently we told of losing our goat to a chap we ran across who had never heard of our A.R.R.L., but altho such birds are rare it is not unusual for us to discover that apparently well-informed amateurs have no knowledge of what we are or why we exist. When they got into the game they heard of the A.R.R.L., liked what they saw of it and joined, largely perhaps because everybody else they knew belonged. As time passed they heard of our relay work and got a place in it, and they see and perhaps like some of the other things we do. But the Big Idea often never gets thru to them.

The A.R.R.L. is an organization of amateurs, and every official in it is likewise an amateur. From its very inception it has been non-commercial, its originators being amateurs with no axes to grind and clearly realizing that there could be no successful organization unless it be co-operative. The phase in which the non-radio public best knows us is as relayers, but we are much more than that. We are the amateurs and the writer of these poor lines is likewise an amateur. QST is our magazine and thru it we bind ourselves closer and accomplish things together, but QST is incidental to the League and simply does its best as the A.R.R.L.'s mouthpiece to further things "of, by and for the amateur."

Offhand we know no parallel to our organization. Always we have steered a careful course among the rocks of commercialism and personal ambition, and today we truly have a great big national self-governing institution which is a leader in amateur thought. We stand for observance of the law and for scientific progress. Our union makes possible many things of co-operative benefit: our relaying, our ability to speak as a solid body when dangerous legislation threatens, the many things of national breadth which we undertake. Almost every amateur of any prominence belongs to our League and so, as we are the amateurs and incapable of becoming a body to merely exploit the amateur, we are recognized as the leaders, the body politic in the amateur world.

From these things and based upon them there has come into existence a wonderful spirit—the A.R.R.L. spirit. There is a clean organization of the amateurs themselves, whose interests are those of its individual members, and with a feeling akin to amazement amateurs have realized this and come into our ranks. Look at our Operating Department, with almost four hundred officials serving without com-

pensation, grinding out letters, perfecting their network, inspired by the common cause and safe in the knowledge that they're not being "exploited"—realizing, in fact, that the A.R.R.L. is *they themselves*. Consider the official relay stations, the fading test recorders, the membership of our Board of Direction, the affiliation of some two hundred clubs—all of us imbued with the same wonderful spirit and working together in the advancement of a thing we all love, Amateur Radio. That's what it means to belong to the A.R.R.L.

### This Word "Citizen"

YOU'VE seen it—we use it frequently in these columns. Some folks seem to object to it, mostly because there isn't anything the matter with the word "amateur" while "citizen" brings up to them visions of soviets, Citizen Bessey and Citizen Galyean and so on, red flags and parlor Bolshevism, etc.

Now there's nothing the matter with the good old word "amateur." It correctly defines what we are, and implies a good clean sport. In sports it has always been unfortunate to lose one's amateur status, and likewise in these days the word rarely carries any stigma of inefficiency or clumsiness but generally quite the contrary. It means something definite and pleasing, and is the word under which we have our rights in the law.

On the other hand we are trying to get away from the idea that our radio is a plaything, and establish before the general public the fact that serious communication is being accomplished by private citizens. Do you realize that our radio provides about the only way by which an individual can communicate intelligence to another beyond the sound of his own voice without paying tribute to a government or a commercial interest? It's so, and it's a big thing and becoming increasingly important as new-comers enter the game. Simply to use a word implying that we love our sport and are skillful at it does not seem enough to us. When we speak of "Citizen Wireless" we convey a picture—no longer of little boys in short trousers playing with toys, no longer of eccentric dabblers, but of a vast field in which the private citizen of this country may enter and carry on useful communication. And when we stand up before a Congressional committee it's a good term too—just think exactly what it means!

So there're things to be said both pro and con and the subject is by no means a closed one. While we like the expression "Citizen Wireless" because it implies perhaps a more serious effort than the word "amateur", we're not abandoning the latter nor endeavoring to foist the former where it may be distasteful. Let's talk about it a little in QST—just what do we think about the matter?

# The Operating Department

F. H. SCHNELL, Traffic Manager  
1045 Main St., Hartford, Conn.



**C.W.** is fast supplanting the spark transmitter, and while this change is being made our message traffic is suffering. For the month of May a total of 6,699 messages is reported as against 10,532 for the month of April. A drop of about 37%, but as soon as a few more good C.W. stations come to the front our traffic will climb very rapidly.

The New England Division is honored for the third time in succession with the star station in traffic handling, and this month 1ZE (formerly 1HAA) must take second place to 1CK, who handles messages at a terrific speed and can be heard at 30 per 'most any night. F.B., Robinson.


MR. P. F. ROBINSON, 1CK  
Braintree, Mass.  
412 Messages  
New England Division

There is no use trying to dodge the issue. C.W. is here to stay and unless we are afflicted with a foggy brain, C.W. will be so far ahead of the spark that messages of unimportance will be left for that means of communication, while the messages of more importance will go via C.W., because they will get thru. And even when the "rock-crusher" at 9ZN is thrown into the discard, we will not be surprised, and all of you know what Matty thinks of a good spark. However, glance thru the Central Division report and note that communication is maintained with C.W. while the spark stations have given up in despair. On the other hand we point out to you the work being done by 2ZL, 4GL, 3AAO, and 1TS, all of which are C.W. stations. The spark set at 2ZL was junked so long ago that not even a punctured condenser remains. And 2ZL moves messages in groups of 5 and 10 almost every night regardless of QRN, providing of course that other stations are on the job. The only good reason that we can give for your not hearing the hundreds of C.W. stations is because you do not listen nor tune properly for them. Spare the key some night and just listen for C.W. stations. We will

venture a guess that you will be astonished at the goodly number you hear, and upon inquiry you will find most of them using less than 50 watts. And notice how the C.W. signals just cut right thru static.

Considerable activity in the Roanoke Division is the changing over of transmitters. The spark is going out while the C.W. is coming in. And that absence of signals from the Delta Division is caused by old man QRN. In other words they have no C.W. stations with which to carry on communication in the division. How about it, Jawn; when can we expect to hear your C.W. sigs?

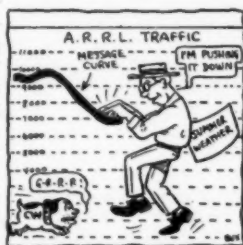Reports from the Pacific and Midwest Divisions are missing. The other reports follow:



## NEW ENGLAND DIVISION

G. R. Entwistle, Mgr.

Conditions for DX work have been bad lately, due to QRN, aurora, etc. The spark stations seem to be affected more than C.W. Organization is one of the activities taking the most time at present. Especially is this true in Boston, where the newly formed Boston Executive Council is endeavoring to bring all classes of radio amateurs into a closely allied body.

The Boston Executive Council has secured the co-operation of the Army, Navy, A.R.R.L., Department of Commerce and commercial interests. The Council has adopted the Chicago Plan by revising it to the needs of Boston.

The Police Departments in Boston, Hartford and Lowell are co-operating with the amateurs in the transmission of reports of stolen automobiles and any other information through which the public may help them.

A.D.M. Robinson (1CK) reports a new radio station in Lowell, 1LZ, who we expect to help in a route through central New England. 1HAA has been comparatively quiet this month, handling only 304 mes-

sages. Part of this slump was due to bad weather and the rest to lack of pep in his non-synchronous. 1HAA is now installing a 500 cycle quenched spark set to operate on a special, 1ZE. 1ZE will have three working waves, 200, 250, 375 meters. D.S. Johnson (1DY) must have a job. He is not heard on the key much lately. 1MAD of Pawtucket, R. I., is another comer. He has a 1KW spark set and promises to be a help to DX work. 1CF, 1UN and 1DH are making a lot of noise on C.W. 1XE and 1QR are working fine concerts nearly every evening.

D.S. McLean (1JQ) reports conditions between Springfield and Boston are improving only slightly. Southbridge does not seem able to get in communication with Springfield as yet due to a tremendous amount of QRM caused by high tension wires near that station. 1GY signals fade badly. Springfield finds it more satisfactory to work with Boston. 1WR comes through QSA and if not too much QRM can handle traffic through him. Recently 1XM and 1QR have been coming through QSA. In a short time we will have a station in operation on C.W. at Warren, Mass., N. B. Judkins, 1PM, formerly of East Providence. This station will be half way between Springfield and Worcester, and there is no doubt but that traffic can be handled through in fine shape.

In regard to Albany: We find many stations en route to Albany—1KBO at Easthampton, Pittsfield Boys Club at Pittsfield, and other stations in between points,—so that by fall this route will be well organized.

By the next issue of QST we will be able to outline a route north and east of stations not more than 25 miles apart that will make it possible to handle traffic under all conditions. At the present time 1CCY, 1UAV and 1JQ are handling all Springfield traffic including police reports.

A.D.M. Castner (1UQ) of Portland, attended the banquet of the C.W. Club of Boston and reported C.W. increasing in his district.

#### ROANOKE DIVISION

W. T. Gravelly, Mgr.

*Reported by A. S. Clarke, Traffic Assistant.*

C.W. is taking this division by storm. From all parts come reports of C.W. sets being built and when fall opens up practically everybody will have some sort of C.W. set. Remodelling of sets, addition

of new equipment and general preparation for better work next fall is the order of the day. Static has been so severe that the number of messages handled shows a decrease. C.W. seems to be the only thing that cuts through the terrific QRN.

The Division Manager is planning a complete re-organization of the division with several new appointments to be made.

D.S. Wohlford reports that 3BBF at Catawba has his transmitter in good shape and is working Roanoke regularly. A new station is reported in Lexington, Va., and one also at Salem. The Virginia Polytechnic Institute at Blacksburg will have three 1KW outfits.

A.D.S. Higgins will operate a set in Galax instead of Oldtown. A.D.S. Gundry at Stonega reports communication established with Bristol and is trying to connect up to 5DA. 3GO at Norfolk is undergoing a complete remodelling and when the season opens up, will have spark and high powered C.W. and phone. 3EN, city manager White of Norfolk, is putting in 15 watt C.W., also 3VV. 3ACT is handling his share of relay traffic, in spite of QRN, and is installing C.W. 3ACE, 3ACK and 3ACZ are reaching out but static has prevented much traffic being handled. The terrible QRM from NAM is being worked on but still remains the champion nuisance of the district.

The situation in Charlotte, N. C., remains about the same, with several C.W. sets in course of construction. A new 1KW set is in prospect at Asheville, N. C., also a C.W. set. 3BZ and 3AEV are both installing C.W. sets.

No report from D.S. Heck of West Virginia, but 8SP's spark is still heard so we know that traffic is being handled in that section.

No report received from Blair of Richmond. It is regrettable that of the 60 some stations in Richmond no one seems to be interested in DX relay work. They seem to be entirely contented to sit down and talk among themselves and call the neighbors in to listen to KDKA's music and news.

Although static will prevent the usual amount of relay work, there is no slackening of interest or laying down on the job in this division. Everybody is working and planning for the biggest season of all next fall and winter. So look out for the sparks and C.W. of the Roanoke Division when Old Man Static goes to sleep again.

Reported messages, 100.

#### EAST GULF DIVISION

E. H. Merritt, Mgr.

Practically all work reported this month has been accomplished by blasting thru QRN, as we have had a liberal supply on hand every night now for nearly two





months. There is a fine spirit being shown by the fellows still hammering away and actually getting thru where it appears to be impossible. The fact that everyone is rebuilding and getting ready for the fall season makes us believe that the East Gulf is going to show up some of the other divisions too. F.B., fellows.

4EG of Woodruff, S. C., reports that he has at last been able to reach out and connect a few DX stations. He says prospects for improvement in S. C. are good, stations in Greenville, Greenwood and Gaffney all trying to get started. This is the first real good news received about S. C. and it is about time we had a few good stations in the state.

D.S. McIlvaine reports that all Alabama stations were hard hit by storms during the month, practically every antenna in the state being blown down except at 5XA. Carrie, of Montgomery, had his antenna destroyed by lightning but other damage was not severe. 5JO in Birmingham has installed a radiophone and will have it ready next fall. The radio club in Mobile is progressing nicely. The chief operator at NGT is giving them instructive talks and assisting with their sets.

In Florida we are going to lose a couple of good men, 4AM and 4DL. 4DL will return next fall but 4AM is moving to Ohio. We are sorry to lose him from the East Gulf but know he will make a good man for the Central Division. 4AM was one of the first to help open the Florida route for traffic.

4ZN has been held up a long time trying to find a condenser that will hold up under his "coffin". He has moved his station to a better location.

Near Jacksonville, the Lybeck Ocean Harvester Co. has installed a radiophone and is experimenting with their fishing boat, using 350 meters. Anyone hearing "LOH" (temporary) on fone please write J. S. Chapman care of the company at Lybeck, Fla.

D.S. Benning of Georgia has little to report except that about half of Atlanta has been bitten by the C.W. bug. The Atlanta Radio Club has adopted the Chicago plan to control QRM. They are also getting all local stations down to 200 meters. 4AU, 4BT and 4XC recently made a week-end visit to 4BQ. They report that with his new apparatus and remodeled station 4BQ should be the best station in the south. 4BQ reports that a radio club has been formed in Cartersville, Ga.

4BK has installed a 1KW now, and has otherwise improved his set. 4DV in Columbus is still working on his set and has already connected with several DX stations. 4CU in Jackson, Ga., is heard occasionally. 4AG reports that QRN has held him almost helpless for two months. He is also improving his set and getting

ready for better weather. 4DT in La Grange, Ga., has busted loose with a good station and has taken a big hand in handling traffic this month. 4GL in Savannah is blasting thru QRN almost anytime with his C.W. Mr. Hill has about the best C.W. set in the Division but several others have promised to make him hustle to keep it the best. Let's hear more from C.W. men in the East Gulf.

Reported messages, 198. Busiest station, 4FD, 58.

### CENTRAL DIVISION

R. H. G. Mathews, Mgr.

The severe static of April and May has reduced traffic work throughout the greater portion of the Division. This is especially true of those routes depending entirely on spark transmitters. Apparently the use of C.W. is a solution of consistent summer work and accordingly strenuous efforts are being made throughout the Division to form and put in operation such routes. The District of Eastern Ohio is especially active in this respect and we believe that satisfactorily and consistently operating routes will soon be in existence connecting Ohio with both the east and west by daylight with all parts of the country.

Mr. and Mrs. Chas. Candler, D.S. of the Miami Valley District of Ohio, report message work decreased considerably, due to the season and the fact that part of the stations were out of commission. 8ZL and 8FT were out of commission for all but a few days during the month. 8FT is now ready again, but 8ZL will be out for some time longer. Other stations in the district were considerably handicapped by having to find outlets for their traffic other than 8ZL and 8FT on whom they had largely depended.

Cincinnati seems to have fallen back into her old rut of keeping by herself rather than co-operate with the rest of the district. The personnel there never send in any report, either general or traffic.

Two newcomers from Dayton, 8AJB and 8AEE, sent in good reports this month and are to be commended for their good work. 8AWU and 8ANY are handling Xenia traffic in good shape, and a station is starting at London, O. 8AEY at Lebanon is beginning to work more regularly and comes in handy to link up with Cincinnati. Nothing more has been heard from Circleville or Chillicothe.

It is regretted that so many stations fail to send in reports. Not half of the stations do so and many of those that are left out do good work and are among the most active in handling traffic. These include the entire number in Cincinnati, 8AEY at Lebanon, 8HG and 8JB at Columbus, 8TN at Dayton and many others. I should like through the columns of QST

to request that all stations in the Miami Valley District who are interested in or take part in relay work, get in touch with 8ZL and ask for appointments. Many of these stations could be used as alternates in routes already established and others could link up in new routes.

J. Warren Wright has been appointed City Manager of Springfield. He has recently received a special license and his station call has been changed from 8DC to 8ZAA.

All messages sent by 8IB and 8IV this month were transmitted on C.W. and buzzer modulated sets. A small portion of the work at 8ZL last month has also been done by radiophone.

Mr. K. A. Duerk, 8ZY, D.S., Toledo District of Ohio, reports that in this district most of the good DX relay stations are either closed down or, due to the poor relay weather, not operating very much. 8ZR has been heard only a few times. 8KP is temporarily out again, due to burned out transformer. All Detroit and Michigan traffic gets off in good shape, being sent through 8LV at Ann Arbor. Eastern Ohio traffic has not been going quite as promptly as in the last few months, because of the standbys, 8ZN and 8ZR, not being on as much as usual. We don't know the cause of this at 8ZR as they have a half dozen operators, unless it would be that QRN has them scared out. At 8ZN, Mr. Kauffman attends college at Pittsburgh, and Mr. Preston's work has kept him busy, so that he has not been able to devote as much time to operating as formerly. The north-eastern part of the district has not been developed like it should have been. There seems to be a lack of interest in real relaying. Accordingly, to stimulate development in that part of the District, Mr. James P. Turner, of 8AKM, 681 George St., Clyde, Ohio, has been appointed Assistant District Superintendent, having charge over the counties of Wood, Ottawa, Sandusky, Seneca, Huron, Erie, and Lorain. These counties are now out of 8ZN's jurisdiction. Mr. Turner is a wide-awake radio man, and has offered to do his best in getting that part of Ohio lined up. He states that he can cover that territory with his car, and see the operators personally. Upon Mr. Kauffman's recommendation Mr. Ulmer, of 8AJK, has been appointed C.M. of Bucyrus, Ohio.

Mr. J. A. Kolb, 90X, D.S. of Kentucky,

reports that due to the heavy QRN very little work has been done. The number of amateur radio stations is rapidly increasing in this district. Formerly the amateurs were satisfied to work locally but after seeing the results achieved by 90X, they speak only of DX.

9VZ, Covington, is having trouble with his aerial and condenser, hence his DX is curtailed; 9IO has a C.W. set going and is reaching out; 9UH, Newport, the star DX station of Kentucky, continues to do very good work; 90X, Louisville, will dismantle and install at a new location.

Mr. Hutchinson, A.D.S. for Northern

Indiana, advises of a very meagre report from Ft. Wayne, yet it would be supposed from the number of stations there that there should be much more reported. No South Bend stations have been heard during the month. Are they all dead? It seems that from the number of aerials which the A.D.S. has seen there should be at least one active station in the city.

9ME is again on the air and comes in louder than ever. 9DF, Angola, is rebuilding his receiving set. 9DBQ, Stroh, is again back on the air. 9HR, Middlebury, Ind., has re-installed his transmitter, more than doubled

his radiation, and with a new short wave regenerative set and two-step amp. has things in fine shape. The A.D.S. is ready for the summer relay season. 9HR has been getting in to Chicago regularly. 9ALY, Goshen, Ind., has just installed a new and much higher aerial, and a new short wave set preparatory to jumping into the summer relay game. 9FS, Goshen, Ind., has installed a new short wave regenerative set and is all set for summer work. 9FS has been doing exceptional DX work, being on the job practically constantly, and proves a valuable station to the district. 9FG, Goshen, Ind., is on the job very little.

9AZX, at Jonesboro, Ind., has installed a 3 tube C.W. set and comes in very QSA at all points in the district. He will prove valuable in handling traffic to Indianapolis. 9AUC, at Albany, Ind., has offered his assistance in handling southern and western traffic. Prospects in the District are very bright for summer work and the A.D.S. will do all in his power to see that things get into good working order.

The station at Purdue University has been in operation regularly throughout

#### Howard H. Moore,

9FV, A.R.R.L. District Superintendent for Northern Indiana, passed from this life at his home in Elkhart on May 28th, after an illness of many months.

Mr. Moore was always one of the Central Division's best men and a strong A.R.R.L. booster. He made a good district out of Northern Indiana with almost nothing to work with, and his interest and loyalty to his work is attested by the fact that during his last two months he handled his district activities and made his reports from his sick bed.

Truly here was A.R.R.L. spirit, and in the passage of 9FV to a land where signals never fade we have lost a faithful friend and co-worker in the cause of Amateur Radio.

the past month.

9YB has been doing some pretty good work.

9UJ at Rensselaer, Ind., has some new equipment and is coming in pretty well. He will make a pretty good outlet to Hammond and Gary when he gets a little more experience in operating.

Mr. Burhop of the Wisconsin District states that many of his stations did not submit reports for April. 9TO of Antigo, who hasn't had very much success with his  $\frac{1}{2}$ , is expecting to put in a 1 KW United Wireless transformer.

The Fox River Valley bunch, Neenah, Menasha, Appleton, and Oshkosh, are expecting to organize an executive council and hold joint meetings. The Oshkosh Radio Club is starting the movement. M. C. Lapp, of the Ann Arbor Fleet, has put up a 1 KW station at his home at Plymouth. His call is 9DLX, and he has been extremely successful in DX work. 9ACM, of Sheboygan, has installed a 1 KW transmitter and added two steps to his regenerative receiver and is helping out great. 9DNL and 9DMU of Manitowoc with  $\frac{1}{2}$  KW transmitters and regenerative receivers are in shape to help 9ZL.

Mr. C. E. Darr, D.S. of Michigan, reports: this state is rapidly falling in step with the others in becoming CW-ized. 8KM, 8BO, 8OJ, 8ADY, 8LV and 8ZZ all have C.W. sets that are doing good consistent work and are in close touch with the DX Ohio stations in daylight. A daylight route exists from Detroit to Grand Rapids. Detroit can now work Cleveland in daytime on 5 watts C.W., a thing that never could be done on spark even at night so we have reasons to feel elated over C.W. Traffic (DX) has fallen off somewhat but we are rather busy with interstate traffic.

The Cleveland Radio Association has formed traffic regulations which are being put into effect with excellent results. These regulations are as follows:

- 8:00 A.M. to 7:00 P.M. Free Air. If possible, confine testing to 6:00 to 7:00 P.M.
- 7:00 P.M. to 10:00 P.M. Local work only, 50-mile radius. One-quarter kilowatt limit.
- 10:00 P.M. to 11:30 P.M. Long Distance tryout. No local work.
- 11:30 P.M. to 8:00 A.M. Long Distance A.R.R.L. message work only. No Conversation.

Stations operating up to 11:30 P.M. will cease work at that time. Work only one long distance period.

Reported messages, 2444.

#### DELTA DIVISION

J. M. Clayton, Mg<sup>r</sup>.

Due to the few good nights for radio,

the amount of traffic handled thru the division for the month has been exceedingly small. From now on till September or October it's a case of relaying via Uncle Sam's relay whenever any stray messages come wandering thru.

5ZP has been forced to take a vacation on account of bum health, and is spending most of his time in bed right now. Where there's life there's hope, tho, and we all know that such a natively strong chap as ZP is, will pull thru in fine shape and we also know he will be back at the set as soon as he can.

Hutcheson, 5DA, D.S. of Tennessee, reports several new stations being installed in that state.

There has just been a station completed at Chattanooga. Knoxville boasts of six DX stations now. Mr. M. M. Roddey of Cleveland, Tenn., is putting in a 100 watt C.W. station, and 5ER of Nashville threatens to do the same thing.

5ZAC, ex 5EA at Baton Rouge hasn't been heard from for several months. Evidently Barrow has decided to let QRN down him 'way too early in the year.

5ZAB, Pullen, of Houma, La., had a little aerial trouble when their main pole was blown down in a storm. They have decided to start rebuilding their station for next season.


5YH is still on the job, quite busy right now trying to get the howls out of a new three step short wave regenerative receiver. Captain Baldwin quits tearing off the tinfoil he has pasted on the back of the panel, as a capacity shield, every now and then to handle a lil traffic. However, there have been comparatively few nights this month in which it has been possible to even copy DX stations thru QRN.

No report received from Mississippi. We suppose that Prof. Kennon at 5YE has been too busy with school work.

DeBen, A.D.M., contributed a notable piece of work to the art of relaying when he discovered not only a RADIO station in Memphis, Tenn., but a whole nest full of hams in a radio club there. How he ever located 'em is beyond us. We have been longing for ONE real station in Memphis ever since the days of T. J. M. Daly of 5AK who used to be Thordarson's record-buster in the days of 825 miles on galena night after night.

5ZK is leaving Franklinton for the summer months as he is planing to take an auto trip up to Canada.

No report from Anthony of Shreveport.

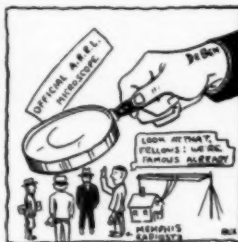

The last time we heard Willie on radio, he was giving the natives an exhibition of the whys and wherefores of radio at some County Fair at Shreveport. That was way late in the wee hours of morn so we guess Willie has been going to bed early ever after to make up for lost sleep.

5JD of Little Rock has been on the set very little this month, mostly due to QRN being too bad to do much good consistent work. Kinsolving is going to blossom out next season with a "sink" gap and all that. If this whole Delta Division ever opens up all at once next season the air will be full of nothing but sink gaps.

We have a new station at Thibodaux, La., 5YL, which looks like it will be a corker.

#### DAKOTA DIVISION

Boyd Phelps, Mgr.

Relaying has dropped off considerably during the past month. OM Static is taking a whack at the ether and traffic has been reduced to almost nothing. In the month of May sun spots and Aurora Borealis played havoc with both wire and wireless. This discouraging stunt of nature has caused most of the best DX stations to be out, either for repairs or for their owners to catch up on sleep lost during the past season. Either excuse is somewhat justifiable but it is hard on relay traffic. This gives an excellent opportunity for the smaller stations to prove their worth. The ones that claim the big boys handle traffic right over their heads during the winter are now in a position to be of great help to relay traffic by filling in the large gaps that are now open in so many of the relay routes. There is a place for a good station in every town on the relay routes which are now largely on paper only.

To handle traffic successfully during the summer season all stations on the route should be within daylight range of each other and none of the jumps over forty miles. Last summer it was found that over certain areas the best time for working was at daybreak when the static was at a minimum. However, in other localities experiments seemed to indicate that at noon or at sunset was also a very good time to clear relay traffic. These experiments were not nearly exhaustive enough and it is one of the things to be accomplished this summer. With this in mind, stations are urged to test with each other at all times of day to determine the best hours of working in certain directions and to let the D.M. know their conclusions.

Northbound traffic if routed so as to reach Sioux Falls, S.D., can be easily handled north over a very good route to all of eastern North Dakota and as far north as Winnipeg, Manitoba, in Canada. The summer northern route is a very

successful fizzle when it comes to short jumps. The absence of stations of any description west of Ellendale, N. D., to the 7th district necessitates clearing on only the better nights but all stations plan on listening at least half an hour each night as quite often some very good nights turn up and messages

may be cleared by the pound. The route from Wahpeton to Minneapolis would be working nicely if all the stations could work the stations next to them on the route. Stations are especially scarce outside of Duluth and Superior so that no route can come within a hundred miles of these cities. Mr. Bridges, 9YAC, has plenty of confidence in a C.W. set he hopes to have finished soon so perhaps we need have no fear of not getting msgs. to his part of the country.

Station owners in every town are urged to get in touch with their District Superintendents or Division Manager as there are many positions open on the routes that must be filled to make relaying all the year around a success.

Reported messages, 210.

#### NORTHWESTERN DIVISION

R. T. Galyean, Acting Mgr.

Howard F. Mason, 7BK, newly appointed A.D.M. of Seattle, reports that 7IY and 7BK have been handling nearly all the Seattle traffic the past month. Traffic east goes thru 7FI with little trouble; and traffic south is sent thru 7CW, 7DA, or any number of 6th District stations. Summer conditions practically prevail but no trouble is experienced in working Portland stations, which roar in 'most every night. 6th District stations are heard consistently except those around Los Angeles and the southern part of California. 7MH of Olympia has been coming in good of late, and his station may be part of that daylight route to Portland which we are all looking forward to. North of Seattle, 7LS of Ferndale has been on the job regularly and has done his part well. With his help a day-light route from Seattle to Canada is now in operation. 5CP of Vancouver, B. C. seems to be taking traffic and reaching out in fine style.

In Tacoma, Miss Dow, District Supt., reports that, with the coming of summer, fading seems to be more noticeable. Portland stations are beginning to be more in evidence, 7DA being the most reliable





station handling traffic to the south. The most consistent station to the east is 7FI at Pullman, Washington who is in almost constant communication with stations both east and west of him. 7YA is the most reliable 375 meter station to the east.

H. E. Cutting, 7LY, A.D.M. of Bozeman, Mont., reports things in that end of the Division going as well as usual. There has been little slowing up due to QRN as yet, and signals seem to keep their normal strength. There are two northern routes to the east that can be depended upon at the present; one is thru 7CC to 7LY to 7ZO and the other thru 7YA to 7ZO or 7LY then to 7EX or 7ZG. From these stations to the south traffic is handled thru 6ZH or 6ZR.

At Portland, Old Man QRN has started his program of relentless interference, and the Sixth District stations have begun their summer fading program which retards the speed of traffic flowing in that direction. The northern stations in Tacoma, Seattle and Vancouver, B. C., are coming to life as far as the Portland District is concerned. These stations are seldom heard during the winter months, but with the coming of warm weather their signals seem to get through to Portland with but little QSS. This is one of the freaks of the Northwest.

The eastern stations in Idaho and Montana are coming in with their old reliability, the weather having little or no effect upon their signals. The Eugene, Oregon, stations are getting south at times, but are seldom heard here. 7CN at Marshfield has been heard during the month but has not been worked. Messages in that direction are QSR'd through the 6th District stations who seem to have less trouble in working him. Astoria and the lower Columbia River District seem to be dead at present as no stations are reported working out. The Upper Columbia River district seems to show life at times when 7ZH at Enterprise is on the job, but he seems to be taking a lot of sleep lately.

7ZJ at Vancouver has installed a 375 meter wave with which he steps out equally as successfully as with his old 200 meter wave. He has been heard this month by 9KL and 9YW. You'll hear him yet, Hiram!

In Portland 7ED, 7JW, 7GA, and 7DA on sparks and 7ZI on C.W. have been very successful in clearing traffic through this district. 7ZI has worked as far south as Los Angeles with his C.W. set in which he is using two 5 watt oscillators.

At last we have the long needed station at Corvallis, Oregon, where the Oregon Agricultural College is located. 7YJ, ex 7PV is coming through like a local station on his 375 meter wave. 7CW at Silverton, and 7BH at Salem, Oregon, are still holding their share of the air with the same old reliability and efficiency. Owing to lack of

organization in many parts of the Northwestern Division, complete reports have not reached the new management. The whole Division is undergoing a complete reorganization, a report of which will be forthcoming in the near future.

Reported messages, 720. Busiest station, 7BK, 112.

## ONTARIO DIVISION

K. Russell, Mgr.

May has been the best ever for the Ontario Division. In spite of extremely heavy static throughout almost the entire month a practical working relay chain through Southern Ontario has been initiated and by far the most messages ever handled in Ontario Division have been relayed this month. This has been in the main due to the fact that several new stations have been put in commission, and have vastly improved the chances for a really reliable working chain in the fall.

W. Carter reports from Windsor that messages are going thro' well tho the QRN has been terrific lately. A new Radio Club has been formed in Windsor and vicinity which will endeavor to handle traffic in co-operation with the A.R.R.L. working under a modification of the Chicago plan.

In the Southern District there has been a change in the D.M., as Wes. Mitchell, 3BA, has had to abandon the position owing to press of business. Gowan of 3DS in Kitchener has taken over his work. This district has shown a startling improvement within the past six weeks, and there are now several good reliable stations which can be counted on for assistance in relaying messages south and west, notably, 3KS in Niagara Falls, Ontario, 3MO in Port Colborne, and 3LI in Welland. All these stations have been in touch with Toronto and other Ontario stations many times, and will furnish invaluable assistance in forwarding traffic from now on.

In the Toronto District there has also been some improvement and the new station erected by E. Rogers of 3BP has been of considerable value for relay work. Mr. Rogers has moved his station complete to New Market, Ontario, about 30 miles north of Toronto. This has enabled him to use a longer wave length, and has got him out of the local QRM so that his range is much more effective now. He has already succeeded in working 3DS in Kitchener, 3BA in Brantford, and 3KS in Niagara Falls. Traffic from this station has also been forwarded thro a number of Buffalo stations. 3BP advises that during the past winter season his signals were copied at sea 1600 miles east of Newport News, and at 9OE in Wichita, Kansas. He reports having handled 24 messages in less than a

week after getting set installed. In Toronto, 3GE has been maintaining a regular early morning schedule with 8CG in Niagara Falls, N. Y., and at present the most reliable means for getting traffic to Toronto and other Ontario points seems to be through the latter station, or 8FE or 8AHV.

In Eastern Ontario static and vacation time has cut down work to a very large extent, and no report has been forthcoming from that region this month.

Reported messages, 73.

#### ALASKAN DIVISION

Roy Anderson, Mgr.

Thru the kindness of 7PO of Seattle, two more Alaskan amateurs have been brought to light. Those two are R. E. Pratovich, Bay View, Alaska, and L. C. Grove, of Kenai, Alaska. Letters have been sent these amateurs for particulars as regards their set.

Canadian 3HL advised that there were two amateurs in Prince Rupert and Canadian 4CB advised there were four. An attempt has been made to learn the power of these stations.

According to Mr. Maynard, these amateurs will only be allowed 50 meters wave length because they are on a route of navigation. The same probably holds true of all British Columbia coast stations. Those farther inland, however, are allowed from fifty to two hundred meters. There are about sixty licensed amateur stations in B. C. and with this number it will be, probably, possible to establish a relay route thru B. C., southward into the states, or, preferably, communication can be carried on with Seattle direct and the B. C. stations will have to be called upon only occasionally or else a route can be established eastward thru Canada.

Next month's report will probably contain more timely information as to these B. C. stations, as well as those in Alaska.

#### WEST GULF DIVISION

F. M. Corlett, Mgr.

Mr. Tilley, So. Tex. Dist. advises reports are rather meager on account of having hardly three nights to handle traffic during the month due to heavy QRN, but day-light work has been going on in his district with a rush and a surprising number of messages have been handled.

Austin is down to one station, 5ZU, so it falls to 5ZU to stand watch all hours of the day and regular schedules are maintained daily with 5XB, 5YI, 5YK, 5FA and 5KP and several others. Day-light work within 200 miles is comparatively easy.

The Texas University's station is nearing completion and will have a regular staff of operators who will stand watch each night from 7 to 11 p.m.

Mr. Sahn (5YK) at New Braunfels, Texas is making good.

A.D.S. Daniels, of Houston, reports conditions for reception and transmission for the past thirty days have been spasmodically good then bad, and most of the traffic moved into or out of Houston and vicinity has been done during day-light hours, with but few exceptions.

Earl Lester, 5NK, is our newest first class station and is doing some creditable work.



5ZW is doing some fine short distance work with his C.W. 5ZAA and 5CA are getting some interesting results with 110 A.C. on the plates of audiotrons and VT's.

D.S. Falconi, of the New Mexico District, states that atmospheric disturbances are slowly but surely isolating the southwest, though traffic has been going through. In an effort to make the handling of traffic during the summer possible, a C.W. set has been installed at 5ZA, and schedules are desired with other C.W. stations within easy range so that tests may be made. The power at 5ZA is 20 watts.

D.S. Dill of the Oklahoma District informs us that as far as League matters are concerned things look very well, but the chances of passing traffic through regularly do not look very encouraging. Traffic has been moving slowly at times, but impossible to work at all some evenings. Traffic can be handled with 5ZA on his C.W. set when his spark is unreadable through the static.

Several new stations have been found over the state this month.

Station 5RK of Norman, Oklahoma is now doing some good work, also 5JR at Enid is still working OK. 5CP of Oklahoma City is installing C.W.

H. P. Heafer, Dist. Supt., reports a complete reorganization plan in the Northern Texas Dist. Mr. John S. Dorsa, A.D.S., Dallas Territory, did not make a report. This is regrettable as there is some very good work being done in that Territory and no doubt has been reported by individuals. It is understood Dorsa has converted his aerial into a clothes line and his condenser tank into a wash tub; in short John is in the Laundry business now having purchased an interest in a local laundry. His report must have been lost in the wash. Huh?

In spite of the Laundry QRN, regular QRN and some O.W. QRM, there has been some relay work in the Dallas Territory and in Dallas proper some interesting de-

monstrations of radio telephony, including radio dances, radio lectures and radio concerts, Mr. Bennett Emerson, 5ZG, furnishing the transmitting set.

Central Territory briefly reports by Mr. Guy Neel, 5XJ, a number of new stations among them being Mr. William Clark, 5ZAF, Waco. This station will prove very valuable as a relay station.

Western Territory, J. M. Martin, A.D.S., reports several new stations going up in vicinity of Amarillo but very little relay being done due to heavy static. A few messages are getting thru.

#### ATLANTIC DIVISION

Chas. H. Stewart, Mgr.

##### *Report of Trunk Line Tests*

On the nights of May 23, 24 and 26, trunk line tests were conducted over the northern and southern routes of the Northern Section of this division. They were none too successful, due to the unfortunate conditions that prevailed. In the first place the short notice given to stations along the lines caught a number of them unprepared and it just happened that quite a few were at the time undergoing repairs and changes. This particularly existed in the case of the most essential stations. Furthermore, many others were temporarily closed on the account of owners taking examinations at colleges, etc. In addition to this, to make matters worse and preventing large gaps to be covered, the atmospheric conditions throughout both New Jersey and New York were reported very bad on the first two nights. Fortunately weather conditions improved the last night and this was a great help.

All the fellows took keen interest in each test and showed their true spirit by co-operating heartily. Several of the Boiled Owls stayed right with the test until it was impossible to hear the faintest sign of a signal from any station on the route. FB, and thanks for the way in which you all responded. The story of the tests is given for the benefit of those who were not on the job and missed a lot of fun. A complete copy of all logs has not been turned in, therefore some credit may be missing where it is due.

##### **New York to Philadelphia Test.**

It was originally planned to route this message via the northern route through 3XM, Princeton, N. J., but at the last minute advice was received that because of examinations held on the above dates they would be unable to work. This station, being the only one which can consistently work Philadelphia and New York, in not operating made a change necessary and therefore the southern route was selected. This had to be abandoned immediately as it developed some of the re-

liable stations were temporarily out of commission. Furthermore, the local conditions prevented communication from Long Island points to Atlantic City, N. J. Knowing that transmission on the 23rd was impossible, 2JU handed a message to 2ZL addressed to 3ZS for broadcasting notifying him of test being called off. This message was received by 3NB at 10:30 p.m. (few words missed but were copied by 3AAN who furnished same), QRN bad, poor signals and extreme QSS on all N. Y. City stations. Relayed this message to 3HJ, QSO good. 3HJ immediately relayed to 3ZS. Signals from 3ZS not audible at 3NB. At 10:58 3HJ handed reply to 3NB but it dropped dead there as the latter could not connect up with any 2nd district station. It was sent to 2GR the following evening and relayed from there to 2JU. May 24th: Signals of 3NB were coming in very good at 2JU and in view of this it was planned to try to work him direct which was done. Another message addressed to 3ZS was sent without breaks to 3NB at 11:08 p.m., who immediately relayed it to 3EH. 3EH started to give message to 3ZS but blew condenser and had to deliver message over the land telephone. May 26th: Message from 2JU to 3NB at 10:10 p.m. 3NB called 3HJ and started message at 10:16 but 3ZS who was standing by copied this message direct from 3NB. Reply sent from 3ZS to 3HJ at 10:20 who in turn sent it to 3NB at 10:24. 2JU standing by, copied message direct from 3HJ and gave final OK to 3NB at 10:25. Actual time consumed both ways 15 minutes. There was no slip in the handling of this message and credit is due all concerned. The time, which probably is no record must be considered very good.

##### **New York to Albany.**

May 26: This message together with one for Buffalo was sent by 2JU to 2GR at 10:38 p.m. 2GR had difficulty in raising stations between that point and Albany. Stations 2BB, 2DA, 2AR and 2BM could not be heard and delay existed on account of none of these stations answering 2GR. 2UA was on job and could have cleared 2GR but it would have done no material good as he would have had trouble working north. 2SZ, 2AWF and 2FG all copied message while being sent 2JU to 2GR but only 2SZ was able to get it complete, due to the others experiencing QSS and bad QRM. At 11 p.m. 2JU and 2SZ got in communication with each other and the latter OK'd for the msg. However, immediately upon copying message from 2JU to 2GR he relayed it to 2FG, which was at 10:42. For some unknown reason 2FG did not secure reply but the fact remains it reached Albany in 4 minutes.

##### **New York to Buffalo.**

On the nights of the 23rd and 24th very bad luck was experienced, due to the bad

conditions. The first night message was given by 2JU to 2DI who in turn relayed it to 2UA. 2UA could not clear it further as he could not get in communication with anyone north of him. 2BB was on the job and copied message direct from 2JU but he also being unable to work any one north, message as far as the reports so far indicate dropped dead there. About the same conditions existed the following night but 2GR had been added and message was started through him with 2DI standing by. It is possible that one or more of the up-state stations had copied direct from 2JU but logs received up to the present writing do not show this. The final night was a little more successful. This time, although the message never reached Buffalo, it did get to Utica. 2JU started to 2GR who could do nothing on account of no stations working north to Albany. 2SZ had copied the message direct from 2JU as did 8HP. 2SZ not knowing that 8HP had copied it, called him several times but conditions between these points were bad and he could not connect. In the meantime 8HP was calling his head off, trying to raise stations west to Buffalo. He got hold of 8MDG, sent message twice but had to give it up as the latter station could not get it. Then he got in communication with 8FE, but on account of bad conditions he could not get it. The last attempt was made with 8AGK, when he sent message four times but it was utterly impossible to push it through and it had to drop there. 8HP certainly deserves thanks for his courage and patience in trying to get that message through. If we had better weather conditions, without question the Buffalo message would have been delivered and reply received and it is to be regretted that the outcome was so unfortunate.

#### Reports

It is noticed that the coming of summer with its QRN has caused a slackening of interest in relay affairs with a marked decrease in messages handled.

Mr. Lester Spangenberg, 2ZM, one of the few remaining old-timers in this Division, has been forced to resign as D.S. for northern New Jersey and may possibly have to withdraw from the game. This is sadly regretted, as 2ZM is a true amateur, a wonderful asset to our organization, and very well liked by all fellow amateurs. Mr. Ted Ostman, 2OM of Ridgewood, N. J., has been appointed as the new D.S. Ted has all the best wishes of his many friends and will prove his worth as a capable representative.

That stations in New Jersey may easily know who their D.S. is, the territory previously allotted the two Supts. has been changed in a few places, so that all stations whose call letters began with the number

3 will come under the jurisdiction of Mr. Marcus Frye, 3NB, Vineland, and those whose calls begin with the number 2 will come under Mr. Ostman, 2OM, Ridgewood.

We have lost one of our most efficient stations in the suspension of license of J. K. Hewitt, 2RK of Brooklyn. This suspension has caused considerable comment and agitation in this vicinity and it is to be regretted that such a thing should fall upon one of our best stations.

The Second District Council is forming regulations and traffic rules. Without question it will be something long wanted and we will not have to look forward to next season with the conditions of last season in mind. An invitation is extended all radio clubs in the Second District to join the council at once in order to be represented.

Benzee Bros., D.S. for Western N. Y., report only 391 msgs. handled, somewhat of a decrease. Numerous spark stations are being converted to C.W., and with the new C.W. stations traffic will be kept moving thru the summer. City Manager Haire (8GI) of Rochester has been forced to resign account entering the commercial game. 8FE is now using C.W. and has done very good work with four VT-2's. J. J. Young, 8HJ of Elmira, has been appointed City Manager of that city, and reports traffic moving very nicely there.

Carl E. Trube, D.S., Hudson Valley, reports that section of the N.Y.C.-Buffalo route from Yonkers to Hudson in splendid working order. 2DN, 2BK, 2BB, 2DA, 2AR and 2BM are handling traffic consistently. 2OA, 2HJ, 2UA and 2DK make a fine outlet for New England traffic, and all are handling heavy business. Complete record of traffic is not available, but 2BK handled 209, giving an idea of the volume. Plans are under way for a branch route towards Binghamton and all stations wishing to be appointed official relayers thereon should communicate with Mr. Trube.

F. H. Myers, D.S., Capitol Dist., reports a great deal of interest in the formation of his newly-created district, with everyone working hard on the New York to Buffalo route. 2SZ is back after repairs; 2FG temporarily closed. E. M. Williams of 2SZ has been appointed C.M. for Troy and the following official relay stations appointed: E. Wirsing, 2AWF, Albany; Geo. Benas, 8HP, Utica.

Dr. E. A. Cyriax, D.S. for New York City, reports that altho his district contains more stations than any other in the country, it has few DX stations and practically all outbound traffic must be relayed to a suburban DX station. Until local QRM is reduced local DX men will not be able to do their share. It is hoped that the Council regulations will overcome this handicap. 2CI and 2IF have been appointed official relay stations. Will others wishing appoint-



ments please communicate with Dr. Cyriax? 2DI handled 51 msgs.; 2CT closed down but expects to be on again shortly.

F. A. Maher, D.S., Brooklyn, advises that in the enforced absence of 2RK the traffic ordinarily handled by him is being absorbed very nicely by the other DX stations. 2WB is back after a long absence and proves a big help. The following are also doing their share: 2BO, 2ARY, 2MM, 2MB, 2PF, 2OW, 2DO, and 2RM.

Ted Ostman has just been appointed D.S. of Northern N. J. and so has not had sufficient time to become acquainted with his position. Traffic reports show a slight decrease as expected. 2AXB handled 25 messages during three weeks in May; 2AFP 68 for the month; 2BOC 80, and 2OM 248. 2VA not very active account college exams. 2UE is changing from spark to C.W. 2AJF is doing splendid work with his C.W. and we would like to see him handle more traffic.

Marcus Frye, Jr., D.S., Southern N. J., reports the same slowing up in movement of traffic as other sections. For the first time in history this district has been in direct communication with Baltimore, and considerable traffic has now been handled. Altho the distance is short it has always been very difficult to work this city, due to peculiar local conditions. 3FB is under repairs. A series of tests between 3NB and 3XF has been carried on in effort to establish daytime communication but results have not been very satisfactory to date. 3BA reports 14 msgs., 3AAN 20, 3EH 20 and 3NB 54.

H. S. Collins, D.S., Long Island, reports a much-needed efficient station in that of 2BML, Riverhead, L. I. Without question this station will be of great assistance in clearing traffic between N.Y.C. vicinity and New England. 2BGR and 2AJW are doing very good work with their C.W. sets and clearing lots of traffic. 2JU handled 123 msgs. during the last month. 2ZL and 2EL are doing excellent work and have cleared more traffic than many others, altho the exact number is unknown. (2ZL-2EL: Hw abt a report?—T.M.)

B. P. Williams, D.S., Western Penna., reports traffic fallen off due to summer weather and static. On Branch Line 2 between Monaca and Uniontown not much traffic is being handled, altho large volumes are moving from Monaca to Erie. Regular summer work is being pursued by 8WY, 8HA, 8HY, 8JQ and 8RU. 8ZD, 8DV, 8VQ, 8PN and 8MT will be off duty, overhauling and rebuilding. Our newest station, 8RU, will take the place of 8ZD in Pittsburgh for the summer. Western Penna. is decidedly hilly and stations located on high ground find QRN much more terrific than in other parts of the country, handicapping them by comparison with other localities where operators are sticking at it regard-

less of the warm weather. There are a number of good stations north of New Castle in this district whose applications for places on Line 2 Mr. Williams would like to have.

In Central Penna., D.S. H. M. Walleze reports QRN fast shortening the working range but traffic passing fairly well. The trunk line east from Milton is taking shape. A new station at Shamokin, 3AJZ, has opened up and should be able to work Reading, who has a schedule with Allentown, from where traffic passes easily to New York and some to Philadelphia. As yet no one has been located to substitute for 8XE this summer.

Slackening in traffic work is noticed in Eastern Penna. District, in the report of Supt. S. W. Place. Mr. Ehrhardt reports things dull in his territory, with few new stations. 3WX's new station is almost finished and will be regularly QSO Reading and York. Mr. Place's station has been granted a license to operate on 375 m., call 3ZV, and a C.W. set is now under construction, which will help in moving traffic.

Geo. L. Deichmann, 3HG, the recently appointed D.S. for Eastern Maryland, reports he has been unable to collect much data for his report this month. 3HG has been forced to abandon his morning schedule with 3ALN, Washington, because of examinations, but Baltimore C.W. stations, including 3ER, 3OU, 3AC, 3GZ and 3CT have arranged to keep up the connection. 3OU and 3AC have blossomed forth as regular DX stations and 3EQ, 3CT, 3EM, 3AJD and WJ have come to the rescue of summer traffic with C.W. stations that show some promise of putting the sparks on the shelf as long as static continues so annoying. 3EM has likewise abandoned the spark for C.W. Baltimore, Washington and Hagerstown at a joint club meeting have arranged for a regular daylight schedule connecting them. Conditions between Baltimore and Phila. are suffering badly for lack of perfect connection during the summer towards Phila. and Wilmington. It is suggested that the Phila. C.W. stations that are doing exceptional work should make tests with those in Baltimore with a view of perfecting a reliable schedule.

In the Dist. of Columbia, Francis Baer, D. S., the C.W. stations of 3AAO and 3ABI have blossomed forth as real DX workers. 3AAO is using two U tubes as oscillators with an antenna current of 3.5 amps., and has for nearly two weeks kept a reliable nightly schedule with 4GL in Savannah at 10:30, with 2BML at 9, and lately with 3ER in Baltimore at 9:30 on Mondays, Wednesdays and Fridays, all using straight C.W. 3ABI has a schedule with 1TS at 9:30 p.m. 3XF has made several unsuccessful

(Concluded on page 62)

# Calls Heard



## HEARD DURING MAY. Unless Otherwise Specified.

### Instructions to reporters:

(1) Typewrite or neatly print the calls, "double-spaced," on a separate sheet of paper, running them across the sheet, not down a column, and writing on but one side of the paper.

(2) Arrange alphabetically thru each district, from 1 to 9, with no break between districts, using commas to separate items and putting parentheses around calls of stations also worked—all as per the lists below.

(3) The period covered by the report shall be from the first of one month to the first of the following month. All lists must be received by us by the 10th of the second month, for publication in the next following QST.

Heard at Sea by ex-92T from March 22 to April 7.  
At dock in New Orleans: 4CG, 4XC, 4YA, 5AF spk. & C.W., 5DA, 5EW, 5HO, 5IB, 5IF, 5JA, 5MY, 5NG, 5XA, 5XB, 5YH, 5ZA, 5ZR, 5ZX, 5AS, 5DZ, 5ML, 5ZL, 9CA, 9EL, 9GO, 9HI, 9KR, 9LQ, 9NQ, 9OE, 9OX, 9PS, 9UF, 9UT, 9XM, 9YA, 9ZB spk. & C.W., 9AAC, 9AAG, 9AFX, 9AIZ, 9ANV, 9AON, 9ARJ, 9ASN C.W., 9DSX, 9DGP, 9DIW, 200 miles southeast of South Pass (La.): 2RK, 4XC, 4YA, 5CA, 5EC, 5EG, 5IB, 5JD, 5LA, 5NC, 5XA, 5XB, 5YH, 5ZA, 5ZAA, 5DC, 5FK, 5SP, 5ARS, 5CA, 5EL, 5GJ, 5NQ, 5QO, 5WE, 5ZB C.W., 5AAC, 5AHO, 5AON, 5ARJ, 5XF-1 C.W., 350 miles southeast of South Pass: 1XM C.W., 1JAP, 3RK, 2ZL C.W., 4BP, 4DL, 4FD, 4AU, 5ZE, 5ZAB, 5DC, 5XK C.W., 5ZC, 5EL, 5MC, 5AOH, 5BY C.W., 300 miles southeast of Key West: 4DL, 4FD, 5ZAB, 700 miles southeast of Key West, off Puerta Plata, Haiti: 1XM C.W., 4DL.

### Heard Aboard KOGS, S. J. Mallory, Opr.

Jan. 21 (60 miles south New York): 1FI, 2AGS, 2AOG, 2AUJ, 2BGR, 2EL, 2IT, 2TK, 3EN, 3FG, Jan. 22, (200 miles south New York): 1XT, 2DA, 2DN, 2EL, 2HN, 2OA, 2PD, 2ZM, 3ACM, 3BG, 3BH, 3BZ, 3EH, 3EJ, 3HG, 3HJ, 3ND, 3PU, 3UC, 3YV, 4BY, 4JS, 4XE, 4ZD, 4ZL, 4JN, 4ZN, 4ZQ, 4F1 C.W., Jan. 23, (450 miles south New York): 1HAA, 2OA, 2RK, 3ND, 4BK, 4BY, 4FD, 4RP, 4XE, 4ZD, 4AWX, 4OX, Jan. 24, (700 miles south New York): 1IRJ, 2EL, 2NY, 2OA, 2RK, 2ZC, 3CC, 3DH, 3HJ, 3HX, 3KM, 3NF, 3VV, 4AG, 4BK, 4BY, 4CD, 5EA, 5YE, 5ACF, 5ARS, 5BO, 5HA, 5IK, 5ML, 5OI, 5SP, 5ZL, 5ZR, 5AEG, 5BY, 5EQ, 5FS, 5OX, 5UU, 5VZ, 5WE, 5YC, 5ZB, 5ZL, 5NSF C.W., Jan. 25, (off Miami): 2EL, 2OE, 2RK, 3EN, 3HJ, 3NB, 3NC, 4AT (daylite), 4BK, 4BY, 4CK, 5ER, 5JE, 5ZX, 5ANB, 5ZD, 5ZL, 5OX, 5ZB, Jan. 26, off Key West (QRN bad): 5LH, 5JE, Jan. 27, (200 miles west Key West QRN bad), 5LR, Jan. 28, (400 miles east Tampico): 5BR, 5HL, 5IS, 5KP, 5LR, 5XA, 5YH, 5ZK, 5AAC, 5AAG, 5AEG, 5AEY, 5AXJ, 5LR, 5MC, 5OE, 5YM, 5ZB, Jan. 29, (100 miles east Tampico): 5BC, 5LR, 5ZF, 5AAC, 5AEG, 5LR.

In port Tampico (Feb. 6th to Feb. 14th): 5DA, 5EJ, 5HL, 5HZ, 5JD, 5JE, 5LR, 5YH, 5ZC, 5ZG, 5ZT, 5ZU, 5ZW, 5ZX, 5LR, 5OE.

Feb. 15, (100 miles northeast Tampico): 4XC, 5EW, 5FA, 5HL, 5HZ, 5IF, 5IS, 5JE, 5JX, 5KP, 5LM, 5LR, 5MF, 5XA, 5XB, 5YH, 5YM, 5ZA, 5ZF, 5ZG, 5ZK, 5ZP, 5ZR, 5ZU, 5ZX, 5IG, 5AEG, 5EL, 5FU, 5HI, 5HN, 5LR, 5MC, 5OE, 5SZ, 5WE, 5ZZ, Feb. 16 (250 miles southwest South Pass): 2RK, 4XC, 5HL, 5HN, 5HV, 5HW, 5IS, 5JE, 5MF, 5YH, 5ZA, 5ZK, 5RADE, 5ZY, 5AAAF, 5EL, 5EQ, 5HI, 5HN, 5LR, 5NQ, 5OE, 5TV, 5ZL.

Feb. 17 (off Burrwood, La.): 1IRJ, 4AG, 4FE, 4XC, 5DA, 5EJ, 5JD, 5JE, 5LR, 5MF, 5XA, 5YH, 5ZA, 5ZP, 5HG, 5IK, 5XK C.W., 5ZA, 5ZY, 5AIX, 5EL, 5EQ, 5ET, 5HI, 5LR, 5MC, 5WE, 5XM, 5ZB, 5ZJ, 5ZQ.

In port Gulfport, Miss. (Feb. 18 to 22nd): 2RK, 3GO, 4AG, 4AU, 4BK, 4BY, 4CG, 4FD, 4XC, 5BM, 5CL, 5DG daylite), 5DL, 5DQ, 5EA, 5EK, 5ER, 5HL, 5HV, 5HW, 5IE, 5IS, 5JD, 5JE, 5JX, 5KP, 5LA, 5LR, 5MA, 5MF, 5OD, 5XA, 5XB, 5YE, 5YH, 5ZA, 5ZC, 5ZD, 5ZE, 5ZG, 5ZK, 5ZP, 5ZS, 5ZU, 5ZX, 5AKV, 5DC, 5KP, 5XE, 5XS, 5ZE, 5ZL fone and spk., 5ZY, 5ABD, 5AEG, 5AON, 5ASL, 5BW, 5BY, 5CZ, 5EL, 5EQ, 5FU, 5HI, 5HN, 5JN, 5LA, 5LC, 5LR, 5MC, 5OE, 5QO, 5UF, 5UK, 5UU, 5WT, 5XM, 5ZB, 5ZL, 5VM.

Feb. 24, (80 miles south New Orleans): 2EL, 2RK, 3AHK, 3GO, 4BK, 4BY, 4CG, 4EK, 4XC, 5DQ, 5ER, 5HL, 5HS, 5HW, 5JE, 5LR, 5XA, 5XB, 5YE, 5YH, 5ZA, 5ZC, 5ZK, 5ZP, 5ZR, 5ZU, 5AFS, 5AGK, 5CH, 5HG, 5ID, 5XE, 5ZA, 5ZE, 5ZL, 5ZR, 5ZY, 5AKH, 5DC, 5DU, 5EL, 5EQ, 5FU, 5HI, 5HN, 5JN, 5LA, 5LC, 5LR, 5MC, 5OE, 5UK, 5VZ, 5XM, 5ZN, 5ZQ, 5ZZ.

March 9, (50 miles south New Orleans): 4XC, 5DQ, 5HB, 5HN, 5HP, 5HV, 5HW, 5IB, 5JD, 5JE, 5LA, 5XA, 5YH, 5ZP, 5ZX, 5ZY, 5BW, 5EL, 5HN, 5LR.

March 10, (150 miles southwest South Pass): 2RK, 3GO, 4XC, 5IF, 5XA, 5ZF, 5ZP, 5TK, 5KP, 5VJ, 5ZL, 5ZR, 5ZY, 5ANV, 5BW, 5DIW, 5EL, 5ET, 5FG, 5FU, 5GN, 5GT, 5HI, 5JN, 5LF, 5LQ, 5LR, 5OX, 5VN, 5WE, 5XM, 5ZV.

March 12 to 21 (at Tampico) on two bulbs: 1IRJ, 2RK, 4XC, 5AO, 5DT, 5EW, 5FD, 5FL, 5HL, 5IB, 5IF, 5JA, 5JE, 5JI, 5LA, 5LR, 5MF, 5MX, 5MY, 5YH, 5ZA, 5ZAA, 5ZC, 5ZF, 5ZR, 5ZS, 5ZT, 5ZU, 5ER, 5IG, 5ON, 5ZR, 5AAC, 5AAW, 5AEG, 5DC, 5DIW, 5EL, 5FU, 5HI, 5HN, 5KO, 5LR, 5MA, 5MC, 5OE, 5OI, 5QO, 5YA, 5ZJ, 5ZY, 5GT fone, April 11 to 20 (in Tampico, but on crystal): 5HL, 5XI, 5ZAA, 5XI, 5ZY, 5AEG, 5MC.

### 1MO, HARTFORD, CONN.—All C.W.

1BV, 1CBJ, (1FQ), (1NAQ), 1QN, 1TBE, (1TS), 1QAJ, (1UN), 1YM, 2ADL, 2AJF, (2AJW), 2BFZ, 2BML, 2CT, 2PA, 2BB, 2DN, 2HI, 2UD, 2ZL, 2XAC, 2XK, 2XX, 3AJ, 3AAE, 3AAO, 3BC, 4GL, 8DE, 8IV, 8NQ, 8RQ, NSF, NMW, XBI, XF1.

### 1FBH, STAMFORD, CONN.—All C.W.

1CK, 1FZ, 1BQH, 2DR, 2RB, 2UD, 2QR, 2XX, 2ZL, 2ZM, 2AJF, 2AKO, 2AWL, 2BDU, 2BML, 8RM, 8XK, 8ZW, NSF, XK1, XK4, KVKA.

### 1VAV, BRIDGEPORT, CONN.

1AW, 1CK, 1CM, 1CZ, 1CAS, 1CBJ C.W., 1DR, 1DY, 1DAL, 1FY, 1FBG C.W., 1GM, 1JT, 1LBR, 1MK, 1NBA C.W. & fone, 1QN C.W., 1RV, 1SBZ, 1TS C.W., 1ZE, 2AEF, 2AFZ, 2AFT, 2AID, 2AJR, 2AJW C.W., 2ANJ, 2ARY, 2ASB, 2ASL, 2AWL fone & C.W., 2AXB, 2AYS, 2BK, 2BDU fone & C.W., 2BFF, 2BGR, 2BML C.W., 2BNF,

2BNU, 2BQH fone. 2BRC I.C.W., 2CY, 2DI, 2DK, 2EL, 2FS I.C.W. & fone. 2GR, 2HJ, 2HBF, 2IF, 2IQ, 2JU, 2MJ, 2OM, 2OW, 2RB fone. 2RM, 2TK, 2UA, 2UK, 2VA, 2YM, 2ZC, 3AS, 3ACS, 3CC, 3DG, 3FB, 3HJ, 3HX, 3IW, 3CU, 3PU, 3WX, 3XM, 3ZO, 8AGK.

### 11AA, SHARON, MASS. April-May.

2AF, 2AL, 2AWF, 2AX, 2AZ C.W., 2BG, 2BH, 2BM C.W., 2BML, 2BRI, 2BQ, 2BQW fone. 2BZ, 2CC, 2DI, 2DR, 2DZ, 2EL, 2FD C.W., 2GR, 2IL, 2OA, 2OM, 2QC, 2RE, 2RK, 2RW, 2SZ, 2UA, 2VV, 2WR, 2WU, 2XF C.W. & fone. 2XH C.W., 2XJ fone. 2XQ, 2XY, 3BZ, 3CC, 3EN, 3HJ, 3ND, 3OA, 3OU, 3PU, 3XM, 3AC, 3AD, 3AGK, 3AL, 3AMZ, 3AMM, 3ANO, 3ANT, 3AWX, 3BC, 3DA, 3DC, 3DD, 3DR, 3DV, 3FE, 3HV, 3HR, 3IP, 3JW C.W., 3JQ, 3MZ, 3QH, 3RU, 3RW, 3VQ, 3VW, 3XA, 3XE, 3YA, 3ZY, 3AAC, 3HR, 3HT, 3JN, 3KB, 3KF, 3ME, 3UH, 3XM, 3YB, 3ZN, 3ZL.

### 2DK, SCARSDALE, N. Y.

1BBL, 1BM, (1CBJ, C.W. & fone), 1CK, 1FBB, 1GBC, 1GM, 1HAA, 1HO, 1JAP, 1NBA fone, 1WR, 1ZE, (2AJW C.W.), 2AR, (2BGR), 2DA, (2EL), 2FG, 2OE, 3ACS, 3AHK, 3AVG, 3BG, 3CC, 3DV, 33FR, 3GO, 3GU, 3HX, 3OU, 3PU, 3AOT, 3APB, 3DY, 3FI C.W.

### 2BKJ, GRANTWOOD, N. J.—June 1-6.

1ZE, 1DAL, 1GBC, 1CCY, 2SZ, 3BO, 3CC, 3CK, 3EH, 3EZ, 3GX, 3HG, 3HJ, 3IW, 3IZ, 3JR, 3NB, 3OU, 3PU, 3VW, 3XM, 3ZO, 3ALT, 3BO, 3DY, 3HR, 3PL, 3RQ, 3TK, 3TT, 3WY, 3XK, 3XU, 3ZA, 3AGK, 3AKA, 3ANT, 3AYN.

### 3ABP, YORK, PA.—April 20-May 21.

1AW, 1DH C.W., 1DT C.W., 1GBT C.W., 1NBA C.W., 1RD, 1TS, spk. & C.W., 1XB C.W., 1XG, 1XV, 1XX, 2AJF C.W., 2EL, 2HJ, 2MBL C.W., 2RK, 2XF, 2XQ spk. & fone, 2XX, 2ZL, 2ZM spk. & C.W. vy qsa, 3AAE, 3AAB, (33ADB), 3ACS, (3ACY), (3AGT), 3AIC, (3BAH), 3BAK, 3CC C.W., (3DB), 3EN, 3EQ, 3GO, 3KZ, 3LP, 3NB, 3NC, 3NY, 3PB, 3PU, 3SJ, (3WX), 3XF, 3XM, 3YE, 3YK, 3YV, 3ZA, (3ZO) spk. C.W. & fone, 3ZS, 4CX, 4GX, 4ME C.W., 4XB fone, 4XC, 5PA, 5XA, 5XB, 5AGK, 5HJ, 5HP, 5KM C.W. & fone, 5KZ, 5LA, 5OF, 5PT, 5RQ C.W., 5UK C.W., 5XK C.W. & fone, 5XU C.W., 5ZL, 5ZR, 5ZW, 5ZG C.W., 5AAC, 5AJI, 5AL, 5BY C.W. & fone, 5DBT, 5HR C.W., 5JG, 5RN, 5XI C.W., 5ZG, 5ZJ, 5ZL, 5ZN, 5KDK fone, 5NF C.W. & fone, 5WX, 5NMW C.W., 5KQG fone, 5WV C.W., 5XT, Canadian 3BP, 3EL.

### 3AOV, STONEGA, VA.

4AG, 4AL, 4BT, 4CK, (4DA), 5EK, 8AAS, 8AKS, 8AK, 8BM, 8BO, 8DI, 8EC, 8ID, 8LW, 8OJ, 9AAZ, 9AAC, 9ANV, 9AJT, 9APS, 9AZT, 9LQ, 9SH, 9UC, (9UH), 9UZ.

### 3ALR, WASHINGTON, D. C.

1AW, 1MAD, 2EL, 2JU, 2KL C.W., 2OM, 2RK, 2RM, 3BP, 3CC C.W. & spk., 3EH, 3EQ C.W., 3HG, 3HJ, 3IC, 3NB, 3PU, 3XM, 4GL, 4YA, 5ZA, 5AM, 5AIO, 5HR, 5JM, 5PU, 5RQ C.W. & spk., 5XK C.W., 5XM, 5ZA, 5ZR, 5UH, 5UU, 5ZN, 5FI.

### 3EZ, PORTSMOUTH, VA.—May 8-June 8.

1AW, 1BA, 1CZ, 1GM, 1JAP, 1ZE, (2ACD), (2AFJ), 2AHK, (2ARD), (2ARY), (2EL), 2ERN, 2GM, 2KL C.W., (2JU), 2OM, 2TS, 2UK, (2WB), 2XK C.W., 2XM, 3AD, 3AL, 3BG, 3BP, 3BZ C.W., 3CC, (3EH), 3EL, 3EQ, (3FBS), 3FJ, 3HB, 3HG, (3HJ), (3HX), (3IW), 3IX, 3JX, (3KM), (3LP), (3NB), 3NX, (3OU), (3PU), (3QN), 3RQ, 3RX, 3UK, (3WX), (3XF), 3YK, (3YH), 3ZA, 3ZO, (4BY), (4GN), 5AEE, 5AFA, 5AGK, 5AGO, 2AJT, 5AMQ, 5ANW, 5BO, 5BK, 5CI C.W., 5DE C.W., 5DP, 5HJ C.W., 5HR, 5LK C.W., 5OI, (5RQ), 5TK, 5TT, (5TY), 5WA, 5WR C.W., 5WY, 5XA, 5XM C.W., 5XK fone, 5YN, 5ZG C.W., 5AAW, 5AGV, 5ANC, 5ANV, 5FS, 5ME, 5PC, 5UH.

### 5ZU, AUSTIN, TEXAS.

(4XC), 4GL C.W., 4YA, 5AG, 5EA, 5EF, (5EK), 5BR, (5CC), (5FA), (5FB), (5HE), 5HF, (5HL), 5HH, 5HB, 5IP, 5IF, 5IB, (5JE), 5JD, (5JS), 5KB, 5KV, 5LR, 5LM, 5LP, 5MF, (5MG), 5MX, (5NK), (5OR), 5RH, 5WI, (5XB), (5XI), (5YE), (5YH), 5YI, 5YM, (5YK), (5ZA spk. & C.W.), 5ZD, (5ZP), (5ZR), (5ZX), (5XAB), (5ZC), 5ZS, (5ZF), (5ZW), (5ZE), (5ZL), (5ZAA), (5ZAE), (5ZAF), (5ZZ), 6ZL, 8YN, 8ZZ, 8ZY, 9AEG, 9AAC, 9AEY, 9AIZ, (9ALG), 9ARF, 9ANV, 9ANP, 9AR, 9ACJ, 9AUS, 9ANF, 9BW, 9DW, 9DL, (9EL), 9EQ, 9EK, (9HI), 9IY, (9JN), 9JA, 9JM, 9JC, 9KW, 9KV, (9LR), 9LA, 9LI, 9LQ, 9LC C.W., 9MC, (9OE), 9ON, 9PS, 9QO, 9SZ, 9TL, 9UH, (9WI), 9WW, 9XY, 9XAE, 9XM, 9XI, 9YM spk. & C.W., 9YI, 9YA, 9ZJ, 9ZL, 9ZN, 9ZQ, 9ZA, 9ZB, (9ZH), 9ZR, 9ZV, 9ZAB.

### 5FO, NORMAN, OKLA.

9OE, 5NK, 5LC, 5JI, 5ZK, 5OH, 5ZS, 5HQ, 5XI, 9DE, 5NW, 5QA, 5HX, 5ZA, 5DW, 5LK, 5JR, 5HZ, 9AE, 5AR.

### 5YK, NEW BRAUNFELS, TEXAS.

4XB C.W., 5XD, (5XB spk. & C.W.), (5XI), 5YE, 5YH, (5YI), 5YL, (5ZA spk. & C.W.), 5ZC, 5ZD, 5ZE spk. & C.W., 5ZF, 5ZX, 5ZL, 5ZN, 5ZP, (5ZR), (5ZU), 5ZV, 5ZW, 5ZX, 5ZZ spk. & C.W., 5ZAA C.W., 5ZAB, (5ZAE), (5ZAF), (5ZAG), 6ZZ, 9BY C.W. & fone, 9YI, 9ZC, 9ZU, 9ZJ, 9ZO, 9ZA, (9ZD), (9ZK), (9ZM), 9W4 C.W., (AG5), 9A6 C.W. Specials only, including army stations; others too numerous.

### 5KP, ELGIN, TEXAS.

2ZL, 4AG, 4YA, 5AG, 5BV, 5BM, 5CC, 5CL, 5DA, 5DB, 5DW, 5EF, 5EJ, 5EW, 5FL, 5HF, 5HV, 5IF, 5IS, 5JA, 5JS, 5KA, 5LK, 5LM, 5LR, 5MG, 5XA, 5XB, spk. and C.W., 5YE, 5YI, 5ZF, 5ZK, 5ZL, 5ZS, 5ZU, 5ZW, 5ZZ, 5ZAE, 5ZAF, 6GF, 7KX, 7YA, 8KP, 8YG C.W., 8ZG C.W., 9BW C.W., 9EL, 9FF, 9FK, 9FU, 9HN, 9HM, 9HN, 9HT, 9OR, 9OE, 9QU, 9WI, 9XM C.W., 9ZAC, 9ZN.

### 6ZT, SALT LAKE CITY.

5IF, 5ZA, 5ZZ, 6AE, 6AH, 6AK, 6AN, 6AW, 6BJ, 6BQ, 6BR, 6CO, 6CV, 6DH, 6DK, 6DP, 6EA, 6EB, 6EJ, 6EN, 6ER, 6FE, 6FH, 6FI, 6GY, 6HT, 6IC, 6IF, 6IG, 6JN, 6JR, 6JF, 6KA, 6KL, 6KM, 6KR, 6LC, 6MK, 6OH, 6PJ, 6PR, 6PY, 6QJ, 6QR, 6QY, 6RE, 6UM, 6VS, 6WV, 6XZ, 6ZE, 6ZH, 6ZK, 6ZN, 6ZO, 6ZR, 6ZS, 6ZU, 6ZY, 6ZY, 6ZB, 6AAH, 6AAT, 6AAK, 6AAW, 6ACA, 6ACR, 6AFX, 6AFY, 6BAB, 6BAC, 6XAD, 7BH, 7BF, 7BR, 7BV, 7CC, 7CW, 7CU, 7DA, 7DS, 7EX, 7FL, 7GQ, 7IM, 7IN, 7JX, 7YA, 7YS, 7XB, 7ZB, 7ZG, 7ZJ, 7ZQ, 7ZK, 8XK, 9EL, 9HT, 9LR, 9LW, 9OE, 9PS, 9YW, 9AFX, 9AMB, 9AVU.

### 6AUB, SAN DIEGO, CAL.

5ZA C.W. & spk., 6AE, 6AK, 6AQ, 6DP, 6ED, 6EN, 6ER, 6GE, 6HI, 6IF, 6IL, 6JM, 6KA, 6KM, 6LC, 6MK, 6OC, 6OH, 6OW, 6RN, 6SK, 6UM, 6ZA, 6ZH, 6ZK, 6ZN, 6ZR, 6ZU, 6ZX, 6ZZ, 6AAK, 6ABP, 6ACY, 6ADX, 6AIL, 6XAD C.W.

### THACHER SCHOOL, OJAI, CAL.

6AAG, 6AAK, 6ACY, 6ADA, 6ADL, 6AGC, 6AGF, 6AGL, 6AHQ, 6AJE, 6AK, 6ALE, 6APH, 6AAU, 6ARG, 6BF, 6BG, 6DP, 6DS, 6EB, 6EC, 6EN, 6ER, 6EX, 6FH, 6FI, 6GP, 6IM, 6IY C.W., 6JN, 6KL, 6KM, 6KW, 6LW, 6NG, 6NY, 6OL, 6PO, 6PR, 6TF, 6ZK, 6ZN, 6ZU, 6ZX, 6TC.

### 7DA, PORTLAND, ORE.—April 15 to May 15.

(Canadian 5BA), (Canadian 5CJ), (6AH), 6AK, (6CH), (6CP), 6DD, (6DP), 6ED, 6EN, 6EP, (6EX), (6FH), 6GF, (6HC), (6HP), (6IC), (6KA), (6KL), (6LC), (6OC), (6OH), (6OW), 6PR, (6QR), 6SK, (6SR), 6TA, (6TC), 6TV, 6VM, (6WZ), (6ZR), (6ZU), 6ZX, 6AAP, 6AAU, 6AAW, 6ABM, (6ABX), 6ACA, 6ACI, 6ACM, (6ACR), 6AFN, 6AFY, (6AGF), 6AIT, (6AIW), (6ANK), (6APH), (6ZAA), (7AD), (7BA), (7BC), (7BH), (7BK), (7BQ), (7BV), 7CA, (7CE), 7CN, (7CW), 7EO, (7FI), (7FQ), (7ID), (7IY), (7KM).

7KQ. (7D). (7NL). (7NN). (7OF). 7PV. 7YS. (7YA). (7ZG). 7ZH. (7ZM).

**7ZG. BEAR CREEK, MONT.—During April.**  
2RK. 2ZL. 3HK. 5IF. 5ZA. 6AEZ. 6JT. 6KA. 6LC. 6NQ. 6OT. 6VS. (6WV). 6ZA. 6ZH. 6ZU. 6ZZ. 7AD. 7BQ. 7CU. (7DA). (7DH). (7EX). (7FI). 7FL. 7FQ. 7GK. (7IM). (7JW). 7LN. (7LU). (7LY). 7MB. 7MC. 7MP. 7NN. 7NL. 1XB. (7XD). (7YA). 7YG. (7ZM). (7ZO). 9ABU. 9AEG. 9AEY. 9AFX. 9AGN. (9AIF). 9ALG. 9ALC. 9ALU. 9ANF. 9AOM. 9AQE. 9ARJ. 9ASF. 9ATN. 9ATO. 9AUO. 9AVZ. 9AWX. 9AXU. (9AYE). 9AWY. 9DAT. 9DHA. 9DKS. 9DMB. 9EE. 9ED. 9EQ. 9HI. 9HT. 9IY. (9JN). 9LW. 9MC. (9NR). (9OE). 9OO. 9PI. 9PN. 9PS. 9QO. 9RG. 9SZ. 9UR. (9WI). 9TI. 9XI. 9YY. (9XM). (9YW). 9ZAC. (9ZC). 9ZU.

This is the biggest list for the past month and shows the good work done at 7ZG. This was all done on a home made set and a one step amplifier.

**7BK. SEATTLE.—April 15-May 15.**  
Canadian 5BA. 5CP. 6AK. 6CH. 6DD. (6DP). 6DY. 6EX. (6FH). (6HC). 6IY. 6KK. 6KL. 6KM. 6LC. (6OC). 6OH. 6OW. 6PR. (6QR). (6TC). 6TM. (6TV). 6VM. (6VK). 6WD. 6AAN. 6AAU. 6AAW. 6ABM. 6ABX. (6ACR). 6ADH. 6AFV. (6AGF). 6AID. (6AIW). 6AJE. 6ALA. 6ANK. 6APH. 6ZA. 6ZH. 6ZN. 6ZR. 6ZU. 6ZX. 6ZAA. (7BH). 7BQ. 7BV. (7CU). (7CW). (7DA). (7ED). (7FI). 7FQ. 7GA. 7GP. 7HF. 7HN. 7IN. 7JN. (7JW). (7KB). 7KJ. (7LS). (7MH). 7MY. 7NL. (7NN). 7YA. 7YG. (7YS). 7ZG. 7ZL. (7ZJ). 7ZK. 7ZM.

**8ANW. NILES, OHIO.**  
1AW. 1HAA. 1OE. 1RAY. 3RK. 2QR. 2ZL. 3XM. 4CC. 4CK. 5DA. (8AAV). 8ADJ. 8AIO. (8AKJ). 8ALY. (8AEJ). 8AGZ. (8AMF). 8ANK. (8ARW). 8AXC. 8AWX. 8AYN. (8BDP). 8BK. 8BO. 8CD. 8CH. 8DE. (8GW). 8HA. (8HB). 8JM. 8JU. 8NQ. 8OI. 8PT. 8TT. 8XE. 8ZA. 8ZB. 8ZR. 8ZW. 8ZX. 9AAW. 9AL. 9DV. 9HN. 9LA. 9LQ. 9TI. 9WU. 9XM. 9ZJ. 9ZL. 9ZN. 9ZQ.

**8AUG. CLEVELAND, O.—April 15-May 15.**  
1AW. 1XM. 2ANL. 2BML. 2BK. 2DR. 2EL. 2FG. 2JU. 2OM. 2UK. 3AWV. 3CC. 3EL. 3EN. 3KM. 3NB. 3OU. 3PU. 3RW. 3WM. 3XF. 3XM. 4AG. 4BC. 5JD. 5ZL. 8AAV. 8ABG. 8ABZ. 8ACX. 8AGK. 8AGO. 8ANK. 8ARK. 8ATE. 8AWX. 8AA. 8AW. 8DE. 8EN. 8FE. 8KZ. 8QE. 8RQ. 8SP. 8TY. 8UI. 8WY. 8XE. 8YN. 8ZD. 8ZY. 9AAW. 9AWZ. 9JA. 9JN. 9JQ. (9LQ). 9ME. 9NW. 9PC. 9UK. 9UJ. 9UU. 9WM. 9WN. 9WO. 9ZN. NSF. WWV.

**8AGZ. E. CLEVELAND, O.—C.W. Only.**  
1DH. 1QR. (1TS). 1XX. 2CC. 2XA. (2ZL). 2ZM. 2XQ. 2BML. (3CT). 3PU. 3AAE. 3AAO. 4GL. 4XB concert. 5BA. 8BO. 8CF. (8DE). 8GA. 8GE. 8HA. (8IB). 8II. (8IV). 8JJ. (8JM). 8JU. (8KM). 8TF. 8LV. (8OF). (8PJ). (8QY). 8NI. 8RK. (8VS). 8XB concert. 8XK. 8XM. (8YG). 8ZL voice. (8ZG). (8ZN) voice. (8ZY). (8ZZ). 8ABO. 8ALN. 8AMM. 8ANK. 8ARU. (8ASM). 8AYO voice. (8TZV). 9XB. (9XI). (9XM concert). 9ZY. 9AZX.

**8PU. ERIE, PA.—April 21-May 21.**  
1AW. 1CK. 1TS. 1TY. 1XE. 1DAP. 1GBC. 1QR. C.W. 1RAT. 2EL. 2HI. C.W. 2JU. 2RK. 2UK. 2ZL. C.W. 2BML. C.W. 3BG. 3BR. 3CA. (3CC). 3DN. 3EN. 3HJ. 3HR. 3XM. 3AWV. 4AG. 4CK. 5DA. 8BO. 8CG. 8CP. 8DE. C.W. 8DP. 8FE. 8FI. 8HG. (8HJ). (8KK). (8LM). 8LV. 8ML. 8MM. 8NB. 8NQ. 8NZ. 8OI. 8RM. 8RQ. 8SG. (8SP). 8TO. (8TY). 8UY. (8VH). 8WI. (8WY). 8WZ. 8XK. 8AAP. 8AAV. 8AAW. 8ABM. (8ACA). 8APG. 8AGK. 8AGU. (8AHE). 8AHG. 8AIA. (8AIS). 8AKV. 8AMZ. 8ANJ. (8AOT). 8APH. 8AQD. (8AQL). 8AQV. 8ARW. 2ASJ. 8ATW. 8AUB. 8AWX. (8AYM). 8UH. 9UU. 9ZJ. 9ZN. 9AAW. 9AHJ. 9ACM. 9ALS. 9DAX. Canadian 3AB. 3BP. 3DS. 3GL. 3GO. 3LI. 3MO.

**8AOY. LANCASTER, N. Y.**  
1AW. 1CK. 1CZ. 1GBT. 1GM. 1HTF. 1NBA. C.W. 1YR. 2BM. C.W. 2EL. 2XA. 3AII. 3AVG. 3CC. 3HJ. 3NB. 3PU. Canadian 3BA. 3KS. 3LD. 3MO. 8BV.

8CG. 8DA. 8FE. 8FC. 8HA. C.W. 8HJ. 8IL. 8KU. 8KZ. 8LB. 8MZ. 8PJ. 8SP. 8UF. 8WO. 8ZR. 8ADR. 8AGK. 8AHQ. 8AHS. 8AHV. 8AJR. 8AKX. 8AMB. 8AMM. 8AMZ. 8AMQ. 8ANJ. 8ANT. 8AOB. 8APB. 8APJ. 8ARW. 8AVD. 8AVE. 8AYT. 8BBK. 8BDH. 8BEU. 8FQ.

**C. Gartlein and K. White, Florence Hall, Greencastle, Ind., April 1-May 8, Galena.**

1XM. 5EK. 5FD. 5HL. 5IB. 5JD. 5YH. 5YS. 5ZD. 5ZL. 8CD. 9DZ. 8ML. 8YN. 8AGK. 8ARS. 9AV. 9EG. 9GW. 9HI. 9HN. 9HR. 9JA. 9JQ. 9KO. 9KP. 9KR. 9KX. 9LF. 9LQ. 9MC. (QSA). 9NH. 9NW. 9OB. 9OE. 9US. 9QO. 9SC. 9UJ. 9UK. 9UU. (QSA). 9WE. 9YA. 9YB. 9YI. 9ZJ. 9ZN. 9ZS. 9AAV. 9AAW. 9ABL. 9ACN. 9AEG. 9AGR. 9AJK. 9ALV. 9AMK. 9ANV. 9ARJ. 9AWX. 5YE. 5YL. 5ZU. 5ZX. 8ASY. 8LU. 8TK. 9AFK. 9CF. 9VC. 9WC.

**C. F. BURDICK, CASPER, WYOMING, April.**

5HL. 5IB. 5IF. 5JD. 5JL. 5MX. 5ZA. apk. & C.W. 6AEG. 6AEZ. 6AJX. 6DZ. 6JT. 6OT. 6VS. 6ZA. 6ZB. 6ZG. 6ZH. 6ZX. 6ZZ. 7DH. 7FL. 7LU. 7LY. 7MO. 7XD. 7ZG. 7ZM. 7ZO. 8ASB. C.W. 9AAW. 9ACN. 9AEG. 9AEY. 9AG. C.W. 9AGL. 9AGN. 9AIF. 9ALG. 9ALO. 9ANF. 9ANV. 9ARJ. 9ASF. 9ATN. 9AUO. 9UU. 9AV. 9AVS. 9AWG. 9AXU. 9BT. 9EE. 9EL. 9FX. 9HI. 9HT. 9IF. 9JA. 9JN. 9JQ. 9KA. 9LLW. 9MC. 9NQ. 9OE. 9OO. 9PS. 9QO. 9SC. 9SZ. 9TI. 9UG. 9VE. 9WI. 9XAE. 9ZAA. 9ZAC.

**Don't forget to send in your Calls Heard during the Summer months—they mean even more than in Winter.**

## MAY STATION REPORTS

### 4GN, Midville, Ga.

| Steadiest   | Loudest     |
|-------------|-------------|
| 1AW—1XF     | 1AW—1XF—1BZ |
| 2RK—2EL     | 2EL—2RK—2DM |
| 3EN—3GO—3YK | 3GO—3XM—3EN |
| 4XC—4CK—4BY | 4YA—4CK—4DT |
| 5YH—5ZS—5ER | 5XA—5YH—5DA |
| 8SP—8ZL—8YN | 8SP—8ZR—8YN |
| 9ZJ—9UK—9UH | 9MC—9UK—9YC |

### 4XC, Atlanta

| Steadiest    | Loudest      |
|--------------|--------------|
| 1AW—1XM      | 1AW—1XM      |
| 2RK—2EL—2SZ  | 2EL—2RK—2SZ  |
| 3GO—3HJ—3XF  | 3DH—3GO—3HJ  |
| 4FD—4GN—4BY  | 4BY—4FD—4GN  |
| 5ZL—5ZAB—5YH | 5ZAB—5YL—5DA |
| 8SP—8ARS—8ID | 8ARS—8ID—8SP |
| 9ZJ—9LQ—9UH  | 9MC—9ZJ—9LQ  |

### 4DT, La Grange, Ga.

| Steadiest   | Loudest     |
|-------------|-------------|
| 3VV         | 3VV         |
| 4GN—4FD—4AM | 4GN—4FD—4AM |
| 5YH—5DA     | 5DA—5IB     |
| 8SP—8CF     | 8SP         |
| 9AKC—9ME    | 9AKC—9UU    |

### 5HL, Oklahoma City, Okla.

| Steadiest    | Loudest      |
|--------------|--------------|
| 4XC—4YA—4AU  | 4YA—4XC—4AU  |
| 5ZX—5ZU—5ZAA | 5ZAA—5ZX—5ZU |
| 6ZZ          | 6ZZ          |
| 8ZY—8YQ—8ZN  | 8YQ—8ZY—8ZN  |
| 9QO—9AP—9MC  | 9OE—9AEG—9QO |

### 5XA, Auburn, Ala.

| Steadiest   | Loudest     |
|-------------|-------------|
| None        | 2EL—2ZM     |
| 3GO—3HG     | 3GO—3HG—3ND |
| 4GN—4FD—4YA | 4BY—4GL—4YA |
| 5EK—5FA—5YH | 5FA—5YH—5IB |
| 8VS—8OI—8BO | 8BO—8ZR—8ZA |
| 9OE—9ZB—9MC | 9MC—9YC—9FU |

(Concluded on page 62)



# Who's Who in AMATEUR WIRELESS



## MR. O. PSZAW

needs no introduction to our readers. He is a member of every radio club and operates many stations—when he can stay awake.

At club meetings he sits in the back row, says nothing, looks unhappy, and leaves without mixing with the gang. He always votes "aye" unless it is a rising vote which takes too much effort.

Mr. Pshaw will get his rotary gap finished about a week from some Sunday. In the meantime he uses a fixed gap. He will borrow the club's wave meter and ammeter to tune up when he gets the gap done but for the present gets along with any old antenna current.

Mr. Pshaw prefers to be called on full power as there is something wrong with his tuner. He has been wanting to repair



## MR. JAY WATTBURNER

is familiar to all of us because of his theory of radio transmission. Mr. Wattburner discards clear tone, sharp tuning and clean sending as pure bunk, stating that the ether has a limited capacity, hence if signals are fed into it long enough some of them will finally drip out at 9ZN.


For years Mr. Wattburner's organization, the National Union of Tireless Senders, has attempted to saturate the ether in this way.

Their tests are disguised as calls for an imaginary station named "CQ." At present the N.U.T.S. have no station call, each man using his own call.

Why not assign them "ADF" and make each man use it?

it but doesn't seem to get the time.

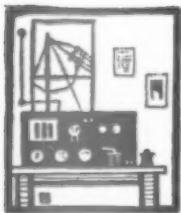
Some day someone will kill Mr. Pshaw, assuming that it is possible to kill a dead one.



# Amateur Radio Stations



*1XM, Cambridge, Mass.*

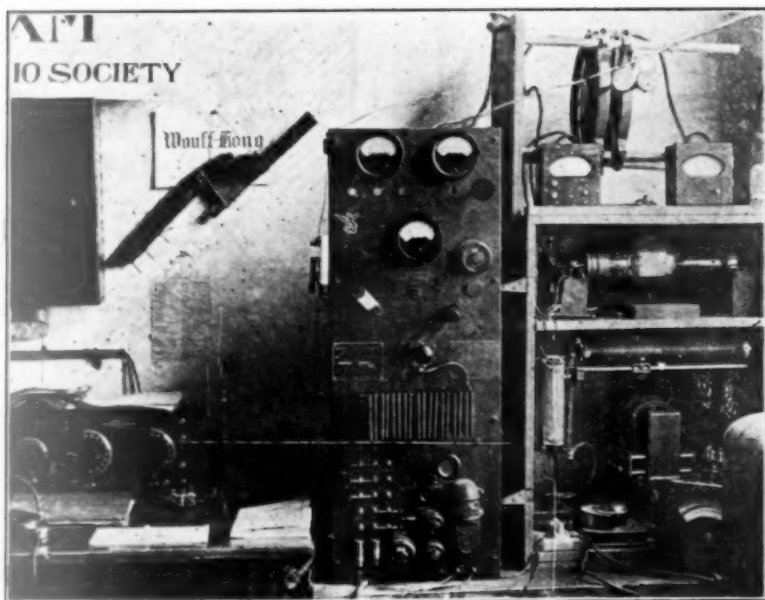

Since 1XM, the station of the Massachusetts Institute of Technology Radio Society, Cambridge, Mass., is now being heard in six districts, some description of the station and the development work now going on may be of interest to fellow members of the A.R.R.L.


The M. I. T. Radio Society was started in 1913 in the old Tech buildings in Boston, with the call 1LC. Since the war the Society was reorganized, affiliated with the A.R.R.L., and a new station equipped in a location on Technology's Cambridge site, handy to the Institute's power house, the aerial being anchored to the top of the 200 foot chimney. The Society now has 175 members, fifty of them commercial operators who stand watches at the station with amateur operators as assistants. Men prominent in the radio field have been secured to speak at the monthly meetings and a banquet is held each year with invitations extended to all the radio amateurs in New England. The present officers

are: Henry R. Kurth of Cambridge, Mass., president; Carole A. Clarke of New City, vice-president, in charge of station; Fullerton D. Webster of Everett, Mass., secretary; Alfred E. Shaw of Parkston, S. D., treasurer; Edmond Bruce of Washington, D. C., chairman, station committee. According to an agreement with Technology's department of Electrical Engineering, the M. I. T. Radio Society is now a part of that department's division of research. The arrangement is such that the undergraduates still retain complete control of the station, which is to be kept in operating condition for the courses in radio communication and engineering, while the department acts in an advisory capacity.

1XM's antenna system consists of an aerial rising at a 45 degree angle with the horizontal, and a counterpoise so designed as to place the anti-node directly in the transmitter inductances. The counterpoise is placed 25 feet above the earth to minimize the ground losses resulting from a

fairly conductive soil. The dimensions are as follows: length of aerial from transmitter, 105 feet, consisting of 4 wires spaced  $2\frac{1}{2}$  feet; counterpoise, 6 wires spaced  $6\frac{1}{2}$  feet. The leads are brought through panels of insulating material fastened in the window, and on which the

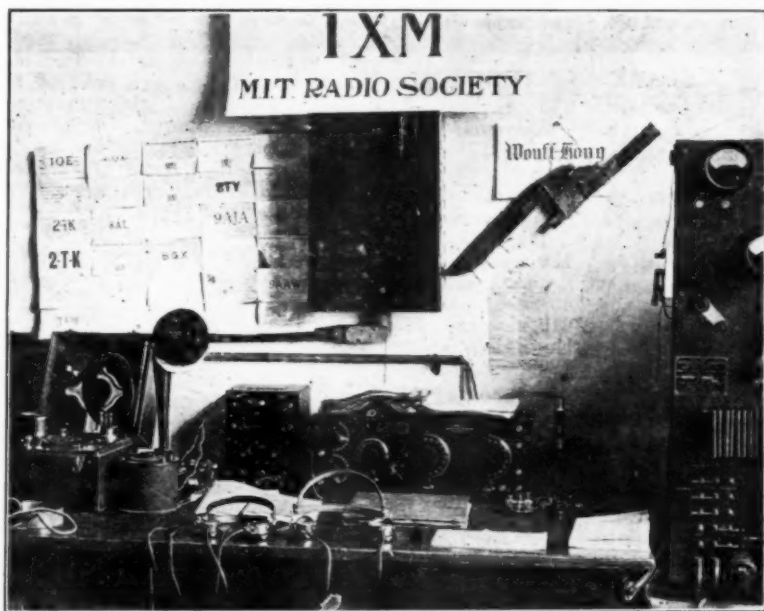
put to the tubes is 380 watts. Due to the limitations of the present 500 cycle generator it is necessary to run them far under their rated capacity. All three condensers are .002 mfd. capacity. A 7000 ohm grid leak is used with best success. A specially built Acme 500 cycle transformer furnishes



lightning switches are mounted. A system of antenna and counterpoise bus bars has been erected around the station so any of the sets may be connected by merely snapping test clips on the busses. Similarly a copper strip ground bus, used for receiving, runs under the operating tables. For "A" battery connections a distribution system is used so that the batteries may be kept near the motor generator and charging panel. Battery connections are made to a distributing panel from which numbered lines run to Fahnestock clips placed at convenient spots on the operating tables. The battery equipment consists of four 4-volt and two 10-volt Edison cells, and three 6-volt lead cells. Other power for operating is obtained from a 110/220 volt direct current line, a 220 volt 3 phase, and 110 volt single phase, 60 cycle a.c. mains, 110 volt D. C. motor generator supply, and a 500 cycle motor generator.

The circuit of the newest C.W. transmitter, now in use for DX work, is given herewith. 1200 volts, 500 cycles, is used on the plates of 2 Type P 250-watt General Electric Plotrons, with a plate current of 0.25 amperes. The filaments draw 3.6 amperes each from a 60 cycle 30 volt filament lighting transformer. The total in-

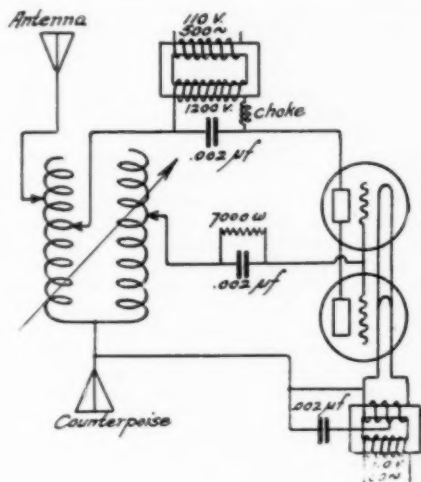the plate voltage. Signalling is accomplished by breaking the transformer input. The inductances are two pancake coils, each one foot in diameter, wound with  $\frac{1}{2}$ " copper ribbon, and have 19 turns each. Thirteen turns are used in the antenna



circuit, eight for the plate, and ten for the grid circuit, with two inches between the coils. All adjustments are extremely critical.

A comparison of the performance of the C.W. and the Wireless Specialty 200-watt 500-cycle quenched spark set operating under identical conditions on the same antenna system is submitted. The same generator is used for both sets.

|                        | SPARK                    | TUBES                         |
|------------------------|--------------------------|-------------------------------|
| Input                  | 300 watts,<br>500 cycles | 380 watts,<br>500 cycles      |
| Output in Antenna      | 93 watts                 | 186 watts                     |
| Transf. Core Loss      | 21 watts                 | 78 watts (designed for 1 kw.) |
| Transf. Voltage        | 8000 volts               | 1200 volts (with drop)        |
| Efficiency             | 31%                      | 49%                           |
| Wave Length            | 199 meters               | 210 meters                    |
| Decrement              | 0.09                     | Negligible                    |
| Consistent Night Range | 250 miles                | 1800 miles                    |

The constants of the antenna and counterpoise are as follows: capacity, 0.00054 mfd., total resistance, 10.5 ohms; natural period, 140 meters.

The contrast between the two sets is very marked in this data. However, the spark set is doing splendid work and oper-

ating very efficiently considering the input power.

In addition to the two transmitters just compared, the Society has a 1 kw. 60-cycle 3-phase Amrad quenched spark transmitter, giving the equivalent of a 180 cycle note; also a Signal Corps SCR-67 box type radiotelephone receiver and transmitter which is used for local work and concerts. This is buzzer modulated for handling local traffic. A Kolster decremeter and several wavemeters are part of the equipment, the services of which may be obtained by neighboring amateurs upon request.

The receiving apparatus consists of a Paragon RA-10, Grebe CR-2, and Clapp-Eastham ZRF regenerative receivers, Armstrong auto-heterodyne receiver, three two-stage amplifiers, numerous Brandes, Western Electric, and Baldwin phones, and Western Electric and Magnavox loud speakers. A set of deForest honeycomb coils brings in the European stations and a deForest jeweler's time set with two-stage amplifier is connected to a telephone line and regulates the Institute's master clock. A loop is used for direction finding.

1XM is open for traffic regularly from 9 p.m. to 6 a.m. Tuesday, Thursday, and Saturday. On other nights a watch is usually kept from 8 p.m. to midnight. A first grade commercial operator is in charge at all times. The division of time as

(Concluded on page 61)

## 5XA, Auburn, Ala.

The noise-maker of the south, Alabama Polytechnic Institute, Auburn, Ala., is here portrayed.

5XA has a peach of a mast, 140 ft. high, of steel pipe, and two aerials, one a 4-wire stretching away for 550 ft. to a 120-ft. tank, and the other a 7-wire nearly vertical one, 130 ft. long, on which the short-wave work is done.

The receiving equipment consists of a Radio Apparatus Co. long wave set and a home-made regenerative for short-wave work, on which about everything is heard from 1AW to 5ZA. An SCR-55, used as an amplifier, can be thrown onto either receiving set. VT-1's are used thruout.

A college-made power panel is at the right-hand end of the operating bench, and to the right of it the transmitter is located. This consists of a 2 KW Packard transformer, Dubilier special condenser, Hyrad disc revolving 3600 r.p.m., and a pancake O.T. Since this photo was taken a new O.T. using 2-inch ribbon and mounted on hinges on the wall has replaced the one shown, incidentally shortening the closed-circuit leads also.

(Concluded on page 62)





# Strays



Announcement has been received of the marriage of Miss Mildred Josephine Finn to Mr. Ralph Howard Groves Mathews, 9ZN, A.R.R.L. Central Division Manager, on April 23d in Chicago. Our phone diaphragms barely stood up under this news, but we are sure the whole amateur world joins with us in hearty expression of good wishes for a long and happy wedded life to Matty and his little lady.

1HAA is no more. Vermilya is now 1ZE, using 200, 250 and 375 meters.

Wouldn't it be wonderful if Kruse owned a lunchroom?

We print the following from the May issue of "Radio News", excerpted from a story by "G. Ridleak":

"...A friend of mine who also gives a weekly wireless concert confines himself to organ recitals. He plays these on a thing which believe is called the "QRT". This instrument, or whatever it is, is said to be the official organ of the Awful Racket Raisers League. From what I've seen, it sure takes a lot of wind to run an organ."

We wish we might also print the letters we have received from indignant A.R.R.L. men. But it really wouldn't do. We leave it to the amateurs of the country to form their own judgment.

In that "\$100 C.W. set", and others as well, it is advisable to use a separate transformer for heating the filaments. Then the filament voltage can be controlled by a rheo in the primary of the filament transformer if desirable and, as a big improvement, the key can be placed in the 110 v. circuit of the plate transformer.

Henry Klaus, 9AK, had a little accident recently, burning out all the tubes in his radiophone. Guess how many? Well, Henry figures that if it had been only four tubes or so it wouldn't have been half bad. The horrid truth seems to have been that there were thirteen of 'em in parallel and they simultaneously exhibited Dr. Goldsmith's "discouraging decisiveness" and went up the flue together! Oh mamma!

Paragraph 86, page 58 of the 1919 edition of the radio laws has been re-

pealed as of July 1. This was the paragraph that formerly gave authority to operate a station while awaiting receipt of a license.

The Somerville Radio Laboratory have added to their line of meters a model JX, 0-15 volt A.C. voltmeter, especially intended for the filaments of power tubes heated by A.C. The desirability of using voltmeter vs. ammeter is recognized but there have been no small scale A.C. voltmeters heretofore. The JX should completely fill this need.

9YA has a calibrated receiving set and will be glad to advise the correct wave length of anyone with whom they work.

The formation of a radio fraternity is announced at Coe College, Cedar Rapids, Iowa, with a chapter at Iowa City also. It is known as Alpha Delta Alpha. Information can be obtained from Paul A. Young, Radio Engineering Dept., Coe College.

On the night of April 19 last the C.W. signals of 8LF, W. K. Thomas, 17 Emerson Ave., Crafton, Pa., were copied by Jack Stevens, 6AOY, Avalon, Calif. Mr. Stevens reports the signals "normally loud—about the same as XF1 and 8XK". 8LF was using four Radiotron U.V.202's, putting 2.4 amps. in an antenna of about 8 ohms resistance, equivalent to an output of about 46 watts. Both participants in this C.W. record are to be congratulated.

On the night of May 14th when auroral disturbances had wire service completely tied up, 1AW undertook to get the Associated Press service from New York for "The Hartford Courant". It was realized that no station outside daylight range was likely to be heard and 1AW simply sat thru a long blank period until finally 2EL was heard. 2EL is Mr. H. H. Carman of Freeport, L. I., one of our best stations. 1AW succeeded in raising him and explained what was wanted and 2EL, after first being told by the New York officers of the A.P. that the wires were O.K., finally secured the news from them by telephone and passed it on to 1AW, where it was rushed to the newspaper office. Thus was

another good job put over for Citizen Wireless and Mr. Carman has our thanks and congratulations on his persistency and success.

A decision of far-reaching importance has just been rendered by Judge J. M. Mayer in the United States District Court in a suit brought by Edwin H. Armstrong and the Westinghouse company against the deForest company. The suit was brought for alleged infringement of the well-known Armstrong circuit patents and the judge's decision broadly sustains the patent and holds it to have been infringed.

The Armstrong patents in question are the so-called "feedback" patents, covering almost any method by which part of the plate circuit energy may be returned to the grid circuit to reinforce the action, and apply to regenerative or oscillating receivers or tube transmitters, whether capacitive or inductive feedback. Mr. Armstrong, and the Westinghouse company by virtue of rights acquired from him, therefore are recognized as having the sole right to the use of the oscillating circuits employed today.

In his decision Judge Mayer paid great tribute to the imagination, clearness and accuracy of thought, perseverance and extraordinary ability of the inventor, incidentally dubbing him "Feedback Armstrong."

In the "Wouldn't it be wonderful—" column of this section in May QST a disparaging reference was made to the ability of the operator at WHE. There is but one operator at WHE, Mr. J. W. Harte, and we have convinced ourselves that he is a very good operator, rather than a poor one. Whereby, of course, a big injustice was done Mr. Harte and we take this means of offering our humble apologies.

On the value of radio frequency amplification: "The effect of amplification of the radio frequency currents is proportional to the square, while amplification of the audio frequency current gives an effect proportional to the first power. If a weak signal is amplified 20 times before it is applied to the detector tube the resulting audibility will be as great as would be obtained by applying the signal to the detector tube directly without amplification and then amplifying it 400 times.—"The Log" (Third Naval District).

No, Oswald, the airplanes don't drag a wire on the ground to make their earth connection—they use a counterpoise.

#### The Bite of the Wireless Bug

By Peter Deets

The wireless bug of which you've read

has bitten me, that's clear; no serum treatment yet devised can help me now I fear. At first I had a simple set, loose coupler and receivers, detector of galena stone, take note you unbelievers. It worked and each and every night, (the effect of the bug increasing), I'd try to understand the code. My efforts were unceasing.

Now and then I'd catch an "o", and "i's" I got with ease. The signals weren't so very good, just loud enough to tease. In order to increase them, I got a two stage set. The code and music now are great, it beats a "Vic" you bet.

Oh! when I think of all the time I've spent in crystal gazing, in search of useful spots thereon, in truth it is amazing; and some day in the years to come when I have learned the code and when I get my license I'll write another ode, and tell you all about the joys, as would old Epictetus, of how it feels to have a case of genuine "Wireless-itis."

They tell us there are a flock of operators on the U.S.S. Tennessee who believe it utterly impossible that amateurs with their limited power could be able to handle the Transcons as we know we did. In fact, it is intimated that the gentlemen believe our story is pure fiction. It would be if we had as much trouble making our sets reach out as the Tennessee does in trying to cover 200 miles with her 10 KW.

XG1 is the U.S. Army Balloon School at Lee Hall, Va., about 20 miles from Newport News. The CW set is an SCR-67, and the spark set an SCR-73.

From the *LaCrosse, Wisc., Tribune*:  
"Citizen's Comfort Considered"

"Wireless Amateurs of England and America will endeavor to get in communication with each other on February first. The operations of the American amateurs are handicapped by Government restrictions. In order that the operation shall be conducted with as little annoyance to the outsiders as possible, a new garage has a sound proof room in which the horns are to be tested."

What the hexx!

David Sarnoff, commercial manager of the Radio Corporation of America since its organization, and for fifteen years connected with the Marconi interests, has been appointed general manager of the corporation; and E. P. Edwards, for a number of years assistant manager of the Lighting Division of the General Electric Co., has been appointed in charge of engineering, manufacturing and sales.

Our idea of nothing to do: Listening to somebody's radiophone concert.



THE A.R.R.L. has the pleasure of announcing the ratification of affiliation of the following additional societies, as of June 4, 1921:

Maryland Radio Assn., Baltimore, Md.  
Southern Ontario Radio Assn., Windsor, Ont.

Wireless Assn. of Pennsylvania, Philadelphia, Pa.  
Staunton Radio Club, Staunton, Ill.  
Wireless Assn. of Ontario, Toronto, Ont.  
Hill City Radio Club of the Summit Y.M.C.A., Summit, N. J.  
Stoneham Radio Assn., Stoneham, Mass.  
Premier Radio Club, Grantwood, N. J.  
Manhattan Assn. of Radio Scouts, New York City

Radio Research Assn., New York City  
Waco Hertzian Society, Waco, Tex.  
Community Radio Club, White Plains, N. Y.  
The Radio Assn. of Salem, Salem, Ore.  
Collegeville Radio Club, Collegeville, Pa.  
University of California Radio Club, Berkeley, Calif.

Radio Club of the Bronx, Bronx, N. Y.  
Napa Amateur Radio Club, Napa, Calif.  
Peninsula Radio Club of San Mateo, San Mateo, Calif.

The Mt. Sterling Radio Assn., Mt. Sterling, Ill.

Laconia Radio Club, Laconia, N. H.  
Peoria Radio Club, Peoria, Ill.  
The North Shore Radio Club, Chicago, Ill.  
Triangle Radio Society, Rochester, N. Y.  
Yonkers Radio Club, Yonkers, N. Y.  
Radio Club of the Y.M.C.A. of the Oranges, Orange, N. J.

Tech Radio Club, Oakland, Calif.

The Maplewood High School Radio Club, Maplewood, Mo.

Y.M.C.A. Radio Club of Rome, Rome, N. Y.

Fordham Radio Club, Bronx, N. Y.

Ottawa Amateur Radio Assn., Ottawa, Ont.

Rubber City Radio Club, Akron, Ohio

Ft. Worth Radio Club, Ft. Worth, Tex.

Northwestern Indiana Radio Assn., Hammond, Ind.

Westfield Radio Assn., Westfield, Mass.

Brockton District Radio Club, Brockton, Mass.

Mystic Valley Radio Club, Malden, Mass.

The Ypsilanti Radio Assn., Ypsilanti, Mich.

The Limited Radio Assn., Chicago, Ill.

Radio Club of the Carnegie Inst. of Technology, Pittsburgh, Pa.

St. Paul Central High School Radio Club, St. Paul, Minn.

University of Virginia Radio Club, University, Va.

The Conneaut Radio Club, Conneaut, Ohio

Scenic Highway Radio Club, Clinton, Iowa

Fall River Amateur Radio Club, Fall River, Mass.

Regina Amateur Radio Assn., Regina, Sask.

#### National Convention

At the First National A.R.R.L. Convention at Chicago Aug. 30—Sept. 3 important discussions of co-operative measures, club organization and activities, community work, etc., are scheduled. These will be of high interest to all forward-looking clubs and we suggest that as many societies as possible arrange to have at least one member attend the convention to partake in the discussions and secure ideas that will undoubtedly be worthy of local application. In other words, everything that clubs are interested in is going to be up for discussion at these meetings and it's going to be worth while to have a representative there to soak up ideas and report, if nothing else.

#### Here's Co-operation

The radio clubs at Washington, Baltimore and Hagerstown are having a series of get together—get acquainted meetings that already have eliminated all petty local differences and have done much to cement that locality into a smooth-working unit.

The first meeting was held at Washington on April 22d under the auspices of the Washington Radio Club, Mr. S. Kruse presiding in the absence of Mr. H. H. Lyon, president. About 125 were present.

A remarkably simple radio recorder was exhibited by Dr. E. A. Eckhardt, of the Sound Section of the Bureau of Standards. Using but two VT-1 (Western Electric J) tubes and an average amateur antenna this device recorded on paper, perfectly, the signals of YN, WII, and WSO through medium static.

Several men from each of the three cities told of the operating conditions and schedules followed in their own localities and how the stations in the other cities were heard. A great deal of very interesting information regarding the possibilities

of regular relay routes between Baltimore, Hagerstown and Washington, which heretofore have not been in regular communication, was obtained.

After the formal meeting dinner was served at the Canton next door. Everyone ate all they could and enjoyed greatly talks by L. C. Young of NSF; S. Kruse of WWV; E. B. Duvall, A.R.R.L. A.D.M., of Baltimore; S. W. Piper, vice-president, and E. A. Green, secretary, of the Hagerstown club and several other prominent amateurs. The meeting was a great success.

The Washington and Hagerstown radio

happy mood snappy music was rendered by an Hawaiian orchestra which, to put it lightly, did do things up brown.

This meeting was one big success and accomplished this if nothing else: a friendly feeling and the assurance of co-operation by everyone present.

The third meeting of the series will be held soon.

#### The Radio Club of the Bronx

The Radio Club of the Bronx was organized in 1920. For a few months it struggled along on its charter membership unable to grow because of the lack of



Washington—Baltimore—Hagerstown Meeting, May 17.

clubs, and representatives from clubs in Martinsburg, W. Va., and Waynesboro, Pa., were guests at a co-operative meeting and banquet given by the Maryland Radio Association, of Baltimore, at the Caswell Hotel at that city on May 17th.

The Baltimore meeting proved to be one of the most lively affairs held in the Third District since the Convention in Philadelphia last February. Addresses were made by Mr. L. C. Young of NSF, Mr. Henry Lyon, president of the Washington Radio Club, Mr. S. Kruse of the Bureau, R. E. Linthicum, V.P. of the Washington club, E. B. Duvall of the "Radio Condenser" staff, and E. R. Bateman, president of the local club.

The business of this meeting was devoted to suggestions for the arrangement of DX schedules for the summer months between these cities, both for daylight and evening working. At the close of the business meeting a banquet was served for the eighty-five present, and to keep the diners in a

facilities. After merging with the R.R.C. to form one strong organization, we incidentally acquired a large meeting room and an operating room in the Bronx Y.M.H.A.

At present we can accommodate a much larger membership. To those who wish to join we extend every advantage associated with a strong and growing radio club. We cordially invite visitors and promise a pleasant and enjoyable evening to those interested enough to attend any of our meetings.

The club set at present is undergoing repairs but we hope in the near future to institute an operating schedule and become a link in the great chain of relay work that is being done in the Bronx.

The newly elected officers of the club are Sam Ellner, pres.; Nat Sauberman, secretary; and Michael Levine, treasurer. Kindly address all communications to the secretary—789 East 163rd St., Bronx, N.Y.C.



# Radio Communications by the Amateurs

The Publishers of QST assume no responsibility for statements made herein by correspondents.



## C.W. QRM

2637 Garfield St., N.W.,  
Washington, D. C.

Editor, QST—

It has been brought home of late to those of us in the operating game that CW transmission has possibilities for creating interference that we had not anticipated. It is true that straight CW is very sharply tuned and that a comparatively large number of CW sets may be operated in close proximity without interference if the proper receiving apparatus is used. There are several variations from this ideal condition when CW is put into operation. In the first place, very few of us transmit CW. We modulate intentionally with buzzer, voice, or by an alternating plate power source, or unintentionally by commutator hums or electrolytic rectifier noises. All of these things, especially voice modulation broaden the wave and cause it to depart rather widely from the ideal sharp tuning. Some of this interference can be avoided by carefully filtering out commutator noises and using pure CW in place of commutator or otherwise modulated CW. The telephone is inherently broad tuning, and for that reason, to me an obnoxious perversion of the CW set.

There is another type of interference which is due to oscillating receiving sets which are used in CW work. Each of these sets, if operated autodyne, is a moderately good transmitter capable of creating considerable local interference, especially when several operators are listening to the same sending station and hence are radiating unintentionally on about the same wave length. We have found it quite possible to send for a mile or so by using the receiving set as a CW transmitter. It follows that we can create considerable interference over at least the same range. This nuisance has already become a practical operating difficulty in Washington and if the much announced conversion of amateurs' transmitters to CW should become a fact, we are likely to be operating under difficulties that will make our late spark interference seem tame by comparison.

Will not someone suggest a type of receiving set which when used for CW reception will not radiate and yet can be handled with sufficient ease so that a CW set may be followed through its wave

length variations? The same operating difficulty has led to the use of the separate heterodyne in Europe. It would seem most unfortunate that we should complicate our sets in a similar manner.

Sincerely,  
S. Kruse.

## RECEIVER CIRCUIT DESIGN

104 West 49th St.,  
New York City.

Editor, QST—

Have read with interest Mr. Hatry's letter on page 58 of the May QST in which he presents a simpler regenerative circuit than any of those given by the writer in the March QST.

For about nine months, just after the ban was lifted, the writer experimented with nothing other than single-tuned receivers, and tried about every circuit that came to hand that looked anywhere near feasible, and some that could well be used as monuments to the deviser's imagination. Over twelve receivers were actually assembled and built employing some different form of tuning or regeneration, while there is no complete record of number or circuits that were tried. However, after getting one out of the lot that seemed the best, it was given a careful test against a loose-coupled variometer set, with discouraging results.

Mr. Hatry's circuit was tried among others, and despite a trial of different inductances, condensers, etc., it was found that to cover the range Mr. Hatry attributes to it, all four adjustments had to be carefully juggled, while to work from about 180 to 300 meters, the antenna inductance had to be varied, as well as the capacities, while the plate inductance was left at a fixed value. This left three adjustments, and when compared with the three in Figs. 1 or 2, as given by the writer, the single-tuned set showed a woeful lack of selectivity, and was extremely critical in adjustment for phone reception.

The antenna used in this test was a very short single-wire of low capacity, and it was noticed that good selectivity was only obtained, as Mr. Hatry states, when the antenna series condenser was set at very low values, in the writer's case from about 50 mmf. to 250 mmf.

However, for constructional cost, Mr. Harty's set has it all over the writer's, and works very well where there is less QRM than in and around New York.

A very good single tuned set may be constructed with only one condenser, using the tickler circuit. In this case the condenser is used in the ground lead, regeneration being obtained by a tapped tickler tightly coupled to the antenna inductance. The antenna inductance should be tapped every ten turns, and the tickler every three after about 20 turns, with enough wire used to cover the desired range of wave lengths. This set has the advantage of no moving coils, and only one condenser, and operates very nicely, even on phones.

Capacity tuning of the plate circuit is not entirely satisfactory for several reasons, one of which is that the condenser alone does not always permit a zero regeneration adjustment. Take for instance a case where for a given station a large inductance is used in the plate circuit, with a correspondingly small shunt capacity. If we then try to shift to a weaker station on approximately the same wave, the condenser, even at zero, may not be low enough for best regeneration. This means that the inductance must be reduced, the condenser reset, and the antenna condenser probably reset, and yet if we try to shift the regeneration by the shunt condenser alone, it is probable that good results will not be obtained. However, this trouble is not confined to single-tuned sets alone, and should be considered when designing any type of tuned plate set.

The writer hopes Mr. Harty will not be offended by this comment, as he probably realizes the faults of single-tuned sets as well as anyone else, and knows that they cannot be compared to sets designed as carefully, only with inductive coupling.

With best regards, I am,

Yours very truly,  
McMurdo Silver.

#### UNRELIABLE STATIONS

Marion, Mass.

Editor, QST—

Just a word about "Spasmodic hams". We have them all around me. For instance, where are all the hams and official relay stations in Fall River and Rhode Island the last many weeks? Also Martha's Vineyard, and several other nearby places?

I have messages on hand for all these birds. In their succession, they will come on the job every night for two or three weeks, when there is nothing on the hook for them, causing all kinds of careful tuning to work around them. Then when messages arrive, they are off the job for a month at a clip and the messages must be mailed.

This is no fading or poor radio weather

for they are all well within range when on the job. No monthly reports have ever been received from any relay station as long as I have been D.S. for So. Mass., and what I turn in is gathered by observation only.

How come such stations exist at this late day of advanced Citizen Radio? What are we going to do about it? Shall we consider them dead and never forward them a message whether they are on or not, or shall we just forget it and put them down on our list as "inactive spasmodic radio stations" with which radio communication is unreliable?

Very truly yours,  
IZE.

#### GOOD WORK ON CRYSTALS

1619 Grand Ave.,  
Connersville, Ind.

Editor, QST—

I write to tell you about a crystal detector set which has done very good work in recent months.

The set was installed in February and consists of a balanced type galena detector, five hand-wound honeycomb coils, a shunt and a series variable condenser, two pairs of phones, and a fixed condenser. The aerial is a single wire 125 ft. long, 35 ft. average height, within a few feet of the branches of four trees. The ground is three water pipes connected together and then joined to the set by a wire 30 ft. long. The set was intended to receive time signals but amateurs and commercials were also heard. For amateurs, two single-layer H.C. coils in series with the series condenser were used, while a 12-layer coil and shunt condenser were used for Arlington. After a little practice in adjusting the detector very good signals were received and as we became more skilled our range rapidly extended until we heard NAB, NAE, NAR, NAS, NAT, WNU, NGL, WLC and others. Of the amateurs we have heard from the 1st, 3d, 4th, 5th, 8th and 9th districts, including 1XM, 3DH, 3YE, 4AL, 4XC, 5MF, 5BM, 5HL, 5HV, 5HY, 5IB, 5YH, 5JD, 5ZD, 5ZL, 5ZX, 5ZU, 8WC, 8ZW, 9ABU, 9AEG, 9GW, 9YI, 9YB, 9LO, and 9ZC.

Some freaks have been experienced, the most notable being the reception of signals from 9ABU, Carrington, N. D. He was heard sending CQ's and a letter to him brought the reply that he was sending at the time heard but using only 60 watts on a Ford coil and about  $\frac{1}{4}$  amp. in the aerial. But freaks are exceptional, as stations like 5HL, 5YH and 9AEG have been heard clearly nearly every night.

From this it is obvious that exceedingly good work can be done on a crystal. The only essentials are fairly good crystals,

patience in adjustment, and careful listening.

I would be glad to hear from other amateurs who are doing good work with this kind of a detector.

Yours truly,

Carl W. Gartlein, 9DQD.

#### LOSSES IN "A.C." C.W.

Mass. Inst. of Tech.,  
Cambridge, Mass.

Editor, QST—

The popular tendency of late in A.C. vacuum tube transmitters is to avoid the usual rectifiers by the use of the so-called self-rectification systems of using a separate oscillator for each half cycle.

I have taken careful measurements of the characteristics of this system and am disappointed in the large losses occurring in the tube not in immediate operation.

I would like to point out the following concerning the transformers utilizing the secondary centre tap for connection to the filament junction and grid bias.

At a given instant, the centre tap is negative in respect to one outer terminal. At the same instant it is positive in respect to the opposite outer terminal. It necessarily follows that this centre tap is neutral in respect to both terminals. This means that the tube note developing oscillating energy has a negative charge on the plate and a POSITIVE grid charge. This results in surprisingly large losses of oscillating energy by passage of current from this grid to the filament. Fortunately, the phase relation is so disturbed that the transformer input decreases and the losses are not as great as one would at first suppose. Nevertheless, the input-output ratio of such a system has discouraged its use at the station of the M.I.T. Radio Society.

Our available time for experiment is extremely limited and I would appreciate together, I am sure, with many other experimenters any information on this topic published in the pages of QST.

Sincerely,

Edmond Bruce.

#### OUTTA SPIRITS

Richmond, Virginia,

Dear Eddy:—

Say, OM, where do they get that stuff Ouija is all wrong? I owe my life to that bird for several reasons which I am going to set forth in this horrible example of narration.

To begin with, my spark had never been heard outside of the city limits, even though it was a full grown 1 KW with a radiation of 1.4 amps. using the best ground I could get. Hooked myself onto the city

water mains, buried wires, strip, etc. I could not make a soul hear me even though I used up about \$17.43 worth of juice per month and the Power Co. sent up to test my meter voluntarily for "high bill". Well I had almost given up in despair, cursed those birds who said they sent thousands of miles on 1KW, laffed loudly at those who said they got 8 amps on 1 KW, etc., as the greatest flicker I could get was 1.4 on a big meter.

I dropped around to a girl's house one night recently and the gang were there playing Ouija Board. Now, I am very very skeptical regarding talking with spirits, especially this time of the year as my stock is about all out now. But they harangued me to ask the thing a question, swearing it would answer. So as radio was prominent in my mind and the girls operating the thing didn't know anything about radio, I thought here is a chance to QRT Ouija in our locality. So I asked it would a ground or counterpoise aid me in furthering my distance. It answered 'counterpoise'. So I began to sit up and take notice. Then I fired another, asking how long, and it told me and after a fifteen minute session with it, it had given me complete description of the counterpoise, how to insulate it, how far off ground to put it, the number of wires, etc. Then I asked what radiation should I look for and it said five amperes. Then I asked it to give me the call letters of several friends and it just naturally faded the Government call book out entirely. So I say this Ouija bird must be T.O.M. himself. After getting all the dope I went home and slept on it. The more I thought abt it the more convincing his argument was, and I didn't have my hands on the board at all. Just a coupla Janes working it.

The next day was Saturday and as I took a half-day off I bought the stuff for the counterpoise and went home and put it up. After getting it up and disconnecting the ground, I pressed the key and the hot-wire meter took a healthy flicker and went over to about 5 and I took my hat off then. The gang in town reported me very much more QSA and I went home and ate supper and the first night I listened in after I put the counterpoise up I worked 3BZ, a distance of 150 miles, who reported me QSA. This was the first time I had ever worked out of town on the set and the "Combination" was found. Have since received several letters and cards reporting my spark QSA in nearby cities and I hope to get further by adding more wires to the counterpoise. Now don't think I am in the same class with the fellow who reports he was arrested for being crazy—talking in a radiophone and the neighbors sent a cop over because he mumbled to himself (seemingly) all the nite.

If I am heard any more it's due to that confounded Ouija and let me say a word right here in its behalf.

"IF YOU WANT DISTANCE AND ADVICE, GET A OUIJA BOARD".

It has Dr. Radio, Zenneck, T.O.M., M. B. West and all the other dopesters beat a mile; although I am firm believer in all of the above, I am for the Ouija without exceptions. I accept the nomination.

Now you can either believe that or not but T.O.M. has good food for thought in one of his "rotten" arguments by naming it "Rotten Ouija Dope."

Got to go now, spilled enough for this time. Take it or leave it, the counterpoise is there to stay. If Hertz's spirit told me to stick up the counterpoise, I thank him, for it sure did prove a revelation to me.

CUL and lets hear what the gang has to say abt this.

73's

C. D. Blair, 3ZL.

#### TRANSMITTING ON VT-1's.

92 East Franbes Ave.,  
Columbus, Ohio.

Dear Mr. Warner:


In regard to my low powered C.W. set you recently inquired about. It used only a VT-1 receiving tube that I was fortunate enough to get a hold of and surely proved itself a wonder.

I received letters from Mr. Furrow, 8FT, of Troy, Ohio, and Mr. Endley of Mansfield, Ohio, 8ZR, both saying my CW signals came in fine. Stations up to ten miles reported my buzzer modulated and voice readable at quite a distance from the phones, one station even reported buzzer and voice readable over the entire floor of his house. The distance to Troy and Mansfield is between 60 and 65 miles, the straight CW sigs only being readable there. What seems the most remarkable part of it, is that all the work was accomplished with an antenna only 20 ft. high, a single wire from the back porch to a nearby telephone pole about 60 ft. long. There were numerous large buildings very close which do not help matters any.

I used an old 500 volt motor, which gave about 500 volts when driven as a generator at normal speed, although voltages as high as 600 have been obtained without undue overload. 500 volts is about as high a voltage as the VT1 bulbs will stand without blueing over and excessive heating. When working at exactly 400 volts and with a filament current of 1.2 amp. I got a radiation of 400 milamps. I generally work the voltage at 375 volts as I believe the tube will have a longer life.

I am enclosing two circuits with con-

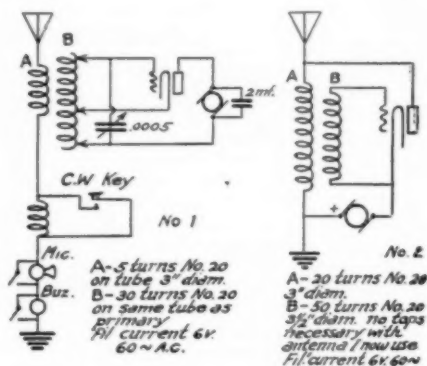stants which I have used with equal success with the VT-1. Circuit No. 2 seems to work better with the Marconi bulbs and not require a very critical adjustment of turns, ten turns in the primary does not affect radiation in the least. It seems very queer but is an actual fact. Am able to put about 350 milamps in the aerial with one Marconi bulb. 400 volts on plate.



I used 110 V. AC supply stepped down with a toy transformer to light the filaments.

The above work was all accomplished during the daytime. Have worked with 8FT—62 miles at 1 P.M. and 8ZR heard my sigs at 5 P.M. so you see I must have had quite a little range at night.

Sincerely yours,

Robert C. Higgy, 8IB.

#### ARTISTIC REPORT POSTCARDS

711 W. 23d St.,  
Austin, Tex.,

Editor, QST—

It is the general practice among amateurs to let others know how their signals are "coming in" and this is often done by means of postal cards.



FIGURE 1



Some amateurs have cards printed, but this involves too much expense for the average "radio shark".

A very serviceable card stamp may be made by cutting the call letters out of some material such as an old inner tube, and then gluing them to a block of wood. The letters of course must be reversed as in Fig. 1. After the glue has dried all of the letters may be made the same thickness by rubbing the stamp block on a piece of fine sandpaper. An ordinary stamp pad will serve to ink the stamp.

Yours sincerely,  
Geo. E. Endress, 5JA.

PAGE MR. GROVES.

Mercer, Pa.,

Editor, QST:—

"A Novice" certainly raises an interesting point when he asks in the January QST why we do not hear more from the amateurs on the performance of the honeycomb coils. We are all interested in the fine work Mr. A. L. Groves has done, but we would like to know whether any one else has had his success with these coils. I have read Mr. Groves' articles attentively, and he has been kind enough to write me several letters in an endeavor to get me into the straight and narrow path, but up to date I have not been able even to approximate his performance. While giving Mr. Groves full credit for his wide experience and undoubted skill, I am inclined to think there is something very favorable in his location. There seems to be regions that attract radio waves that have passed over other territory with seeming contempt. Every radio situation is to a great extent a law unto itself. An aerial and an equipment that will give a certain result in one place will not duplicate that result in another in all cases. It looks as if the tuning of honeycomb coils for long distance reception were almost an art by itself; but it is one well worth pursuing, for success in spite of difficulties is a reward worth having.

Mr. Novice's experience has been astonishing. He tells us that his coils perspired profusely and that the water literally dropped from them. Now, I have labored some with these coils, and I can testify that in my case it was the operator that did the sweating. I fear that Mr. Novice's locality is very wet and needs the attention of the prohibition enforcement officers.

But testimony is what is wanted, so I shall proceed to detail my experience with the honeycombs. Aerial 116 feet long and 62 feet high; 6 cooper cables spaced 26 inches apart. Last February I got two coils of 1200 turns each and one of 750 turns. These I mounted on a straight rod. I used one audiotron and Holtzer-Cabot

receivers. As to results: I heard the Atlantic coast stations, Mexico City and sometimes San Diego, Calif. Of the stations on the other side I heard POZ many times, YN once and MUU two or three times; all nicely readable. As spring advanced I had frequent engagements with King Static, and was finally routed and driven from the field. This winter I got the coils out again, and purchased a number of others. The latter were mounted on plugs. I also mounted my original three on plugs so all could be used on one of the hinged mountings. Now the strange part of the story is that although I am using the same aerial, the same tube, the same 'phones and the same coils (and more) that I used before, I do not hear any European stations at all. Why is it thus? I do not know.

I have been after the CW stations exclusively and have used the tickler circuit. I have no duplicate coils except the two 1200's. It is with these two, using the 750 for a tickler, that I have had my best results. Perhaps if I had more duplicates, I should have better success. NPL XDA and the Canal Zone are as far as I have penetrated this season. I get NPL by using two 1200's with a 750 as a tickler, and the secondary condenser (.001) set at 54. I can hear WSO almost any way, without primary and aerial connection. But the signals come from the aerial just the same. I can place one hand on the aerial binding post, and, by using the other hand as a primary, get greatly increased signals from WSO. It is probable that a 23-plate condenser in shunt to the secondary would work better than a 43-plate, as it would allow greater freedom of movement in making adjustments.

From the above it will be seen that neither my success nor my activities have been great. I intend, however, to get more ammunition and continue my campaign against Europe, hoping for a set of coils that will enable me to hear the ex-Kaiser groan as he confesses his sins.

S. F. McCartney.

#### CORRECTION

Thru our error the advertisements of Radio Testing Station in May and June QST quoted their aerial wire "per 100 ft., 58c; per 100 ft., \$5.50." The figure of \$5.50 is the price for 1000 ft.

#### 1XM, CAMBRIDGE, MASS.

(Concluded from page 52)

agreed upon by the Greater Boston Executive Council, on which the Society is represented, will be strictly followed.

During the month of April 1XM handled 171 messages, worked forty stations outside of the first district, and has copied 124 DX stations. 5ZA, 4YA, and 4BY

have been copied and the last mentioned also worked. 2DN, 2BK, and 2OW have been easily worked after daylight.

The Society is indebted to the Acme Apparatus Co., Atlantic Radio Co., Radio Equipment Co., Clapp-Eastham, W. J. Murdock Co., General Radio Co., and American Radio and Research Corp., for their co-operation.

Communications should be addressed to the M. I. T. Radio Society, Box 160, Massachusetts Institute of Technology, Cambridge 39, Mass., or telephoned direct to the station.

### OPERATING DEPARTMENT

(Concluded from page 45)

ful attempts to arrange schedules with Hagerstown stations; they are unable to receive Washington regularly account bad induction. During the recent aurora disturbance, many nights passed without Washington stations hearing any but Baltimore stations. This is phenomenal, as the signals were strong and steady, whereas normally night communication between these cities is almost out of the question.

It is hoped that the good work of the numerous DX men in the District of Columbia will continue thruout the summer, and there is every indication to this effect. The use of straight C.W. is showing itself very effective in maintaining communication under adverse state conditions, the chief difficulty being inability to raise stations other than those with whom schedules are pre-arranged.

Reported messages, 1519.

### 5XA, AUBURN, ALA.

(Concluded from page 52)

5XA is under the direction of Mr. V. C. McIlvaine, Laboratory Instructor, Box 12, Auburn, to whom correspondence

### MAY STATION REPORTS

(Concluded from page 48)

#### 5ZU, Austin, Tex.

| Steadiest    | Loudest      |
|--------------|--------------|
| 4XC—4GL—4YA  | 4XC—4GL      |
| 5XB—5YK—5ZA  | 5XB—5YK—5ZA  |
| 6ZZ          | 6ZZ          |
| 8ZZ—8YN—8ZY  | 8ZZ—8ZY—8YN  |
| 9AEG—9LR—9EL | 9EL—9AEG—9OE |

#### 7DA, Portland, Ore.

| Steadiest         | Loudest           |
|-------------------|-------------------|
| Can. 5BA—Can. 5CJ | Can. 5BA—Can. 5CJ |
| 6ZU—6AH—6KA       | 6ZR—6ZU—6AH       |
| 7YA—7BK—7FI       | 7YA—7FI—7BK       |

#### 7ZM, Moscow, Idaho

| Steadiest    | Loudest       |
|--------------|---------------|
| None         | 5ZA           |
| 6ZR—6ZX—6AGF | 6ZR—6AH—6OC   |
| 7YA—7CU—7ZJ  | 7YA—7YS—7CU   |
| 9AGN—9LW     | 9AGN—9LW—9AEG |

#### 9YB, Purdue University, Lafayette, Ind.

| Steadiest   | Loudest     |
|-------------|-------------|
| None        | 3XM—3YE—3YA |
| None        | 4YA—4AG     |
| 5E—5YH—5DA  | 5DA—5YH—5EK |
| 8ZR—8CF—8SP | 8YN—8ZR—8ZW |
| 9LQ—9ZJ—9FS | 9ZJ—9LQ—9OE |


**Remarks:** Very few stations coming through from First, Second, Third, Fourth and Fifth districts. Reception has been unusually poor during latter part of month.

A newcomer, 5EK, in the Fifth District has been heard a number of times and seems to be the most consistent of the stations in that district but not as loud as some of the others.



8ZR seems to be holding out in the Eighth District but most of the other good stations mentioned in past reports seem to have dropped off the earth. A new special 8YN comes in very loudly.

In the 9th District, 9LQ now gets credit for being the most consistent station. Since 9ZJ has gone down to 200 meters his signals although loud have a tendency to swing more. 9FS has been working consistently during the past month.

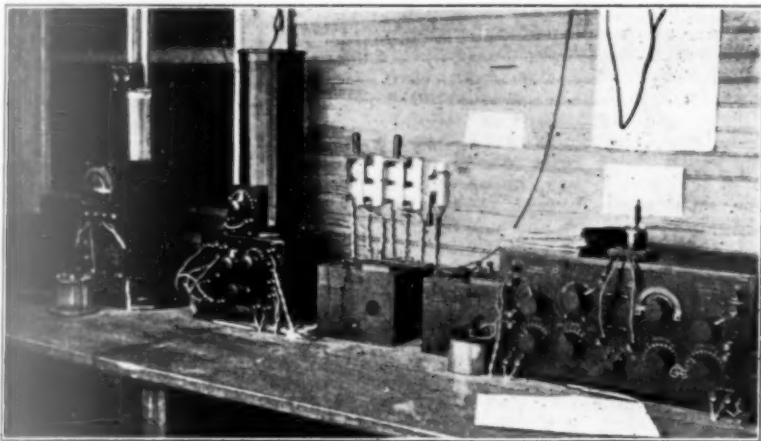should be addressed. Mr. McIlvaine advises us that 900 watts is the greatest power 5XA uses, at which input 4.5 amperes antenna current was attained on 270 meters with the coupling shown.



# SHRAMCO - R E O -

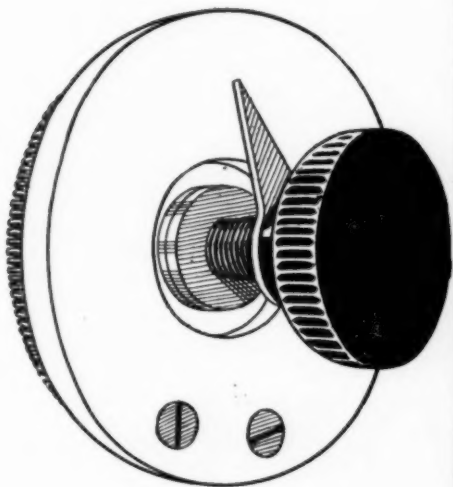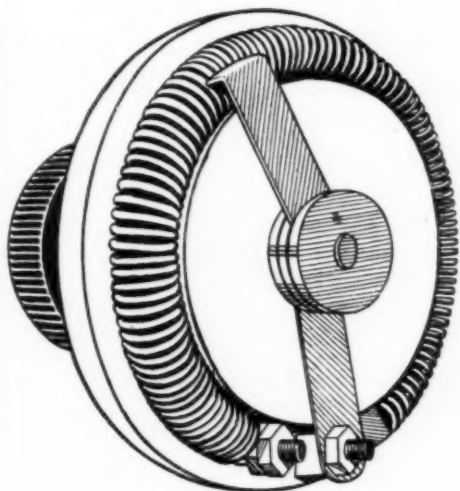

## for your power tube--

*New type Shramco Reo, No. 90P.*

*1.5 ohm Nichrome resistance.*

*Current capacity 6 amperes*

*Price \$2.00, 1 lb. postage.*

**A** BACK MOUNTED panel rheostat, specially designed for the Radio U.V. 202 and other transmitting tubes. Resistance element (1.5) ohm) is "Nichrome" wire, mounted on a solid block of asbestos. Allows unusually accurate and delicate variation of the filament current. All metal parts brass. Spring

phosphor bronze blade. Base 3". Overall height 2½". Handsomely finished and accompanied by an unconditional guarantee of complete satisfaction. Get the most out of your expensive power tube by using a good rheostat. Order a Shramco Reo to-day! Now ready for immediate shipment.

### for your VT detector

*and amplifier, use the original Shramco Reo, type 90. Similar to the power tube type, but with a "Nichrome" resistance of 6 ohms. Price, \$2.00, plus postage for 1 lb. We also make the "Midget" Shramco Reo, 5 ohm resistance, 2½" base.*

**SHOTTON RADIO MFG. COMPANY, INC.**

**P. O. BOX 3, SCRANTON, PA.**

*Catalogue "K", listing a complete line of high grade parts at reasonable prices, sent to any reader of QST for five cents in stamps.*

# ESCO

## GENERATORS—MOTOR-GENERATORS—DYNAMOTORS



4 to 32 Volts for Filament.  
350 to 2000 Volts for Plate  
Capacity 20 to 2000 Watts

LIBERAL RATINGS

Write for Bulletin #231 Which Lists  
200 Combinations.


Motors and Generators Developed and  
Built for Special Purposes.

Pioneers in the Manufacture of High  
Voltage Direct Current Radio Generators.

**ELECTRIC SPECIALTY CO.**


215 SOUTH STREET

**STAMFORD, CONN., U. S. A.**

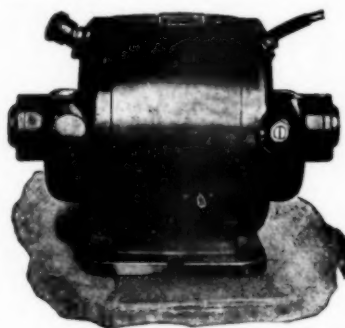
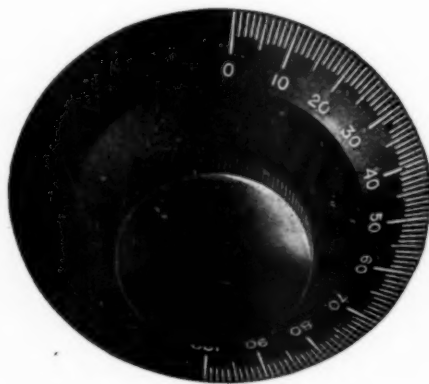
### THE VARIOMETER

The now famous Z. R. V. Variometer has met with a tremendous sale, thousands being in use, by those who know the quality of Clapp-Eastham products.  
Complete with knob and dial.....\$6.50  
Without knob and dial..... 5.75  
Variocoupler to match with knob and dial 7.50



### THE DIAL

This 3" knob and dial is our own product heavy brass dial black oxidized finish, composition knob 1 3/8" diameter. Supplied for 1/8" shaft only. This dial cannot chip or warp and will run true. Its beauty is in keeping with the best products of the instrument maker.  
Price dial and knob #F800H complete..\$0.75


Complete catalogs sent for 6c stamps  
Patronize your local dealer: If he won't supply our material your order will receive immediate Factory attention.

**CLAPP-EASTHAM CO., 114 Main St., Cambridge, Mass.**

Headquarters for Radiotron Tubes. All types in stock.



## CORWIN'S Improved SWITCH LEVER

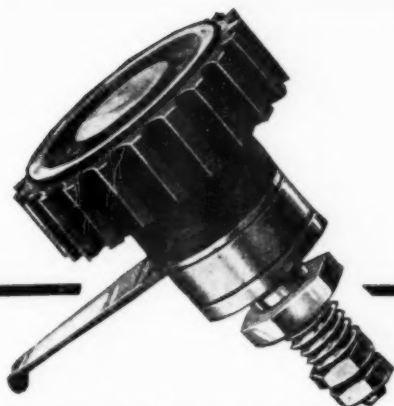

PRICE:—  
90 cents,  
Postage,  
5 cents.

A switch lever may be just a small item, but it pays to get a smooth running, well made switch like the one pictured above. This new Corwin switch is a handsome accessory that will add to the appearance as well as the efficiency of your set. The knurled knob is a special composition,—identical with the knobs used on the standard #67 Corwin Dial. The brass shaft is moulded right into the knob, so that it can never come loose. Blade, bushings, etc., are nickel-plated brass. Contact radius,  $1\frac{3}{4}$ ". Send your order today. Satisfaction guaranteed.

## NEW RADISCO VARIO-COUPLER

This is the coupler that caused such a sensation when it was announced two months ago. Sales have been tremendous, but we, never-the-less, have a generous supply on hand, ready for immediate shipment. "Accurate to the .002 part of an inch!" Moulded base, Formica tube, all metal parts brass. Price \$7.50 postpaid.

## CORWIN'S 1921 CATALOGUE—10c.

If you haven't already sent for your copy, don't lose another day. You will certainly want these 32 pages, listing all Corwin and Radisco instruments. You will find in this catalogue a good instrument for every part of your station at a price that won't "take the joy out of life". One dime and your name brings the catalogue by return mail.

### A few specials from our catalogue,---ready to ship at once

New Patent Plug.....\$2.00  
Postpaid.

#### FIRCO VOCALOUD

The ideal loud speaker. Requires no batteries, no adjustments, no extra equipment whatever.

Station type, .....\$25.00  
(in mahogany cabinet)

Laboratory type ..... 23.00  
(on metal base)

#### UNIVERSAL-COIL MOUNTING PLUGS

Anyone can easily make smooth-running mountings with these plugs. No bending, no filing, they are made to fit exactly, in the first place. Suitable for Radisco and all hand wound coils. A few minutes work with these plugs will save you dollars that can be put into better apparatus. Price 80 cents, postpaid.

#### GRID CONDENSERS

Radisco, postage 3c .....35c

#### "B" BATTERIES

Radisco No. 1 (2 lbs.).....\$1.50

Radisco No. 5 (5 lbs.) ..... 2.65  
Eveready Storage Battery  
prices on application

#### ROTARY SWITCHES

Clapp-Eastham No. 19.....\$1.00

Clapp-Eastham No. 19A..... .35

Our Own No. 1..... .40

Our Own No. 2..... .55

Postage ..... .05

#### CORWIN DIALS

No. 66, 3".....\$0.75

No. 67, 3" with knob..... 1.30

No. 68, 3 $\frac{3}{4}$ "..... 1.00

No. 69, 3 $\frac{3}{4}$ " with knob..... 1.70

Postpaid

#### RECEIVERS

Murdock No. 55, 2000 ohm.....\$4.50

Murdock No. 55, 3000 ohm..... 5.50

Brandes Superior ..... 7.00

Baldwin C .....16.50

Baldwin E, improved .....20.00

Brownlie new .....12.00

Shipping weight, 2 pounds.

#### VARIOMETERS

Radisco No. 1 .....\$7.00

Radisco No. 1D ..... 8.50

All orders for apparatus not listed as postpaid must be accompanied by postage charges.

## A. H. CORWIN & CO.

Dept. D4.4 W. Park St., Newark, N.J.

Remember Corwin's reputation for shipping mail orders promptly and in perfect condition.

# FORMICA

## Sheets, Rods, Tubes

Made From Anhydrous  
Redmanol Resins

Insist on getting the best insulating material  
in your equipment and apparatus.

FORMICA is approved by the Bureau of Engineering, U. S. Navy, and is used by the leading manufacturers of radio apparatus.

**Highest Insulation Resistance**  
**Lowest Power Losses**  
**Splendid Appearance**  
**Excellent Machining Qualities**

*The following dealers can supply you  
with FORMICA sheets, tubes and  
rods.*

Manhattan Electrical Supply Co.,  
17 Park Place, New York, N. Y.

Clapp-Eastham Company,  
139 Main St., Cambridge, Massachusetts.

The Radio Electric Company  
3807 Fifth Ave., Pittsburgh, Pa.

Pennsylvania Wireless Mfg. Co.,  
507 Florence Ave., New Castle, Pa.

Radiotelectric Company,  
919 Huron Road, Cleveland, Ohio.

The Wireless Manufacturing Co.,  
Canton, Ohio


The Precision Equipment Co.,  
2437 Gilbert Ave., Cincinnati, Ohio

Detroit Electric Company  
434 Shelby Street, Detroit, Michigan

The Wireless Shop,  
511 West Washington St.,  
Los Angeles, California

Leo J. Meyberg Company,  
428 Market St., San Francisco, Cal.

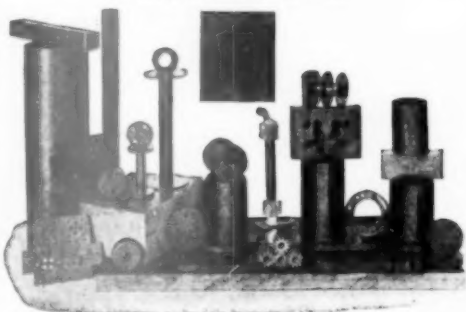The Formica Insulation Co.  
CINCINNATI, OHIO




# -A--A

AUDIO

FREQUENCY


## Amplifying Transformers

**HIGHEST QUALITY**  
**MOST EFFICIENT**

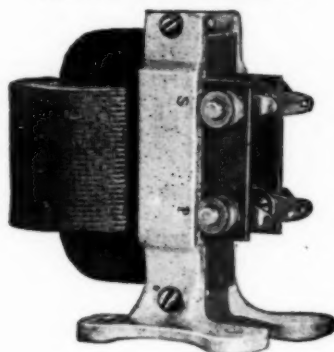

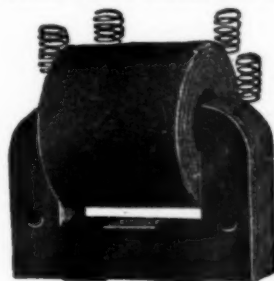**\$5.00**

**NOTE THE NEW (ONE PIECE)  
PUNCHED LAMINATIONS**



**UNMOUNTED**

**\$4.00**

**SEMI-MOUNTED .....\$4.50**

**—DEALERS WANTED—**

Shipments Made From Stock Prepaid.

Note Change of Address

**All American Elecl. Mfrs.**

**1516 NORTH LOREL AVE.,  
CHICAGO, ILL.**

Announcing the

**VOCALLOUD**



\* \* \* \*

#### Laboratory Type

(Mounted without cabinet  
on metal base.)

Complete with 6" cord, \$23.00  
Sound chamber alone, \$12.00  
Sound chamber, with base, \$15  
Vocaloud reproducer with 6"  
cord, \$9.00

#### Station Type

(Complete as shown in  
large photo)

**\$25.00**

\* \* \* \*

At Last - -

**The Ideal Loud-Speaker for \$25.**

Hook a Firco Vocaloud right on to your receiving apparatus, and get your signals QSA—all over your house! No batteries, no adjustments, no extra equipment needed whatever! Just hook your Vocaloud in and listen!

Vocaloud reproduces wireless telephone perfectly, as well as code. Its reproducing elements are the same as a high-priced phonograph.

The reproducer itself employs the famous Baldwin amplifying mechanism. The sound chamber is designed and shaped like a human ear,—the most perfect sound amplifier known. These exclusive features are not duplicated in any other loud speaker at any price. Yet the price of a complete "station type" Vocaloud, (shown above) in an exquisite solid mahogany cabinet is only \$25.00.

Examine a Vocaloud at your radio dealer's. If he should lack a supply, write for leaflet direct to


**John Firth & Company, Inc., 18 Broadway, N. Y.**



**FIRCO** Audion Detectors  
and Amplifiers  
Radio Frequency Amplifiers  
High Voltage Units  
(with any primary voltage)  
Baldwin Phones  
Firco Vocaloud  
Saco-Clad Transformer  
Firco Accessories  
Kolster Decimeter  
United States Bureau  
of Standards Wavemeter  
Eldredge Meters  
(individually calibrated)  
Brownlie Phones  
(adjustable)

**FIRCO RADIO**  
**EQUIPMENT**  
*"Pioneers—since 1901"*

## DO YOU KNOW?

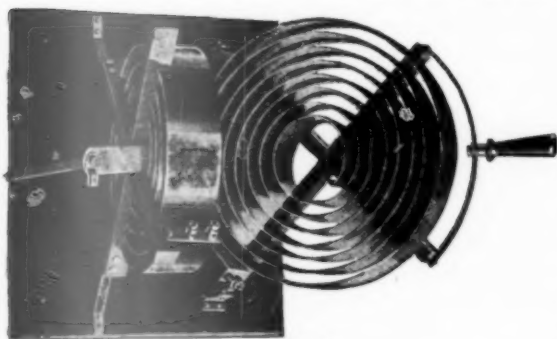

DX-52 PRICE \$25.00

That the current put into your oscillation transformer often exceeds the 2000 ampere mark? That if your O. T. is not wound with sufficiently large ribbon this current will be lost due to the resistance of the small ribbon?

Our DX-52 oscillation transformer is built to take care of this enormous current, being wound with  $2\frac{3}{4}$ " phosphor bronze ribbon, 4 turns on the primary and 8 turns on the secondary.

Aside from that it has bakelite insulation thruout thus insuring you against possible leakage due to poor insulation.

Another feature is that the coupling is adjustable while transmitting or testing allowing you to keep an eye on the radiation meter.

4 large  $1\frac{1}{2}$ " wide clips are furnished free with this instrument DX-52 Price \$25 This is the O. T. used by 8ZR in their trans-continental transmission to 6EJ, 6AK and 7ZJ.

Don't forget our DX-51 Spark Gap and C.W. power motor advertized in the March issue of QST. Price \$30.00.

*Write for our latest bulletin.*

**THE AMERICAN RADIO SALES & SERVICE CO.**

**GREAT AMERICAN BUILDING**


**MANSFIELD, OHIO**

Testing Station 8ZR

## A 6 Volt Battery Will Operate A C.W. Transmitter

when used with a

### RAY-DI-CO "DYNAMOTOR"

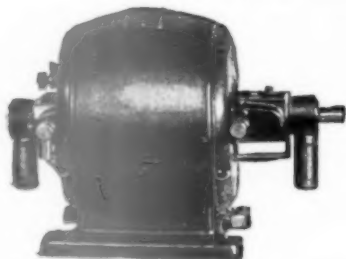

Ray-Di-Co "DYNAMOTOR" operates on 6 volts delivering 400 volts for space current.

"DYNAMOTOR" entirely enclosed—fool-proof—portable—can be placed on automobile, motor boat or used for portable work or in station.

Capacity 15 watts—Net weight 18 lbs.

**Price \$52.35 F. O .B. Chicago.**

*Usual Ray-Di-Co standard of construction prevails.*

## RAY-DI-CO

(Ray-Dee-Ko)

2653D N. Clark St.,

Radio 9AG

Chicago, Ill.

H. H. BUCKWALTER, 713 LINCOLN ST., DENVER, COLO.

*Representative*

Colorado, Wyoming, Utah, Nebraska, Western Kansas, Northern New Mexico, Deadwood and Lead, S. Dak.

*"Meet us at First National Radio Convention Chicago Aug. 30-Sept. 3."*



## THE LATEST "MURDOCK" VARIOMETER

NO.  
345  
"MURDOCK"  
VARIOMETER  
\$7.50



THE PRICE  
IS  
UNUSUALLY  
LOW

THE QUALITY  
IS  
REMARKABLY  
HIGH

WINDING FORMS ARE "MURDOCK" MOULDED

### OTHER "MURDOCK" RADIO INSTRUMENTS

#### REAL RADIO RECEIVERS

No. 55 Double head receivers,  
complete with head band and  
cord:—

|                |        |
|----------------|--------|
| 2000 ohm ..... | \$4.50 |
| 3000 ohm ..... | 5.50   |

#### VARIABLE CONDENSERS

|                                   |        |
|-----------------------------------|--------|
| No. 366, 43 Plates, .001 MFD..... | \$4.75 |
| No. 367, 43 Plates, .001 MFD..... | 4.50   |

#### VARIABLE CONDENSERS

##### Panel Type

|   |        |
|---|--------|
| No. 3661, 43 Plate, .001 MFD<br>with knob and extension handle          | \$4.25 |
| No. 3662, 43 Plate, .001 MFD<br>with knob, dial and extension<br>handle | 5.00   |
| No. 3681, 23 Plate, .0005 MFD<br>with knob and extension handle         | 3.50   |
| No. 3682, 23 Plate, .005 MFD<br>with knob, dial and extension<br>handle | 4.25   |

BUY THEM FROM YOUR DEALER

Bulletin No. 20 Sent Anywhere on Request

## WM. J. MURDOCK CO.


65 CARTER ST., CHELSEA, 50, MASS.

509 Mission St.,

San Francisco, Cal.
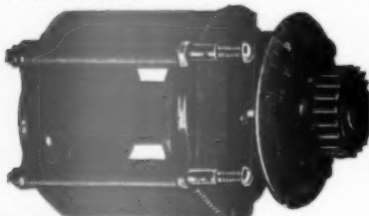
## The ESCO Regenerative Receiver-- Improved

The original ESCO REGENERATIVE RECEIVER as described in previous issues of this magazine has been improved upon. The new set as illustrated above is contained in a smaller cabinet than originally so that now the set is easily portable. All of its former excellent operating features are but enhanced in the new outfit. The wave length range is 150 to 600 meters so that all amateurs and the majority of the commercial stations may be heard. Our new circular describes the set in full. Write for it. Price F.O.B. Columbus, Ohio or Philadelphia, Pa. is \$50.00. Shipping weight 11 lbs.



ESCO variometers and vario-couplers as shown alongside are sold separately for the convenience of those amateurs who prefer to build their own equipment. The instruments are absolutely guaranteed to be satisfactory. Prices are as follows:

ESCO variometer with dial, \$9.50 ESCO vario-coupler with dial, \$10.00  
ESCO variometer without dial 8.50 ESCO vario-coupler without dial 9.00




### PLUGS AND JACKS

The cut illustrates a plug and jack which have been on the market for only a short time but in that time have acquired a wonderful reputation. With their use many practical connections can be effected. Phone and amplifier connections are quickly made in multi-stage circuit. The upper and lower contacts complete a single circuit thru the phones when the removal of the plug automatically connects the amplifying transformer. Jack and plug are nickel-plated and very attractive in appearance.

Plug only, \$0.75; Jack only, \$0.85; Plug and Jack complete, \$1.50.

Shipping weight 4 ounces.

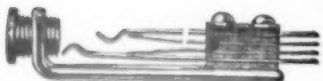

Send 15c for our complete literature of Radio supplies. This amount will be refunded on your first purchase of \$1.50 or over. High printing costs make free distribution impossible.

**The Electrical Specialty Co.**

Dept. L., 48-50 So. Front St., Columbus, Ohio.  
Dept. L., 20 N. 9th St., Philadelphia, Pa.



## —YOUR INTERESTS

are just as valuable to me as are my own. That's one reason why the price of the FADA crystal detector (complete with Super-sensitive Galena Crystal) has been reduced from \$3.00. The other reason is because the demand is so large that for the first time automatic screw machines make the parts in very large quantities.

FADA detectors are used by thousands of amateurs to-day. Many receive radiophone concerts, etc. with this detector and their simple receivers. You'll be proud to own one.

**CRYSTAL DETECTORS now \$2.50 each.**

**FADA panel-mounting RHEOSTAT \$1.25 each.**

Another mighty good buy is the new FADA panel-mounting rheostat. The base is made of an asbestos-synthetic material, Thermoplax, which resists heat up to 600° F. The resistance is 6 ohms and it will carry 1½ amperes. All exposed metal parts polished nickel including screws for mounting. The best rheostat that you can obtain and it costs less than others. Ask your dealers for FADA products.

**FRANK A. D. ANDREA**

MANUFACTURER OF FADA RADIO APPARATUS  
1882-B JEROME AVE., NEW YORK





**"AERIOLA, Jr"**

## **The New Westinghouse Radio Receiver**

**A single-circuit tuner; a supersensitive crystal detector; a fixed condenser; and a set of head telephones, all in one case.**

**Just the outfit to take on camping trips or automobile tours to keep in touch with your home town.**


**Weights only 5 lbs. Wave-length range 190 to 500 meters. Send for Folder 4465.**

**PRICE 25.00**

**WESTINGHOUSE ELECTRIC & MANUFACTURING CO.  
PITTSBURGH, PA.**
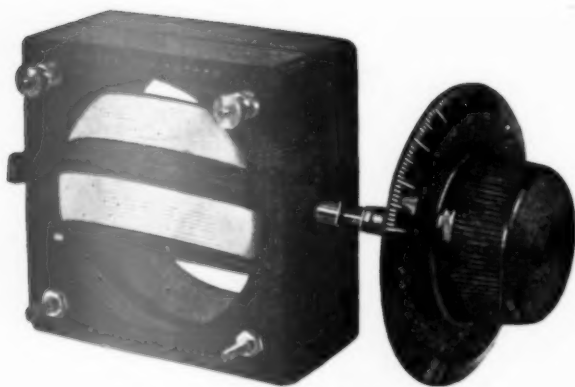
# **Westinghouse**

ALWAYS MENTION Q S T WHEN WRITING TO ADVERTISERS



# TUSKA Moulded Variometer

MECHANICALLY AND  
ELECTRICALLY PEERLESS

TYPE 200.

PRICE \$7.25

SEE THEM AT YOUR DEALER'S

| OTHERS | INDUCTANCE |          | DISTRIBUTIVE CAPACITY |          |
|--------|------------|----------|-----------------------|----------|
|        | MINIMUM    | MAXIMUM  | MINIMUM               | MAXIMUM  |
| No. 1. | 70.3 m.h.  | 940 m.h. | 8.4 mmf.              | 44.1 mmf |
| No. 2* | 75 "       | 440 "    | 22.8 "                | 60. "    |
| TUSKA* | 70.0 "     | 1560 "   | 14.0 "                | 55. "    |

\*Coil wound on OUTSIDE of moulded form. Notice the large distributive capacity for range.


\*Think how EXTREMELY low the DISTRIBUTIVE CAPACITY is in the TUSKA VARIOMETER compared with the EXCEPTIONALLY WIDE range.

Send 5c for C.W. and Variometer Booklets

THE C. D. TUSKA CO., HARTFORD, CONN.

## The McTighe Storage "B" Battery

Patents Pending.

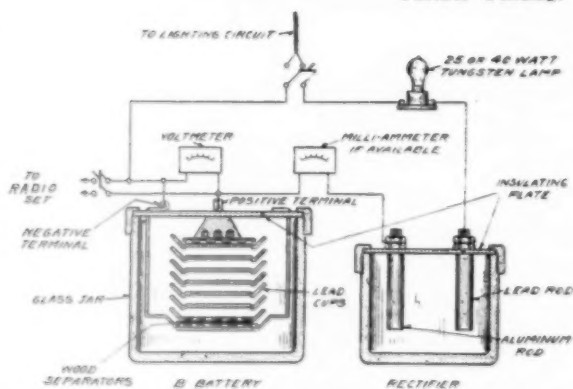

The McTighe Storage "B" Battery consists of 12 cells of the lead acid type giving 24 volts when fully charged. Its capacity, 10 milliamperes for eight hours is ample for using the potentiometer principle for obtaining any desired voltage.

A most satisfactory source of plate voltage for Radiophone and C.W. transmission is obtained by connecting a number of these batteries in series. A 300 volt set can be charged from two rectifiers in series and a transformer with a 400 volt secondary.

The battery and rectifier can be assembled easily and quickly by following the complete instructions which accompany each set of parts. Descriptive leaflet will be sent on request.

### PRICE LIST


|   |        |
|---|--------|
| Set of parts for 12 cell battery without jar..... | \$2.50 |
| Lead aluminum rectifier parts without jar.....    | 1.00   |
| Flint glass jar for battery, 4 x 4 inches.....    | 1.00   |
| Flint glass jar for rectifier, 3 x 3 inches.....  | .75    |

Postpaid.

McTIGHE BATTERY CO., Wilkinsburg, Pa.


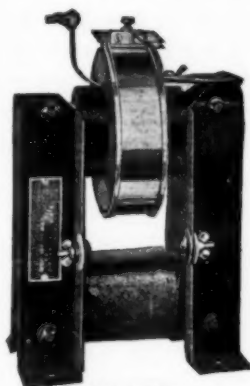
# Important Reductions in Prices of Thordarson Apparatus



TYPE "RS"  
TRANSFORMER

## Type "RS" Transformers


A non-resonant transformer with a lower secondary potential designed to give you the highest possible power factor.

|                          |         |
|--------------------------|---------|
| 1 KVA 15000 VOLTS.....   | \$30.00 |
| 1/2 KVA 10000 VOLTS..... | 20.00   |
| 1/4 KVA 8000 VOLTS.....  | 15.00   |

## Type "R" Transformers

The famous resonant transformer affording the highest practical voltages.

|                          |         |
|--------------------------|---------|
| 1 KVA 25000 VOLTS.....   | \$40.00 |
| 3/4 KVA 10000 VOLTS..... | 28.00   |
| 1/2 KVA 10000 VOLTS..... | 22.00   |

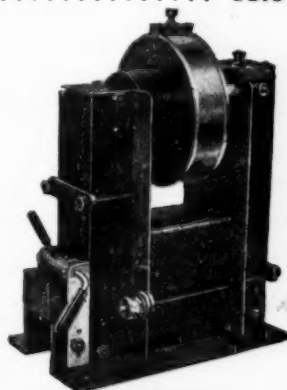

TYPE "R"  
TRANSFORMER

## Other Thordarson Equipment

|                                      |         |
|--------------------------------------|---------|
| POWER CONDENSER (.0018-.009 MF)..... | \$25.00 |
| OSCILLATION TRANSFORMER .....        | 10.00   |
| R8 ROTOR (8 TOOTH).....              | 5.00    |
| R16 ROTOR (16 TOOTH).....            | 5.00    |
| R12 ROTOR (12 TOOTH).....            | 3.00    |

(Specify diameter of motor shaft when ordering rotors.)

A POSTAL BRINGS OUR CIRCULAR TO YOU.

## Thordarson Electric Manufacturing Co.


517 S. JEFFERSON ST.,

CHICAGO, ILL.
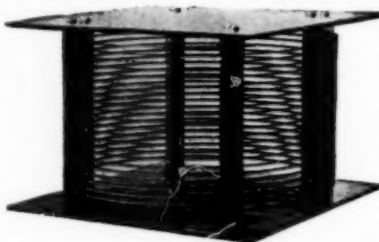
## C-W C-W C-W C-W C-W C-W C-W C-W

Prepare for the bad radio season by installing your CW outfit now. It will carry thru summer static and is ideal for relay work.

OUR C-W CATALOG  
WILL BE READY  
ABOUT MARCH 15th,  
SEND FOR YOUR  
COPY NOW.



OUR NEW C-W  
CATALOG WILL  
BE THE MOST  
COMPLETE AND  
BIGGEST — CW  
ONLY.

CW Inductance No. CW-100 shown above, mounted on Formica exclusively—25 turns edgewise copper strip 3/16 x .050" complete with connection clips, \$10.00.

Send 15 cents for catalog, which amount may be deducted from first order of One Dollar or more.

**"8ZV" WIRELESS MANUFACTURING CO. "8ZV"**  
CANTON, OHIO

### "Chi-Rad" BULLETIN BOARD

#### Knocked Down Variometer Parts.

Read our ad in last month's QST and order your set today. Complete set of parts for two Variometers and Vario-Coupler for only \$10.00. And remember all windings are in place—you have nothing to do but put on the end bearings and connect stator windings together. Guaranteed to be the best value on the market and to give perfect satisfaction when assembled or money refunded. Immediate Delivery—better send us your order right now.

#### The Big A.R.R.L. Convention.

This will be the biggest Radio affair of the year and every Radio-Man should be here during the entire five days, August 30, 31 and Sept. 1, 2 and 3, 1921. Make our store your headquarters, we will gladly show you the latest in apparatus, direct you about the city or put you in touch with other Chicago Amateurs without obligation of any kind. Material and space for letter writing provided free of charge.

Plan on this Convention, make your reservations to the proper authorities AND be sure to visit our booth at the Show—we'll have several surprises for you.

#### A Word About Stock.

We are Chicago and Middle West distributors for all the old reliable makes of Radio Apparatus. We aim to carry the largest and most complete stock in this section of the country and therefore can make Immediate Delivery of almost any desired piece of apparatus. If you are located in the Middle West send us your orders and have the instruments in two to four days. Better yet, if possible drop around and see our display of new apparatus which arrives weekly. All DeForest Interpanel Sets, Midget Radio Phones, etc., in stock. See the new Firth Loud Speaker at only \$23.00.

Blue Print of 4 new C.W. Circuits for 15c. Bulletins of new apparatus free upon request.

### CHICAGO RADIO APPARATUS CO., INC.

C. C. KLENTZ

508 S. DEARBORN ST.,

Phone Harrison 1716.  
(ROOM 210)

L. L. LYNN.

CHICAGO, ILL.

**MAIL ORDER  
"SERVICE"**



Reg. U.S. Trade Mark.

**WE SHIP SAME  
DAY ORDER IS  
RECEIVED**

Our large stock of all reliable makes of Radio apparatus enables us to make immediate Shipment of your orders.

**ANTENNA SWITCHES**

Murdock, 3 pounds.....\$4.50  
Clapp-Eastham, 10 pounds.....12.50

**AERIAL WIRE**

7x22 tinned copper  
100 feet 2 lbs.....\$1.25  
200 feet 4 lbs.....2.40  
500 feet 8 lbs.....6.00

**AMPLIFYING TRANSFORMERS**

A.R. Co. (1 lb.).....\$5.00  
Federal (1lb).....7.50

**"B" BATTERIES**

Radisco No. 1 (2 lbs.).....\$1.50  
Radisco No. 5 (5 lbs.).....2.85  
Eveready Storage Battery  
prices on application

**CONDENSERS TRANSMITTING. (Dubilier)**

No. D-100 250 W. 10,000 V. .007 MF....\$19.00  
No. D-101 500 W. 14,000 V. .007 MF....30.00  
No. D-102 1000 W. 21,000 V. .007 MF... 45.00

**CONDENSERS (Low voltage)**

Western Electric 1MF 500 Volts.....\$1.50  
Western Electric 2MF 500 Volts.....2.25  
No. 21AA Western Elec. 1000 Volts A.C. 2.50  
No. 577 Dubiliere .002 1000 V. ....2.00

**CONTACT POINTS**

CP No. 1, Brass, dozen.....25c  
CP No. 4, Brass, dozen.....35c  
CP No. 5, Nickel Plated.....45c  
Postpaid

**CORWIN DIALS**

No. 66, 3".....\$0.75  
No. 67, 3" with knob.....1.30  
No. 68, 3 1/2".....1.00  
No. 69, 3 1/2" with knob.....1.70  
Postpaid

**GRID CONDENSERS**

Radisco, Postage 3c.....35c

**GROUND OUTFIT**

Consists of SPDT 500 AMP Switch, 25 feet No. 4 wire, clamp and cleats prepaid.....\$7.00

**JACKS AND PLUGS**

Federal Closed Circuit.....\$0.85  
Federal Open Circuit......70  
Federal Double Circuit.....1.00  
Federal Plug.....2.00  
Postpaid

**LOOSE COUPLERS**

Clapp-Eastham Radion.....\$14.00  
Murdock 344.....9.00

6 pounds.

**OSCILLATION TRANSFORMERS**

Radisco No. 5.....\$15.00  
Via. Express collect only

**ROTARY SWITCHES**

Clapp-Eastham No. 19.....\$1.00  
Clapp-Eastham No. 19A......35  
Corwin No. 1......40  
Corwin No. 2......55  
Postage......05

**REGENERATIVE RECEIVERS**

No. CR-1 Grebe 175-680 Meters.....\$90.00  
No. CR-2 Grebe 175-680 Meters.....45.00  
No. CR-3 Grebe "Relay Special" 175-680 Meters.....65.00  
No. CR-3A Grebe With tube control, 175-375 Meters.....45.50  
No. CR-5 Grebe's "Super-Special" 175-3,000 meters, tube control, self-contained. Complete receiving set. Just out.....80.00

**RECEIVERS**

Murdock No. 55, 2000 ohm.....\$4.50  
Murdock No. 55, 3000 ohm.....5.50  
Brandes Superior.....7.00  
Baldwin C.....16.50  
Baldwin E., improved.....20.00  
Brownlie new.....12.00  
Shipping weight, 2 pounds

**RADIO CRAFTS PRODUCTS**

Detector.....\$15.00  
Two step Amplifier.....50.00  
Detector and one step.....45.00  
Detector and two step.....70.00  
Postage Paid

Regen. Receiver, 150-600 M.....\$60.00  
Regen. Receiver, long wave type.....145.00

**TUSKA C.W. APPARATUS**

181 Coil (2 lbs).....\$7.50  
182 Coil (2 lbs).....10.00  
183 Coil (3 lbs).....12.50  
170 Filtr. (8 lbs).....16.00

**VACUUM TUBES**

No. UV-200 Radiotron, detector.....\$5.00  
NO. UV-201 Radiotron, amplifier.....6.50  
UV 202 Radiotron, 5W. power.....8.00  
UV 203 Radiotron, 50W. power.....30.00  
UV 204 Radiotron 250W. power.....110.00

**VARIABLE CONDENSERS**

A.R.CO. .001.....\$6.25  
A.R.CO. .0005.....5.00  
With No. 67 Dial add.....1.00  
Murdock 366.....4.75  
Murdock 367.....4.75  
Murdock 368.....3.75  
Clapp-Eastham 500.....7.50  
Clapp-Eastham 800A.....9.50  
Clapp-Eastham 800B.....11.50  
Complete with dial  
Shipping Weight One Pound

**VARIOMETERS**

Radisco No. 1.....\$7.00  
Radisco No. 1D.....8.50  
3 pounds

**VARIO-COUPLER**

Radisco No. 3.....\$7.50  
Radisco No. 3D.....8.50  
3 pounds

**Philadelphia School of Wireless Telegraphy**

**Note New Address**

**1533 Pine St., Philadelphia**

# SORSINC

22½ VOLT

"B"

BATTERY

4⅞"x5⅞"x8"

## "THE LARGEST "B"—KNOWN"

Behind all this RUGGED CONSTRUCTION—What? The two 19 strand heavy service terminals connect to 15 cells, each 4" long and 1½" in diameter made up into a 12 pound unit that is "CHOCK FULL" of 6400 milliampere hours of energy.

PRICE \$4.00 F.O.B. our N. Y. or Branch Offices Add P.P. Shipping Charges Weight 14 lbs. Write For Folder

If your dealer cannot supply you, order direct from our nearest office

**SHIP OWNERS RADIO SERVICE, INC.**  
80 WASHINGTON ST., NEW YORK CITY

### Branch Offices:

Boston, 175 Commercial St.  
Philadelphia, 201 Parkway B'dg.  
Baltimore, 407 Lobe Bldg.  
Norfolk, 26 Haddington Bldg.  
Savannah, 409 Mendel Bldg.  
New Orleans, 710 Maison  
Blanche Annex.  
London, Eng., 50a Cambridge St., Belgravia, S. W. 1.

Galveston, 313 Amer. Nat'l.  
Ins. Bldg.  
San Pedro, 432 Palos Verdes St.  
San Francisco, 24 California St.  
Portland, Ore., 232 Worcester  
Bldg.  
Seattle, 3451 E. Marginal Way  
Honolulu, 408 Boston Bldg.

Attractive Proposition for Dealers.



RUGGED CONSTRUCTION



## Clear as a Bell The New Bell Rotary Quenched Spark Gap



PRICE \$55.00

Place your order through your dealer

Electrical Supremacy Through Mechanical Perfection Is the Secret of

### THE NEW BELL ROTARY QUENCHED SPARK GAP

Of what value is an electrically correct gap if its bearings are continually wearing out? The Bell Gap Is Built to a Machinist's Ideal as Well as That of the Radio Experimenter's.

THE BELL GAP STANDS INSPECTION AND USE.

**The Electric Machine Co.,**

**Indianapolis, Ind.**



# G "Z-NITH" RADIO APPARATUS

has been reduced in price approximately 15% on each instrument

"OUR LATEST"

O

I

N



Z-NITH MULTICEIVER—MC-3

The prices below represent our contribution toward the reduction of the "High Cost of Radio"

| Instrument                 | Old Price | New Price |
|----------------------------|-----------|-----------|
| Z-Nith Regenerator .....   | \$65.00   | \$55.00   |
| Amplifigon AGN-1 .....     | 75.00     | 64.00     |
| Amplifigon AGN-2 .....     | 105.00    | 89.25     |
| Amplifigon AGN-3 .....     | 135.00    | 115.00    |
| Hyrad Disc .....           | 12.00     | 10.50     |
| Hyrad Non-Syn. Gap .....   | 65.00     | 49.00     |
| Hyrad Syn. Gap .....       | 125.00    | 105.00    |
| Jeweler's Time Rec. ....   | 75.00     | 69.50     |
| Multiceiver MC-3 .....     | 265.00    | 236.00    |
| Altaceiver CW-3 .....      | 300.00    | 254.00    |
| C. R. L. Regenerette ..... | 12.75     | 12.75     |
| One-Step Amp. AM-1 .....   | 33.50     | 28.50     |
| Two-Step Amp. AM-2 .....   | 65.00     | 55.00     |
| Detector AD .....          | 20.00     | 17.00     |
| Detector ADP .....         | 30.00     | 25.00     |

The most complete, efficient and flexible receiver ever designed. Described in detail in our Catalog F-21. Write for it.

D

O

W

N

NEW CATALOG F-21 JUST OUT GIVES COMPLETE LIST OF PRICES

## CHICAGO RADIO LABORATORY

Office and Factory: 6433 RAVENSWOOD AVE.

TESTING STATION 9ZN—5525 SHERIDAN RD.

CHICAGO, ILLINOIS

ALWAYS MENTION Q S T WHEN WRITING TO ADVERTISERS

## Cut Prices Only for a Limited Time

50,000 ft. Aerial Wire just received, 85ft. to the lb. pure copper #14 @ 45c. per lb.  
 Brass Rod, 1/4" sq. @ 12c. per ft.  
 1/8" round or square @ 8c. per ft.  
 Series—Parallel Panel Switches 83c. ea.  
 Hard Rubber Binding Posts @ 10c. ea.  
 Buzzer, key and code, mounted on one base, best for code practice \$2.49.  
 A real wireless Key, mounted \$1.50.  
 Pancake Helix (Signal Type) \$2.25  
 C.W. Inductance Coils for 250 watt \$6.00.  
 Loading Inductance \$3.25.  
 3600 Meter Loose Coupler \$10.95  
 600 Meter Loose Coupler \$5.90.

VT Receptacles \$1.00 ea.  
 Radiotrons: Detector \$4.90  
 Amplifier \$6.40  
 Variable Grid Leaks,—necessary to use with Radiotrons, 60c.  
 Fixed Grid Cond. 33c.  
 Porcelain Rheostats for Panel \$1.00; for table, 85c.  
 Nickel Binding Posts, good for Phones, large, 11c.; small 9c. ea.  
 Small size "B" Batteries, Ace type, \$1.00.  
 Nov. date "B" Batteries 50c.  
 New Type Eveready "B" Battery, large, tapped each cell \$2.75.

J J N Variometers . . . . . \$4.00


J J N Variocouplers . . . . . 4.50

# 10% DISCOUNT

FROM LIST PRICE  
 TO  
 RADIO CLUBS

AMERICAN ELECTRIC & WIRELESS SUPPLY COMPANY

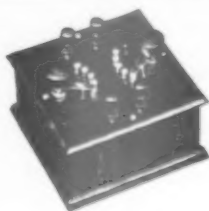Mail all orders direct to 602 W. 145th St., N. Y. C., Dept. Q.



## TRESCO TEN \$ TUNERS

When you think of tuners say TRESCO. One for every need and wave length.

CIRCULAR FREE.

### Knocked-Down Condensers

Assemble them and save money.

11 Plate . . . . . \$1.80  
 21 Plate . . . . . 2.25  
 41 Plate . . . . . 3.20 Add P. P.



If you want us to assemble them for you add \$1.00, plus P.P., to above prices. Shipping weight 2 lbs.

10c brings a wonderful catalog of 16 pages. 100 testimonials and freak hook ups for our tuners.

**TRESCO - - - Davenport, Iowa**

## SIX Stages of audio frequency amplification!

See John Firth & Co's August advertisement.

## ? No. 7600 ?

# Radio Telephone and Telegraph Apparatus of Merit

## JUNE AND JULY BARGAINS

|  |        |
|--|--------|
| Unmounted Amplifying Trans-<br>formers .....   | \$3.45 |
| Panel Mount Rheostats .....                    | 1.35   |
| Honeycomb or Duolateral Coils<br>20% Discount  |        |
| Moulded Gooseneck VT Sockets                   | 1.75   |
| D-101 Dustproof Galena De-<br>tectors .....    | \$2.15 |
| Variable Grid Leaks—G-100..                    | .55    |
| Hard Rubber 180° Dials with-<br>out Knob ..... | .45    |
| Hand Key—1K.W. Silver Con-<br>tacts .....      | 2.95   |
| Amrad Panel Rheostats .....                    | 1.45   |

## FAMOUS "K" INSTRUMENTS

|   |         |
|---|---------|
| K20—Enclosed Rotary Gaps                        |         |
| 20a—With Motor .....                            | \$25.00 |
| 20b—Pulley Drive .....                          | 20.00   |
| K1—Open Rotary Gap with<br>motor .....          | 16.00   |
| K2—16 pt. Sawtooth rotor ...                    | 4.50    |
| K3—10pt. Wide tooth rotor ...                   | 4.50    |
| K6—"Cootie" Double Action<br>Key .....          | 4.50    |
| K8—"Big Midget" Audion Cab-<br>inet .....       | 12.50   |
| K7b—Honeycomb Tuner and<br>two condensers ..... | 29.50   |
| K4e—Audion Detector Cabi-<br>net .....          | 25.00   |

## CONDENSERS

|  |        |
|--|--------|
| DeForest Condensers—All Styles for immediate<br>Shipment |        |
| #366 Murdock .001 in case .....                          | \$4.75 |
| #366 Murdock .001 Interior .....                         | 4.25   |
| #368 Murdock .0005 in case .....                         | 4.00   |
| #368 Murdock .0005 Interior .....                        | 3.50   |
| #3662 Murdock .001 Panel Mount .....                     | 5.00   |
| #K10 Chelsea Panel Mount with Dial .....                 | 4.75   |
| Perfection Knock Down Condensers                         |        |
| 11 Plate \$1.80, 21 Plate \$2.25, 41 Plate \$3.20        |        |

## TELEPHONES

|                              |         |
|------------------------------|---------|
| Baldwin Type E .....         | \$20.00 |
| Baldwin Type F .....         | 21.00   |
| Baldwin Type C .....         | 16.50   |
| Brandes Navy Type .....      | 14.00   |
| Brownlie Adjustable .....    | 12.50   |
| Liberty 2200 Ohms .....      | 12.50   |
| Trans-Atlantic Brandes ..... | 12.00   |
| Brandes Superior .....       | 8.00    |
| Murdock #55—3000 Ohms .....  | 5.50    |
| Murdock #55—2000 Ohms .....  | 4.50    |
| Brown adjustable .....       | 17.00   |

## VACUUM VALVES

|                                  |        |
|----------------------------------|--------|
| UV 200 Radiotron Detector .....  | \$5.00 |
| UV 201 Radiotron Amplifier ..... | 6.50   |
| UV 202 5 Watt Transmitter .....  | 8.00   |
| UV 203 50 Watt Transmitter ..... | 30.00  |
| C300 Audiotron Detector .....    | 5.00   |
| ER Detector Tube .....           | 6.00   |
| APVT Amplifier .....             | 7.00   |
| APTT 5 Watt Transmitter .....    | 7.50   |

## TRANSFORMERS

|   |         |
|---|---------|
| Acme 250 Watt semi mounted .....        | \$13.00 |
| Acme 250 Watt fully mounted .....       | 16.00   |
| Acme 500 Watt semi mounted .....        | 18.00   |
| Acme 500 Watt fully mounted .....       | 22.00   |
| Acme 1000 Watt semi mounted .....       | 24.00   |
| Acme 1000 Watt fully mounted .....      | 33.00   |
| Thordarson Type R-1/2 KVA .....         | 22.00   |
| 1500 Volt Acme Power Transformer .....  | 25.00   |
| Thordarson Type RS-1/4 KVA .....        | 15.00   |
| 200 Watt C.W. Power Transformer .....   | 20.00   |
| Same semi mounted .....                 | 16.00   |
| 50 Watt C.W. Power Transformer .....    | 15.00   |
| Same semi mounted .....                 | 12.00   |
| Unmounted Modulation Transformers ..... | 4.50    |
| Mounted Amplifying Transformers .....   | 5.00    |

## REGENERATIVE RECEIVERS

|                                   |        |
|-----------------------------------|--------|
| Clapp-Eastham Variometers .....   | \$5.75 |
| Clapp-Eastham Variocouplers ..... | 7.50   |
| Amrad Variometers .....           | 14.50  |
| Amrad Variocouplers .....         | 17.50  |
| Murdock Variometers .....         | 7.50   |
| Murdock Variocouplers .....       | 8.50   |
| Grebe Regenerative CR-3 .....     | 55.00  |
| De Luxe Regenerative DX-1 .....   | 35.00  |
| (All Bakelite Variometers)        |        |

## METERS

|  |        |
|--|--------|
| Model H Flush Mount Radio Frequency Meters   |        |
| 0-1, 0-3, 0-5, 0-10 .....                    | \$7.00 |
| Midget Flush Mount Milli-ammeters 0-100, ... |        |
| 0-200 .....                                  | 8.00   |
| #471 0-5 Ammeters .....                      | 5.50   |
| #471 0-200 Milliammeters .....               | 5.50   |

*All In Stock for Immediate Delivery.*

Our laboratory and workshops are adequately equipped to satisfy your most exacting requirements in the construction or assembly of special receivers, spark and C.W. Transmitters, or radio telephone sets. Specifications and estimates will be furnished without charge

*For 55 Page Illustrated Catalog—Send 4c in Stamps to*

## KARLOWA RADIO COMPANY

Office—611 Best Bldg.

ROCK ISLAND, ILL.

*Distributors for*

DeForest Radio Tel. & Tel. Co.  
Wm. J. Murdock Co.  
Amrad Products

Acme Apparatus Co.  
Radio Corporation of America  
Chelsea Radio Co.

# Variometer Parts Complete

ONLY  
\$4.<sup>00</sup>

Stators Already Wound.  
All Holes Drilled.  
Will Not Shrink or Warp.  
Blue Prints and Instructions.

## DEALERS

We are recognized distributors for the Radio Corporation of America. Get your Radiotrons from us at regular Dealers' Discounts. All orders shipped same day as received.

**GET** Our New 150 Page Catalog  
Sent for 10c in Stamps or Coin  
Catalog Gives  
C.W. Hookups; tells amateur what is needed for every type set. Highest Grade Catalog Published.

# 10<sup>c</sup>

## The Marshall-Gerken Co.

127 Radio Bldg.,

Toledo, Ohio



## Chelsea Variable Condensers

(Die Cast Type)

| No. | Capacity  | Type         | Size                  | Weight     | Price  |
|-----|-----------|--------------|-----------------------|------------|--------|
| 1   | .0011m.f. | Mounted      | 4 5/8 x 4 5/8 x 3 1/4 | 1 3/4 lbs. | \$5.00 |
| 2   | .0006m.f. | Mounted      | 4 5/8 x 4 5/8 x 2 5/8 | 1 1/4 lbs. | 4.50   |
| 3   | .0011m.f. | With Dial    | 4 1/4 x 3 x 4         | 2 lbs.     | 4.75   |
| 3   | .0011m.f. | Without Dial | 4 1/4 x 3 x 4         | 2 lbs.     | 4.35   |
| 4   | .0006m.f. | With Dial    | 4 1/4 x 3 x 3 1/2     | 1 1/4 lbs. | 4.25   |
| 4   | .0006m.f. | Without Dial | 4 1/4 x 3 x 3 1/2     | 1 1/4 lbs. | 3.85   |

Top, bottom and knob are genuine bakelite, shaft of steel running in bronze bearings, adjustable tension on movable plates, large bakelite dial reading in hundredths, high capacity, amply separated and accurately spaced plates.

Unmounted types will fit any panel and are equipped with counter-weight.

Purchase from your dealer; if he does not carry it, send to us. Bulletin sent upon request.

## Chelsea Radio Co., 15 Fifth St., Chelsea, Mass.

Manufacturers of Radio Apparatus and Moulders of Bakelite.

"EVERYTHING IN RADIO"

WESTERN RADIO ELECTRIC COMPANY

SEND FOR OUR MARCH

STOCK BULLETIN AND PRICE LIST

550 South Flower Street,

Los Angeles, Cal.



**3 \$1  
for 1**



## PROTECT YOUR VACUUM TUBES INDEFINITELY!

### *Multiplies the Life of your Set*

Destructive excessive amperage cannot reach the delicate filaments of any vacuum tube if protected by a

**Radeco**

### **SAFETY FUSE**


*Pat. Pending.*

Slips directly on filament terminals of any standard socket without distorting springs or lowering efficiency. **RADECO** Safety Fuses positively protect your tubes indefinitely.

Carrying Capacity  
1. 1 1/4, 1 1/2, 2, 2 1/4 and 3 amp.  
Size 1/4 inch over all.

**RADECO** Safety Fuses are equally valuable in all C. W. work preventing injury to meters resulting from shorts. Send today cash, money order or certified check.

**3 for  
\$1  
35c. each**

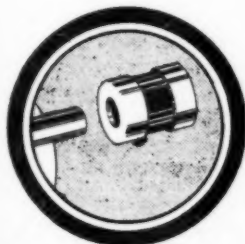

**FROM YOUR DEALER OR BY  
MAIL**

### **FILAMENT RHEOSTAT**



For Back or Front of Panel Mounting. 6 ohms, 1 1/4 amps., 1 1/4" d'a.

**\$1.75 Post Paid**  
*Immediate Shipment.*

Standard VT Socket  
*Improved Contact Type*

**\$1.00 Postpaid**  
Copper foil condenser  
35c P. P.

### **44 V. Variable "B" Battery \$3.60**

Include postage on 4 lbs.

Complete in handy wooden case and adjustable phosphor bronze "jiffy" connectors. Better than block batteries—if one 4.4 V. unit weakens prematurely, it can be removed and replaced—thereby not impairing total voltage, which makes this the best battery value to be had at any price. Set of 10 Renewal Units, 44 volt, \$3.10 postpaid.

Just the thing for C.W. work.

### **AERIAL WIRE 1c. Per Foot**

7 strands No. 22 copper—tin plated to prevent oxidation. Maximum radiation and strength. Include postage on 15 lbs. per 1000 ft.

### **GROUND WIRE 7c. Per Foot**

No. 4 solid copper—rubber covered—triple braid—include postage on 20 lbs. per 1000 feet.

100 amp. 600 volt lightning switches, \$4.00

### **ASSEMBLE YOUR CW. & PHONE SET NOW**

**We Have the Complete Parts**

|  |             |
|--|-------------|
| Power Tubes: G. E., Cunningham 5 Watt.....                 | each \$3.00 |
| G. R. V.T. Sockets.....                                    | each 1.75   |
| G. R. Filament Rheostat, 2 1/2 amp.....                    | each 2.50   |
| Acme C.W. Power Transformer, 50 Watt.....                  | each 15.00  |
| Acme Choke Coils, Double Coil.....                         | each 8.00   |
| Acme Modulation Transformer, semi-mounted.....             | each 5.00   |
| Western Electric 1 mfd. Condenser; tested 1,000 volts..... | each 2.50   |
| Conn. Telephone Transmitter.....                           | each 3.50   |
| Radiation Ammeter; Jewell, 0-1 amp.....                    | each 6.00   |
| Radiation Ammeter, General Radio, 0-1, 0-1 1/2.....        | each 7.75   |

## **RADIO EQUIPMENT CO.**

**630 Washington Street,**

**(4th Floor)**

**Boston**

## CO-OPERATIVE RADIO PURCHASING

Members of this association participate in the profits which have accrued through their own and fellow amateurs combined purchases. In addition to this dividend our service is unexcelled. You also can secure this service and share

in our profits. Order direct from this ad or send a stamp for full particulars. Remember "We take pride in our service." The items listed below are but a few of the items which are carried in stock..

### RADIOTRON TUBES

UV-200 Gas Content Detector \$5.00  
UV-201 Pilotron Amplifier..6.50  
UV-202 5 Watt Transmitter..8.00  
(We supply full directions with either detector or amplifier.)

### AMPLIFYING TRANSFORMERS

Clapp-Eastham type QO unmounted..... 4.00  
Clapp-Eastham type QO mounted..... 6.50  
Acme A2 with binding posts 5.00  
Acme core & coil assembled 4.50  
Acme A2 fully mounted.... 7.00  
U.V. 712 List Price..... 7.00  
Mfg. by Radio Corp. of America.

### CONDENSERS

Connecticut .001 encased...\$6.50  
Connecticut .001 panel type.. 6.50  
Chelsea No. 1 encased..... 5.00  
Chelsea No. 2 encased..... 4.50  
Chelsea No. 3BD with dial for panel..... 4.75

Chelsea No. 4BD with dial for panel..... 4.25  
Murdock No. 366 .001 encased..... 4.75  
Murdock No. 367 .0005 encased..... 4.50

### TELEPHONES

Brandes Superior with Navy Band.....\$8.00  
Brandes Trans-Atlantic with Navy Band.....12.00  
Brandes Navy type with Navy Band.....14.00  
Western Electric type 1002A 15.00  
Murdock No. 55, 2000 ohms 4.50  
Murdock No. 55, 3000 ohms 5.50

### SHORT WAVE SET MATERIAL

Clapp-Eastham ZRV Variometer, without dial.....\$5.75  
Clapp-Eastham ZRV Variometer with 3-inch dial.... 6.50  
Clapp-Eastham ZRC Variocoupler, with knob & dial 7.50  
Clapp-Eastham ZRC Variocoupler, with switch and points..... 9.00  
J. J. Nightingale Variometer 4.50

J. J. Nightingale Variocoupler 5.00  
Murdock G or P Variometer No. 345..... 7.50  
Murdock Variocoupler No. 346 8.50

### AUDION CONTROLS

Clapp-Eastham ZRD detector panel.....\$12.00  
Acme Y-1 detector..... 10.00  
Adams Morgan No. 70 control..... 6.00

### C. W. TRANSFORMERS

Acme 200 watt mounted....\$20.00  
Acme 50 watt mounted..... 15.00

### MODULATION TRANSFORMERS

Acme A-3 semi mounted... \$5.00

### CHOKE COILS

150 M.A. Single coil..... \$4.00  
150 M.A. double coil..... 6.00  
500 M.A. single coil..... 6.00  
500 M.A. double coil..... 8.00

### FILAMENT HEATING TRANSFORMERS

75 watt mounted.....\$12.00  
150 watt mounted..... 16.00

**MUTUAL PURCHASERS ASSOCIATION**  
Dept. Q, 2 Stone Street, New York City

## Quality Radio Equipment

New Grebe Portable

Radio Station Type KT-1

**Especially Adaptable and Efficient for Boy Scouts, Campers and Tourists.**

Absolutely the newest and neatest combination Transmitting and Receiving Portable Outfit on the market. Complete with Grebe CR-5 Receiver, Transmitter, Vacuum Tubes, Batteries and Head Set in attractive and durable case.

**\$175.00 COMPLETE**

Full line of Radiotron Vacuum Tubes and Accessories, and other Highest Grade Radio Supplies

Dealer's Special Proposition—Mail orders promptly filled.

**DOUBLEDAY-HILL ELECTRIC CO.**

715 12th St., N. W., Washington, D. C. Radio Dept.—Desk A 719-21 Liberty Ave., Pittsburgh, Pa.



**Best of Everything in  
Radio Apparatus and Parts.**

Send Stamp for Catalog "Q"

**J. H. BUNNELL & CO.**

32 Park Place,

New York

### CANADIAN AMATEURS

Deal in Canada and Save \$\$\$\$

The Leading Amateur Supply House for  
**WIRELESS**  
Apparatus and Parts.

Send 5 cents for our list.

**THE VIMY SUPPLY CO.**

567 COLLEGE ST.,

TORONTO

KENNEDY  
EQUIPMENT

# ANNOUNCING

## THE NEW KENNEDY UNIVERSAL REGENERATIVE RECEIVER

TYPE 110

**EFFECTIVE RANGE: 175 TO 25,000 METERS**

DETECTS  
REGENERATES  
OSCILLATES  
On all wave  
lengths in  
common use.



Licensed  
under  
Armstrong  
U. S.  
Patent  
No. 1,113,149

**Surpassing** even our highest hopes when we undertook its development, this latest addition to the Kennedy line is of interest **to everyone who uses a radio receiving set.**

Our engineering staff spent many months in developing this unit and released it for production only when its performance surpassed every requirement we had set for it. By our long specialization in receiving equipment we have built up a reputation which is so precious that we can afford to put the Kennedy trade-mark on only the highest quality product.

We have spared no effort to make this the best receiver on the market. We honestly believe that it is.

**These are some of its features:**

- Variable inductive coupling between primary and secondary.
- Extremely sharp tuning because of very efficient inductance units.
- Special Kennedy bank-wound moisture-proof inductors.
- Generous overlap between inductance steps.
- Large balanced primary and secondary variable condensers.
- Micrometer adjustment of secondary condenser
- Variable grid condenser with air dielectric, permitting most effective use of all types of available receiving tubes.
- Adjustable feed-back circuit.
- Fine adjustment of plate voltage by means of potentiometer connected between terminals of filament battery.
- Weston ammeter for measuring filament current.
- Bus-bar type insulated wiring.

*Further details in Bulletin 101, mailed on request.*

Ask your dealer for a demonstration. Compare the performance of this receiver with any other you have ever seen. The users of Kennedy Equipment are our best advertisers.

**THE COLIN B. KENNEDY COMPANY**


INCORPORATED

RIALTO BUILDING

SAN FRANCISCO



TYPE 156 SOCKET

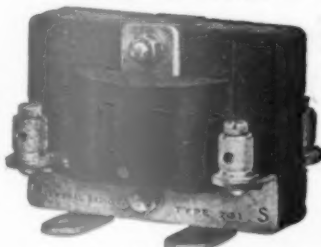

TYPE 231 TRANSFORMER

## Rebuilding Your Set For Results

Summer is the season in which to rebuild your set so that you may get the maximum of results during next winter. By rebuilding your set now, you will have more time in which to look over all of the available radio apparatus and to make a careful selection of those instruments most suited to your needs.

We have several instruments built particularly for the discriminating experimenter. In making your selection, we invite you to consider these instruments. They are fully described in Bulletin 904Q, copy of which will be sent on request. Prominent among these instruments are the following:

### TYPE 156 VACUUM TUBE SOCKET \$1.75

Adapted for Receiving or transmitting tubes. Positive contact springs.

### TYPE 214 RHEOSTAT \$2.50

Made for receiving and transmitting tubes, and panel and portable mountings.

### TYPE 231A AMPLIFYING TRANSFORMER \$5

Designed to give the maximum amplification possible with a UV-201 tube.

### TYPE 231M MODULATION TRANSFORMER \$5

Designed to give the maximum modulation possible without distortion using a UV-202 tube.

### TYPE 127 HOT WIRE METERS \$7.75


Flush or front of board mountings, and a variety of ranges. For filament and antenna currents.

Your dealer can obtain a complete supply of the standard parts, such as switches, binding posts, etc. used in the assembly of our instruments.

*Standardize on General Radio Equipment Throughout.*
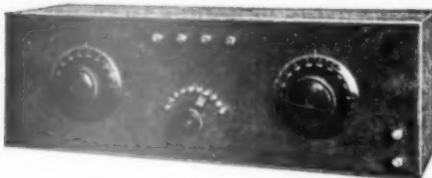
## GENERAL RADIO COMPANY

MASSACHUSETTS AVENUE AND WINDSOR STREET, CAMBRIDGE, 39, MASSACHUSETTS



## A.R.R.L. MEN!

150 TO 25,000 METER REGENERATIVE RECEIVER IS HERE—THE "REGENIFIER"

The most remarkable, as well as welcome, piece of radio apparatus has been developed! No longer is it necessary to change wires and connections or plug in numerous coils, to get all the stations. The Regenifier is the latest innovation of the popular regenerative circuit and applies this unapproachable circuit to a wavelength range covering every wavelength used, without the sacrifice of sensitivity or efficiency on any of the wavelengths covered. It is a marvel for C.W. reception.

### THE REGENIFIER

#### THREE MODELS

150 to 475 meter Regenifier

Only \$48

150 to 4000 meter Regenifier

Only \$68

150 to 25,000 meter Regenifier

Only \$98

DEALERS WRITE.

In operation it is the last word in simplicity. Has only three controls each being variable over entire wavelength scale, there being no change-over from short to long waves. Its super positive control of oscillations and amplification together with its remarkable flexibility of operation has destined it to become the property of every exacting radioman. Encased in genuine Oak Cabinet 7x7x21 inches; panel Bakelite, four inch dials used, all metal parts highly nickelled.

No matter what model you buy, for any wavelengths you desire, the Regenifier will prove superior to any other receiver of similar nature. Each instrument guaranteed for two years. Order YOUR Regenifier at once.

Send For Circular

Glenhurst Research Laboratories,

Omaha

## SAVE A DOLLAR

THE BIG THREE "QST," "RADIO NEWS," "PACIFIC RADIO NEWS." ONE YEAR SUBSCRIPTION TO ALL THREE.

\$5

PACIFIC RADIO PUB.CO.

50 MAIN ST.

SAN FRANCISCO

? No. 7600 ?




# how to find out-


A-P Tubes have been imitated but never equalled. Those who use them **know**. Read this letter. Scarcely a day passes but what we receive, unsolicited, enthusiastic testimonials similar to the following:—

Gentlemen:—"We have recently received a shipment of E.R.'s and Amplifier oscillator tubes. It is our policy to test out all tubes received, under actual operating conditions. They were absolutely the finest bunch of tubes we ever received. It is indeed a pleasure to be able to sit down and with a clear conscience write a letter stating that we are at last receiving really good tubes for the amateur." THE PRECISION EQUIPMENT CO., 2347 Gilbert Ave., Cincinnati, Ohio, by H. F. Brickel, Vice President.

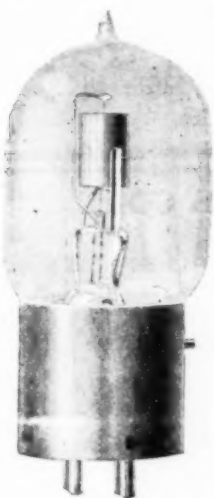
*A-P Tubes are licensed by the Radio Corporation of America under the DeForest Audion and Fleming patents for amateur and experimental use in Radio communication.*



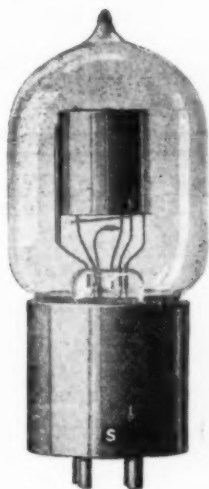THE A-P VT  
AMPLIFIER-OSCILLATOR  
—the amplifier used by the  
U. S. Navy. "Use the tube  
the Navy uses." Price \$7.



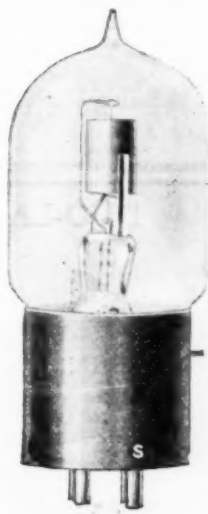THE A-P  
ELECTRON RELAY  
—the most sensitive detec-  
tor of spark signals known  
to the radio art. Price \$6.



THE A-P  
TRANSMITTER TUBE  
—an efficient undamped  
wave transmitter for use  
in radio-telephony. Price  
\$7.50.


Order from your dealer or write direct. And for the best book on Radio ask your dealer for "Elements of Radiotelegraphy," by Lieut. Ellery W. Stone, U. S. N., or order direct from—

**The Atlantic Radio Supplies Co. 8 Kirk Place, Newark, N. J.**  
**The Pacific Radio Supplies Co. 638 Mission St. San Francisco, Cal.**

## use A-P tubes for efficiency

## THE NEW INTER-TUBE AMPLIFYING TRANSFORMER

Model  
U. V. 712  
Price \$7.00

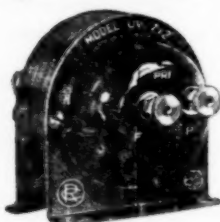

For use with  
Radiotrons  
U. V. 200  
and U. V. 201

After many months of experimental work the General Electric Company has produced an inter-tube transformer of exceptional efficiency. This is Model U. V. 712 which we take pleasure in introducing.

with noisy amplifying circuits are urged to try this new transformer and thus convince themselves of its superiority.

Write for our new special bulletin showing the use of amplifying transformer U. V. 712.

Experimenters who are troubled

**Radio Corporation**  
of America

Sales Division, Commercial Department, Suite 1803  
233 Broadway, New York City

## DUO-LATERAL INDUCTANCE COILS



|                    | Turns | Wave Length | Price  |                          |
|--------------------|-------|-------------|--------|--------------------------|
| LOW NATURAL PERIOD | 25    | 130-250     | \$0.50 | LOW DISTRIBUTED CAPACITY |
|                    | 35    | 180-450     | .55    |                          |
|                    | 50    | 250-700     | .60    |                          |
|                    | 75    | 400-900     | .65    |                          |
|                    | 100   | 500-1400    | .70    |                          |
|                    | 150   | 600-2000    | .75    |                          |
|                    | 200   | 1000-2500   | .80    |                          |
|                    | 250   | 1200-3500   | .85    |                          |
|                    | 300   | 1500-4500   | .90    |                          |
|                    | 400   | 2000-5000   | 1.00   |                          |
|                    | 500   | 3000-6000   | 1.20   |                          |
|                    | 600   | 4000-10000  | 1.40   |                          |
|                    | 750   | 5000-12000  | 1.60   |                          |
|                    | 1000  | 8000-15000  | 1.85   |                          |
|                    | 1250  | 10000-20000 | 2.40   |                          |
|                    | 1500  | 15000-25000 | 2.80   |                          |

EMPYREAN QUALITY THRU-OUT BACKED BY THE EMPYREAN GUARANTEE OF SATISFACTION OR YOUR MONEY BACK—USED IN CONNECTION WITH OUR VARIABLE CONDENSERS AND SPECIAL TURRET COIL MOUNTING, THEY COMPLETE A LONG DISTANCE RECEIVER UNEXCELLED BY EQUIPMENT COSTING THREE TIMES AS MUCH.

Bulletin for a 2-cent stamp.

**EMPYREAN RADIO COMPANY, 159 N. State St., Chicago, Ill.**

## BUZZERS

for all radio work. External tone adjustments.

Satisfaction guaranteed  
"RADIO'S BEST BUY"

60c POSTPAID 60c

**AJAX ELECTRIC CO.**

Palmer St.,

Cambridge 38 Mass.

**SIX Stages of audio frequency amplification!**

See John Firth & Co.'s August advertisement.

# Summertime Radio

No need for you to shut up shop when Summer comes, that is, if you own a



**KT-1  
Portable**

Licensed  
Under the  
**ORIGINAL**  
Armstrong Patents.

At last here's the outfit that makes Summer radio work a pleasure.

Take it out into the country and send up a few hundred feet of antenna on a Grebe Radio Kite, and surprise yourself at its range.

Find out the range of your home station.

Central Radio Co., Inc., Kansas City, Mo.  
Continental Radio and Electric Corp., New York  
Detroit Electric Co., Detroit, Mich.  
Doubleday-Hill Electric Co., Pittsburgh, Pa.  
Electrical Specialty Co., Columbus, Ohio  
Holt Electric Utilities Co., Jacksonville, Fla.  
Hurlburt Still Electrical Co., Houston, Texas  
Kelly and Phillips, Brooklyn, N. Y.  
Klaus Radio Company, Eureka, Ill.

Hickson Electric Co., Inc., Rochester, N. Y.

If you live near a body of water, procure a canoe or row boat and you have a ship station that sails under power of your kite.

Then, when Winter comes again, merely replace the CR-Regenerative Receiver in its cabinet and use it in your station for *real results*.

See it at your Dealer's, today!

Manhattan Electrical Supply Co., New York,  
Chicago, St. Louis.

Leo J. Meyberg Co., San Francisco, Cal.

J. H. Bunnell & Co., New York City

F. D. Pitts Co., Inc., Boston, Mass.

Philadelphia School of Wireless Telegraphy,  
Philadelphia, Pa.

The Newman-Stern Co., Cleveland, Ohio

Western Radio Electric Co., Los Angeles, Cal.

**A. H. GREBE & CO., Inc.**

**74 Van Wyck Blvd., Richmond Hill, N.Y.**

## KNOW THE TRUTH-- STOP GUESSING

EQUIP WITH A

# Weston

### Model 425 Thermo-Ammeter



Flange diameter,  $3\frac{1}{4}$  inches  
Body diameter,  $2\frac{1}{8}$  inches  
Scale length, 2.35 inches

to measure the radiation current and be certain that you are putting current into the aerial.

Model 425 is a small size instrument harmonizing with all other standard radio equipment. It possesses exceptional characteristics which make it the ideal instrument for radio service; its low power consumption allows the greatest possible energy to be put into the aerial; its 50% safe overload capacity is a protection against accidental burn-out; its size is conservative of space; it operates on either audio or radio frequencies.

Information Will Be Furnished on Request

### WESTON ELECTRICAL INSTRUMENT COMPANY

158 Weston Avenue, Waverly Park, Newark, N. J.

Offices in principal cities throughout the world.

## Cunningham and Radiotron Tubes



|                    |   |   |   |   |        |
|--------------------|---|---|---|---|--------|
| DETECTORS          | - | - | - | - | \$5.00 |
| AMPLIFIERS         | - | - | - | - | \$6.50 |
| 5 WATT POWER TUBES | - | - | - | - | \$8.00 |

We Stock a Complete Line of Acme, Clapp-Eastham, Murdock, DeForest, Moorhead, Remler, Grebe, Amrad, Baldwin, Burgess, and Apparatus of Many Other Makes.

Send for Our Special Tube and Combination Offers.



### WHITALL ELECTRIC COMPANY

Call Letters 1IAP

WESTERLY, R. I.

### SOMETHING NEW!

A Log-book for the Citizen Radio Station Operator, in which he can keep a complete record every day of stations heard and worked. We can also supply an entirely new card system, one a plain postal card with your call letters printed on it, the other a double card, having a return acknowledgment postal for confirmation.

### C. B. CLARK AND SON

P. O. Box 246,

Red Bank, N. J.



# RED-HEAD Radio 'Phones

NOW \$8.00

Complete  
Postpaid to  
Any Address

Price cut from \$12.50 to  
to \$8.00  
At one Big Slash!

Buy Now---Profit by our  
bigger sales and lower  
costs

IMPROVED 1921 MODEL  
3000 Ohms

Latest and best we ever made

HIGHER QUALITY AT A LOWER  
PRICE

Newman-Stern sets the pace back to normal! The self-same Red-Head which literally swept the country and sold everywhere at \$12.50 are now yours for only \$8.00. They were admittedly the world's best buy at \$12.50; they have absolutely no competition at this new, low, bed rock price of \$8.00.

The reasons we can make this cut are, briefly: Bigger sales and greater production. Lower manufacturing costs. A determination to bring prices back to normal. To put Red-Head quality within reach of every experimenter.

The new and improved 1921 Red-Heads are as rugged and sturdy as ever—but even more exquisitely sensitive. The same snug fit; the same high grade minutely accurate interior. The same handsome, well finished appearance—but wound to a higher resistance. They are now better than they have ever been before, during five years of leadership.

When we first made Red-Heads we challenged every user to test them out in competition with his favorite receiver; scores of letters from delighted users prove Red-Head superiority in tone and sensitiveness. You will say the same. Try them under our guarantee; we refund your money if they are not just as represented.



## SPECIFICATIONS

3,000 Ohms resistance (each receiver 1500 Ohms) wound with electrolytic copper wire of the highest grade; the best magnet steel available is used—and plenty of it; cast aluminum backs; genuine Bakelite unbreakable ear caps; furnished with braid-covered military type or genuine phosphor-bronze split head-band, extra fine 6 ft. cord with strain loops and posts; cord connections made on outside of receiver, easily adjusted without tampering with carefully adjusted interior; interior parts are highly nicked and polished. Remember the ear caps fit snug and are practically unbreakable.

## ARLINGTON TESTED CRYSTALS



NOW 25 CENTS  
(Reduced from 35c.)

NAA (Arlington) tested minerals are the original tested crystals—absolutely the best that money can buy for radio detector and wave meter work. Exquisitely sensitive.

We scour the world for the best obtainable raw material, we secure scores of samples from every known source of supply and select only those of just the right crystalline structure for perfect radio work.

Each crystal is cut into right detector size, tested for sensitiveness and only those found perfect are good enough for us to sell you. Each "Arlington" is carefully wrapped in foil, packed in a convenient lithographed metal container and comes to you perfect.

SOLD BY REPUTABLE DEALERS EVERYWHERE

Any of the above articles sent postpaid on receipt of price.  
Dealers: Write at once for our New Proposition on Red-Heads.

We pay all transportation charges on ALL goods that we ship.

**The Newman-Stern Co.**

Send for catalog on Electrical supplies. Wireless Goods, Athletic Goods, Toys, &c.

Newman-Stern Bldg

Cleveland, Ohio

## OUR BROAD GUARANTEE

We rely upon the fairness of our customers. A refund or satisfactory adjustment will be made for any merchandise not found entirely satisfactory by you, its purchasers. You are to be the sole judge. Your decision will be ours.

Increase your receiving range with an Arlington. To avoid the many imitations, look for the signature of J. S. Newman on each box.

## WE DISTRIBUTE THE REPUTABLE RADIO PRODUCTS OF LEADING MANUFACTURERS

Being one of the very oldest firms in the country dealing in radio apparatus the best manufacturers have appointed us as their distributors. We list a few of the well-known companies we represent: Remler, Murdock, DeForest, General Radio, Amrad, Grebe, Acme, Federal, Radio Corporation, Magnavox, Burgess, Signal, Federal, Baldwin, Tuska, Corwin, Adams-Morgan.

## IMMEDIATE DELIVERY Prices Include Postage

|  |        |
|--|--------|
| UV-200 Radiotron.....                  | \$5.00 |
| UV-201 Radiotron.....                  | 6.50   |
| UV-202 Power Tube.....                 | 8.00   |
| P1 Corwin Dial, with Knob              | 1.30   |
| P2 Corwin Dial, less knob..            | .75    |
| 981 Tuska Variometer.....              | 6.25   |
| 810 Remler Panel Rheostat..            | 1.00   |
| 1421-W Federal Open Circuit Jack ..... | .70    |
| 1423-W Federal Two Circuit Jack .....  | 1.00   |
| 92 Remler VT Socket.....               | 1.50   |
| A2 Acme A. F. Amplifying Trans. ....   | 5.00   |
| 550 Murdock VT Socket....              | 1.00   |
| HM-100 DeForest Hand Microphone .....  | 6.00   |
| R-500 DeForest VT Socket..             | 1.25   |

Jewel Radio Meters in all needed scales.  
The new DeForest C.W. Unit Panels.  
All the Radio Corporation New C.W. Apparatus.  
All Amrad Cabinets and Units.  
The New Westinghouse Receiving Cabinets.

Our tremendous stocks, the largest in the middle west, comprise over 2500 separate items. Your requirements will receive our immediate attention.



*The first of our*  
**New Series of Bulletins**

On Radio Apparatus is now ready. Bulletins describing more complete and advanced equipment will soon follow.

In the meantime, send five cents for the first Bulletin No. 10, which will indicate the beginning of the line which we will offer to discriminating amateurs, experimenters, colleges, etc.

**PACENT ELECTRIC COMPANY**

(Selling Agents)

150 Nassau Street,

OR

New York, N. Y.

**WIRELESS IMPROVEMENT COMPANY**

(Manufacturers)

66 York Street,

Jersey City, N. J.

**STUART**  
**"77"**



*Dealers we have an  
attractive proposition  
for you.*

**Business is GOOD on GOOD "B" Batteries—  
Because GOOD "B" Batteries Make GOOD Business.**

Stuart Batteries bring in the signals until the last bit of energy is gone—then you realize that Stuart Batteries give you longer life—more PEP and better service at a reasonable cost.  
No. 5677.

Small price—Popular size—tremendous PEP.

Size 5" x 3" x 2 1/4". Weight 2 1/4 lbs. Price \$2.25.

Send us the name of your dealer, and receive the latest Bulletin on Radio batteries, postpaid.

**STUART PRODUCTS CORPORATION**

663 WEST WASHINGTON BLVD., CHICAGO, ILL.

**C.W.—450 VOLT D.C. GENERATOR—C.W.**

**\$37.50**

Get your C.W. set working, fellows. This generator will supply all the high voltage D.C. you need. It's rated at 450 Volts, 400 milliamperes, or 180 watts at 3500 R.P.M., but will carry 600 milliamperes safely without overheating. The voltage will go up, of course, if you use less than the rated 400 milliamperes. A resistance must be used in the field circuit at all loads.

This generator is equipped with Fafnir ball bearings—a sign of the highest quality and a point not to be overlooked.

**1/2 H.P. 110 VOLT, 60 CYCLE, 3500 R.P.M. MOTOR**

**\$42.50**

This motor is really underrated and can be used for all around work but is especially suited to be coupled directly to the generator described above. It also is equipped with ball bearings.

These machines are made exclusively for us by one of America's best motor manufacturers and are guaranteed to be just as represented. This offer is a bargain. Judge for yourself.

Dealers write for particulars.

**THE BEEKAY MOTOR SERVICE**

4615 LESTER AVENUE,

CLEVELAND, OHIO

# Aint it a grand and glorious feeling'

WHEN TRAFFIC IS DULL AND YOU SIT AND PUZZLE OVER WHAT KIND OF A TUBE YOU'RE GOING



TO USE ON THE NEW CWAND RADIOPHONE SET—




WHY — SUDDENLY YOU HEAR A PHONE STATION CALLING 1, 2, 3, 4, ETC., AND THE O.M. COMES IN VERY "Q SA"



AND YOU GRAB THE KEY AND ASK HIM WHERE HE IS—



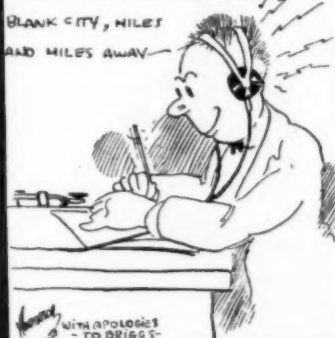AND HE TELLS YOU IN A VERY LOUD VOICE THAT HE IS IN BLANK CITY, MILES AND MILES AWAY—



THEN YOU ASK HIM WHAT KIND OF A SET HE HAS AND WHAT KIND OF A TUBE



AND HE TELLS YOU HE HAS A **RADIOTRON** — THAT SETTLES IT, DOESN'T IT?



WITH APOLOGIES  
— TO BRIGGS

## A power tube for every need



A Popular Size  
Radiotron U. V. 202  
Rated at 5 watts  
Price \$8.00

**Radiotron U. V. 202**  
5 WATTS—Price \$8.00  
Filament requires 7.5 volts at 2.35 amperes. Plate requires 350 volts at .045 ampere.

**Radiotron U. V. 203**  
50 WATTS—Price \$30.00  
Filament requires 10 volts at 6.5 amperes. Plate requires 1000 volts at .15 ampere.

**Radiotron U. V. 204**  
250 WATTS—Price \$110.00  
Filament requires 11 volts at 14.75 amperes. Plate requires 2000 volts at .25 ampere.

**Kenotron Rectifier U. V. 216**  
20 WATTS—Price \$7.50  
New model for use with 5-Watt Radiotron.

**Radio Corporation of America**  
WORLD WIDE WIRELESS

Sales Division, Commercial Department Suite 1803  
233 Broadway, New York City

## Did You Get Your Copy of the "Largest Radio Catalogue in the World?"

Kelly & Phillips' new 200 page catalogue lists all the apparatus available for every radio need. Besides hundreds of illustrations, prices, descriptions, etc., it contains codes, tables, press schedules, and 48 pages of useful information. Mailed anywhere postpaid for 25 cents in stamps or coin. It's a big quarter's worth, and anyway, your quarter is credited to your first \$2.50 order. Send your name and 25 cents today for your copy.

A few specials below reprinted from our catalogue. Right in stock, ready to ship!

|                                |        |
|--------------------------------|--------|
| 22½ Volt "B" Battery, small,   | \$1.25 |
| 22½ Volt "B" Battery, large,   | 2.40   |
| 45 Volt "B" Battery, variable, | 4.00   |

### AUDION RECEIVER PARTS:

|                                    |         |
|------------------------------------|---------|
| Bakelite Panel,                    | \$1.50  |
| 200 meter coil,                    | 1.80    |
| Chelsea condenser,                 | 4.75    |
| Binding posts,                     | .50     |
| Acme detector unit,                | 10.00   |
| Brandes Superior Phones, 8.00      |         |
| Complete                           | \$26.55 |
| Radiotron U.V. 200, detector,      | \$5.00  |
| Radiotron U.V. 201, amplifier,     | 6.50    |
| Radiotron U.V. 202, transmitter,   | 8.00    |
| Baldwin Phones, Type "C",          |         |
| Navy standard                      | \$16.50 |
| Radisco new moulded Vario-Coupler, | 7.50    |

## Kelly & Phillips

Radisco Agency

312 Flatbush Ave., Brooklyn. N.Y.



### All Your Friends Want to Hear that Radiophone Music

—but so many phones cannot be placed in the same circuit.

### THE RADIO MAGNAVOX

will solve your problem and allow everyone to listen in. With suitable amplifiers the signals and music can easily be heard by all. Remember that full field current need not be used except for the very weakest signals, or when extreme volume is necessary.

Price \$ **45**

AT YOUR DEALER'S

Or

## The Magnavox Co.

2725 E. 14th St., Oakland, California  
214 Pennsylvania Terminal Bldg.,  
370 7th Avenue, New York City.



# RADIO APPARATUS

Distributors of Reliable Radio Apparatus to Schools, Colleges,  
Radio Clubs and Experimenters All Over the World!

"PITTSICO"

The Sign of Service!  
All We Ask is a Chance  
to Prove It!



"PITTSICO"

Service Reaches All  
Over the World! Why  
Not Let It Reach You?

## RECEIVING APPARATUS AMPLIFYING TRANSFORMERS

|  |        |
|--|--------|
| No. UV-712 Radio Corporation, new type<br>...just out, very efficient..... | \$7.00 |
| No. 231-A General Radio, new type.....                                     | 5.00   |
| No. 226-W Federal, mounted.....  | 7.00   |

## AMPLIFIERS

|  |       |
|--|-------|
| No. RORK Grebe two step with automatic<br>filament control.....          | 55.00 |
| No. RORD Grebe Det. and two step with<br>automatic filament control..... | 75.00 |
| No. Y-2 Acme in cabinet.....   | 13.00 |

## AUDION CONTROL PANELS

|   |       |
|---|-------|
| No. RORH Grebe in cabinet, with tickler<br>connections..... | 17.00 |
| No. Y-1 Acme in cabinet.....                                | 10.00 |
| No. P-1 Paragon, moulded type, small<br>and compact.....    | 6.00  |

## "B" BATTERIES

|  |      |
|--|------|
| No. 7623 Standard, 22.5 V. small....                 | 1.50 |
| No. 7625 Standard, 22.5 V. large.....                | 2.65 |
| No. 7650 Standard, 22.5 V. variable....              | 3.50 |
| No. 763 Everready, 22.5 V. small.....                | 2.25 |
| No. 766 Everready, 22.5 V. large.....                | 3.50 |
| No. 766 Everready, new type 22.5 V.<br>variable..... | 3.00 |

## CONDENSERS (Fixed mica type)

|  |      |
|--|------|
| No. ROCC Grebe .0002 MF.....                     | 1.00 |
| No. ROCD Grebe .0005 MF.....                     | 1.20 |
| No. ROCE Grebe .001 MF.....                      | 1.60 |
| No. ROCF Grebe .005 MF.....                      | 3.80 |
| No. ROCA Grebe .0002 MF and .5 meg.<br>leak..... | 1.20 |
| No. ROCB Grebe .002 MF and 3 meg.<br>leak.....   | 1.20 |

## DIALS

|   |      |
|---|------|
| No. 41 Chelsea bakelite dial, 1/4" or 3/8"<br>shaft.....                    | 1.00 |
| No. F-800-H Clapp Eastham, new type,<br>just out, bakelite finish 3/8"..... | .75  |
| No. T-1 Tuska, 4" dia. Bakelite, new<br>type, just out.....                 | 1.50 |

## DETECTORS, (Crystal)

|                                    |      |
|------------------------------------|------|
| No. D-101 DeForest, dustproof..... | 2.60 |
| No. RPDA Grebe, dustproof.....     | 2.75 |
| No. 8854 Jove.....                 | 1.80 |

## GRID LEAKS

|   |      |
|---|------|
| No. MW-1 Radio Corporation 1/2, 1, 1.5, 2<br>3 and 5 megohms, complete each.... | 1.25 |
| Grid leaks only.....  | .75  |
| Bases only.....   | .50  |

## REGENERATIVE RECEIVERS

|  |        |
|--|--------|
| No. CR-3 Grebe "Relay Special" 175-850<br>meters.....  | 65.00  |
| No. CR-3A Grebe 175-875 meters with<br>tube control, complete set.....                                       | 45.50  |
| No. CR-5 Grebe "Super-special" 150-3000<br>meters, complete set, ideal for jewelers<br>for time signals..... | 80.00  |
| No. CR-6 Grebe 175-680 meters, Det. and<br>two step amp. self contained complete<br>set.....                 | 200.00 |
| No. CR-7 Grebe 500-20,000 meters "Long<br>Wave Special" complete set.....                                    | 210.00 |

"Let 'PITTSICO' products, super-service and delivery solve your Radio problems!"

**SEND US YOUR ORDERS TODAY!**

Send ten cents in stamps for Catalog No. 22. Over 100 pages, over 150 illustrations, over 600 items  
"PITTSICO" SERVICE REACHES ALL OVER THE WORLD! WHY NOT LET IT REACH YOU!

**F. D. PITTS CO., INC.**

12 PARK SQUARE

DEPT. A.

BOSTON, MASS., U. S. A.

(New England distributors of Grebe apparatus.  
Always in stock.)

## ANTENNA WIRE

|   |      |
|---|------|
| "Pittsco" No. 14 Hard drawn copper, per<br>lb. (80 ft. per lb.).....              | .50  |
| 1000 ft.....  | 5.00 |
| "Pittsco" 7 strand No. 22 tinned copper,<br>stranded (65 ft. per lb.) per ft..... | .01  |
| 1000 ft.....  | 8.50 |
| "Pittsco" 7 strand No. 20 phos. bronze,<br>per ft.....                            | .02  |
| 500 ft.....   | 8.50 |

## RADIOPHONE AND C.W. APPARATUS C.W. POWER TRANSFORMERS

|   |         |
|---|---------|
| Acme 50 Watt 350 Volts, mounted.....        | \$15.00 |
| Acme 50 Watt 350 Volts, unmounted.....      | 12.00   |
| Acme 200 Watt 350-550 Volts, mounted.....   | 20.00   |
| Acme 200 Watt 350-550 Volts, unmounted..... | 15.00   |
| Acme 500 W 1000-1500 V. mounted.....        | 25.00   |
| Acme 500 W 1000-1500 V. unmounted.....      | 20.00   |

## CHOKE COILS

|   |      |
|---|------|
| Acme single coil 150 M. A. capacity.... | 4.00 |
| Acme single coil 500 M. A. capacity.... | 6.00 |
| Acme double coil 150 M. A. capacity.... | 6.00 |
| Acme double coil 500 M. A. capacity.... | 8.00 |

## CONDENSERS (Variable)

|   |      |
|---|------|
| No. 3 Chelsea .0011 Mfd. unmounted....                | 4.75 |
| No. 4 Chelsea .0006 Mfd. unmounted....                | 4.25 |
| No. 182-G General Radio .001 Mfd. un-<br>mounted..... | 9.75 |
| No. 366-Int. Murdock .001 Mfd. unmtd....              | 4.25 |

## FILAMENT HEATING TRANSFORMERS

|  |       |
|--|-------|
| Acme 75 Watt, latest type, mounted.....    | 12.00 |
| Acme 75 Watt, latest type, unmounted.....  | 9.00  |
| Acme 150 Watt, latest type, mounted....    | 16.00 |
| Acme 150 Watt, latest type, unmounted..... | 13.00 |

## FILTERS

|                         |       |
|-------------------------|-------|
| No. 170 Tuska type..... | 16.00 |
|-------------------------|-------|

## INDUCTANCES, C.W.

|  |       |
|--|-------|
| No. 181 Tuska Cap. feed-back circuit.... | 7.50  |
| No. 182 Tuska, split filament.....       | 10.00 |
| No. 183 Tuska Grid tickler.....          | 12.50 |

## METERS

|  |      |
|--|------|
| No. 127 General Radio, Hot wire, flush,<br>.5, 1, 2.5, 5, and 10 Amps.....       | 7.75 |
| Model 301 Weston, D. C. meters, flush,<br>0-100, 300, 500 and 800 milli-amps.... | 8.50 |
| 0-1, 2, 3, 5 and 10 Amperes.....   | 8.50 |

## MICROPHONE TRANSMITTERS

|   |      |
|---|------|
| No. 323-W Western Electric.....               | 3.95 |
| No. 323-W Western Electric, with bracket..... | 4.50 |
| No. 5176-A Connecticut, with Adj. arm....     | 4.00 |
| No. HM-100 DeForest, hand type.....           | 6.00 |

## MODULATION TRANSFORMER

|                                      |      |
|--------------------------------------|------|
| Acme A-3 semi-mounted.....           | 5.00 |
| Acme A-3 fully mounted.....          | 7.00 |
| No. 231 General Radio, new type..... | 5.00 |

## MOTOR GENERATORS

|   |        |
|---|--------|
| International 100 W. 500 V. A.C. Drive..... | 99.00  |
| International 100 W. 500 V. D.C. Drive..... | 110.00 |

## RESISTANCES

|                                       |      |
|---------------------------------------|------|
| Type HS Ward Leonard 5,000 ohms.....  | 2.25 |
| Type HS Ward Leonard 10,000 ohms..... | 3.50 |



## The "Miraco" Vacuum Tube Detector

The new "MIRACO" Detector contains features not found in others at double the price. There is ample space in the hinged covered cabinet for "B" batteries and additional binding posts on the back of panel enable the operator to connect them inside.

**\$7.85**  
Postpaid.

Complete ready to use, only


## The "Miraco" Two Stage Amplifier

The "MIRACO" Two Stage Amplifier is distinguished for its unusual amplification and quietness in operation. May be operated from same "A" and "B" battery used for your detector. But cabinet includes a shelf for additional "B" batteries for the amplifier. A switch automatically changes the circuit from one to two stages of amplification.

Complete ready to use, only **\$29.50**

These "MIRACO" units are ideal for radio-telephone and telegraph work during the static season.

Postpaid.

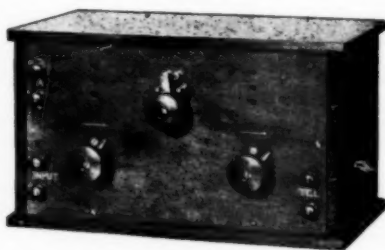


**THE MIDWEST RADIO CO., Dept. E., 3423 Dury Ave., Cincinnati, O.**

### SIMPLEX VARIOCOUPLER



Price as illustrated ..... **\$6.00**  
Simplex Variometer ..... **\$6.00**

This instrument is designed along the same lines as the Simplex Variometer. The Primary Tube is of black polished formica, 4 inches in diameter, the secondary ball and base is of thoroughly seasoned natural finished wood. The windings are of the same size wire as furnished on the Variometer No. 19 cotton covered, and the Primary is tapped in two groups, one of single turns and the other of seven turns each, making it possible to secure any combination up to 49 turns.

These taps are all tinned ready for soldering to leads. Bearings are similar in construction to those furnished on the Variometer having the same contact springs. Furnished with  Shaft long enough for panel mounting.

The Simplex Variocoupler when used with two Simplex Variometers, makes a combination above the average Regenerative Set.

**The Quaker Light Supply Co.**  
728 ARCH St. Philadelphia, Pa.  
Attention: H. J. Dunbar.

### YOU CAN NOW BUY THIS REMARKABLE BOOK

#### THE Alexanderson System FOR Radio Telegraph and Radio Telephone Transmission

By Elmer E. Bucher

10 3/4 x 8 1/4, 56 pages, 38 illustrations and diagrams. Bound in heavy antique paper cover.

Originally Intended for Private Distribution—the requests for copies became so insistent that consent was finally given for a public sale. The only complete description of this famous system as installed in the New Brunswick station is in this book.

Here, for the first time, you get the details of the invention that revolutionized trans-Atlantic wireless transmission—the one producing such a wonderfully clear note that foreign governments sent their experts to investigate and who, on the reports of these experts, ordered the alternator for their own stations.

#### SPECIAL INTRODUCTORY OFFER

Price of Book alone, \$1.25, postpaid. With Wireless Age, one year \$3.25.

Regular Price \$3.75

(Postage Outside U. S. 50 Cents Extra)

THIS BOOK

Is Now Ready to Mail

Order from your dealer or direct from us.

ORDER TODAY

The first edition is limited. Orders filled as received.

DEALERS:—Place Your Order at Once

### WIRELESS PRESS

Incorporated

326-28 Broadway, NEW YORK



**EASTERN  
RADIO**

**INSTITUTE**

TEL.  
BACK BAY  
5964

899 BOYLSTON ST.  
BOSTON, MASS.



## SUMMER CLASSES !

This year the EASTERN RADIO INSTITUTE will conduct their SUMMER CLASSES as usual. New students may begin to advantage in the DAY or EVENING school on any Monday. Special effort will be made to give every possible assistance to those desiring to accomplish the work during the Summer months and in this respect our DAY school offers unusual advantages.

For the last few months we have been telling you of the "RESULTS" accomplished by the EASTERN RADIO INSTITUTE. This month we want to tell you of its "ADVANTAGES."

### "RELIABILITY"

Founded in 1913. Ninth Successful Year.

### "FACULTY"

All Experienced Radio Men.  
Each Instructor a Specialist in His Department.

### "EQUIPMENT"

Latest Spark, Arc, and Wireless Telephone Sets.  
Only School in New England with "Federal Arc Transmitter."

### "INSTRUCTION"

The most Systematic, Comprehensive and BEST Radio Course of Any School in the East.  
Only School in New England giving "Arc" Instruction upon Actual Apparatus.

### "POSITIONS"


Successful graduates of the EASTERN RADIO INSTITUTE are found in responsible radio positions all over the World—Radio Inspectors, Superintendents, Shipping Board Radio Supervisors, Engineers, etc.

### "SERVICE"

Remember—Our Organization with over EIGHT years of Continued RESULTS and SUCCESS is behind every student who enrolls. If you want to become a Commercial Radio Operator let us train you. Just join our SUMMER CLASSES!

Our latest illustrated prospectus is free. If you cannot visit the Institute send for one.  
F. D. PITTS, Director.

## THE STAMP OF APPROVAL!

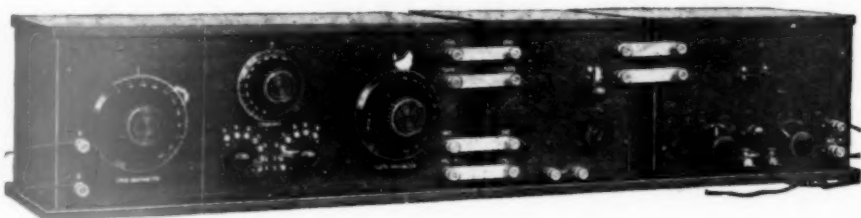

We've won it men! The stamp of approval has been unreservedly placed upon CINO TUNERS in the last 60 Days by the only men who are qualified to do so, when it comes to radio apparatus: The man who has been doing distance and who has established a record!

We know you don't like "patent medicine" testimonials, but would you like to correspond with real DX men and ask them what they think of this Tuner? Just drop us a line and we will furnish you with a list of calls that will convince you!

Then let us have the distinction of being the first radio firm to show you what is meant by PERSONAL SERVICE! The Keystone of our success! The open door between your operating room and our laboratory.

We build C-W apparatus and stock all standard makes of radio accessories.

CINO CT-1 TUNER \$50.00. CD-1 Detector \$18.50. CA-2 Amplifier \$40.00.



**CINO RADIO MFG. COMPANY**  
218 West 12th Street.  
CINCINNATI, OHIO.

Radio 8XY

# Announcement!

Due to the fact that the repair of Vacuum Tubes for radio communication is considered an infringement of the patent rights of the manufacturers, we wish to state that no more Vacuum Tubes will be accepted for repair work by our Laboratories.

**EASTERN VACUUM TUBE LABORATORIES**  
178 WASHINGTON STREET, BOSTON, 9, MASS.

## BI-LATTICE COILS (Duo-Lateral)

For Long Distance Reception This is the Best Type of Inductance

| No. of Turns | Price Unmounted |
|--------------|-----------------|
| 25           | \$0.43          |
| 35           | .44             |
| 50           | .46             |
| 75           | .50             |
| 100          | .53             |
| 150          | .60             |
| 200          | .66             |
| 250          | .73             |

Transportation Prepaid  
In U. S. A.  
Our Products Fully  
Guaranteed

| No. of Turns | Price Unmounted |
|--------------|-----------------|
| 300          | \$0.80          |
| 400          | .93             |
| 500          | 1.06            |
| 600          | 1.20            |
| 750          | 1.40            |
| 1000         | 1.73            |
| 1250         | 2.06            |
| 1500         | 2.40            |

Order direct from ad or send 3c for complete information.

**P. J. STOCKWELL**


**BOX 157-A**

**READING, MASS.**


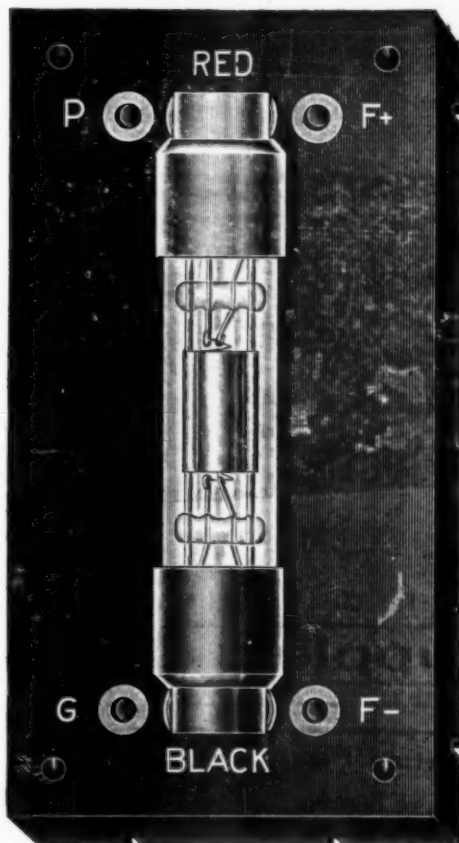
# RAC-3 AUDION

Price  
AUDION  
and  
RECEPTACLE  
\$4.50



AUDIO  
FREQUENCY  
AMPLIFIER  
  
RADIO  
FREQUENCY  
AMPLIFIER  
  
AUDION  
OSCILLATOR

## Full Size FIRST UNIVERSAL AUDION

Manufactured under DeForest Patents No. 841,387 and No. 879,532

## RADIO AUDION COMPANY

90 Oakland Avenue,

Jersey City, New Jersey

No Radio outfit up to date without the RAC-3 Audion.  
No need for buying "soft" or "hard" tubes.

RAC-3 Audions are interchangeable without necessitating critical readjustments.

RAC-3 Audions are not critical to A or B battery adjustments.

Low battery consumption. Filament current 0.8 amp. at 4 volts, maximum. Plate voltage 2 to 22 volts. Clear signals and great sensitiveness on long distance reception.

Perfect oscillation for use in regenerative circuits. Small size. Rigid construction. Non-microphonic. No tube noises due to mechanical vibration.

Maximum insulation between filament plate and grid terminals resulting from new type of tube and receptacle.

No soldered audion terminals.

Maximum direct mechanical contact between audion leads and receptacle clips.

Audion base caps and Receptacle block moulded Grade A Condensite.

Receptacle block is designed to permit built-up panel construction for amplifier panel. Circuit connections may be made from front, back or sides.

If your dealer is not carrying RAC-3 Audions in stock, send attached coupon.

### Mail Order Coupon

Radio Audion Company,  
90 Oakland Avenue, Jersey City, N. J.

Enter my order for.....RAC-3 Audions and.....Receptacles for shipment by return mail. Forward by Parcel Post insured. Enclosed herewith is Postal Money Order for \$.....plus 10 cents for postage and insurance.

Name ..... Address .....

City ..... State .....


ALWAYS MENTION Q S T WHEN WRITING TO ADVERTISERS

# Your one last opportunity

July positively the last month this standard apparatus can be purchased at these tremendous reductions

Control panels with VT Mounting  
as illustrated.....\$11.00  
Same as above, but without VT  
Mounting ..... 9.00

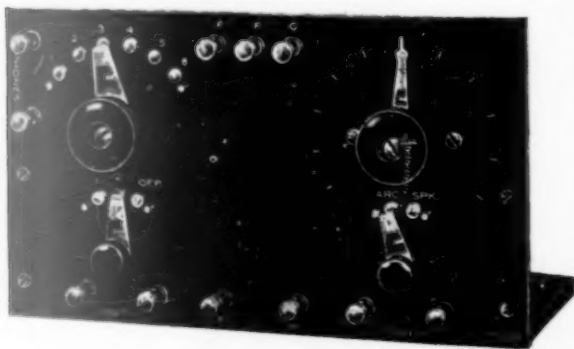CESCO Variometers, each.....\$5.25  
CESCO Variocouplers..... 4.50  
Bakelite Base Crystal Detectors.. 1.25



This Audion Control Panel is the greatest panel value ever offered. It will not discolor like hard rubber, nor is it brittle or easily damaged. The panel is cut from solid sheet—not moulded. Surface highly polished. Lettering and scales machine cut—not stamped—and whitened. Metal parts heavily nicked. Filament rheostat back mounted. Wound for 5 ohms, it permits close adjustment of filament temperature.

That you may be sure not to miss this unparalleled opportunity for saving, mail your orders at once to—

CALIFORNIA ELECTRIC SUPPLY CO. 643 MISSION ST. SAN FRANCISCO, CAL.

## Radio supplies that R right

### The Amateur's Meeting Place

THE ROOM in the back of our store, that has been set aside as a meeting place for amateurs, where they can exchange ideas and experiences is becoming more popular day by day. Visit it soon,—no obligation whatever,—just come in and become better acquainted with fellow amateurs.

#### A FEW SPECIALS.

Variometer, without dial.....\$4.50  
Lightning switches, 100 and  
600 V..... 3.85  
Loose couplers, 400 meters.... 6.00  
No. 14 copper aerial wire, per lb. .50  
Aerial insulators, each..... .28  
Contact points.....3 for .10  
Binding posts, each ..... .05  
At all times, we have a complete stock of brass rods, posts, meters, cabinets, dials, and other accessories at prices that make you happy.

Meet your friends at the Dreyfuss amateurs' test and meeting room.

**DREYFUSS SALES CORP.**

179 Greenwich St. New York City.

### Back To Old Prices



#### Parkin Rheostat

5000 Sold Last Year at \$1.00

NOW REDUCED TO

**75 Cents**

Due to the general drop in the prices of raw material and to our large production, we have been able to reduce all our prices to their pre-war level, and in some cases even lower. New catalog, No. 4, listing our complete line sent free.

Here are a few of the items:

| No.   | Postpaid |
|---|----------|
| 41 Audion panel with rheostat and B Bat. Switch | \$8.00   |
| 43 45 Volt Large B Battery                      | 5.00     |
| 50 Parkin .001mf Variable Condenser, unit only  | 1.50     |
| 51 Parkin .001mf V.C. with knob and pointer     | 2.00     |
| 52 Parkin .001mf V.C. with knob and 3' dial     | 2.50     |
| 53 Parkin Molded Bakelite Fixed Condenser       | .70      |
| UV-200 New Radiotron Vacuum Tube                | 5.00     |

DEALERS—If you are not on our mailing list, write for new catalog and discounts.

**PARKIN MFG. CO.**

San Rafael,

Calif.

## **We Originate Benwood Synchronous Gaps Others Imitate**

The finest rotary quenched synchronous spark gap that has ever been produced.

Cut of this new complete unit not available for this issue but we list herewith several of the outstanding and exclusive BENWOOD features.

**SILENT IN OPERATION—VISIBLE SPARK—NEW TYPE GLASS INSULATORS—REMOVABLE AND RENEWABLE POINT ROTOR (exclusive feature pat. applied for)—3600 RPM. SYNCHRONOUS MOTOR (exclusive feature)—OIL-LESS BEARING (graphite.)**

By driving this gap 3600 RPM. enables the use of a

### **FOUR POINT ROTOR**

thus assuring the MOST EXCEPTIONAL QUENCHING and still gives the very desirable 240 cycle SYNCHRONOUS NOTE that is so eagerly sought after. This gap with a good condenser will give the SHARPEST WAVE that can be obtained with spark equipment. It is so SHARP that it causes comment from all who hear it . . . . .

All BENWOOD GAPS are now equipped with the NEW GLASS INSULATORS which have at last done away with all electrical breakdown in the enclosed type gaps.

**A REAL GAP AT A \$60.00 (bakelite case)**

**PRICE YOU CAN AFFORD \$65.00 (Aluminum case) Write for Circular**

### **BENWOOD SYNCHRONOUS MOTORS**

**can be purchased separately for the next few weeks only**

These motors are of the quick starting induction type and operate on 110 volts 60 cycle current with no transformers or external devices whatsoever. They are ball bearing and remarkably silent while running. They are strictly the finest motor obtainable at any price and are sold at these new low prices.

|                |                          |                           |
|----------------|--------------------------|---------------------------|
| <b>Special</b> | <b>1800 RPM. \$32.50</b> | <b>Immediate Shipment</b> |
|                | <b>3600 RPM. \$37.50</b> |                           |

## **The Benwood Company, Inc.**

**1300 Olive St.,**

**St. Louis, Mo.**

### **MAKE YOUR OWN REGENERATIVE SET From This COMBINATION**



These instruments are wound with extra heavy wire to reduce the resistance, and have special long bearings with a spiral spring inserted to insure a perfect and self cleaning contact at all times. The taps on the Vario-Coupler are arranged in two groups.

#### **PRICES PREPAID**

Variometer as illustrated . . . \$6.00  
Variometer mounted on formica panel & Dial complete 8.50  
Vario-Coupler as illustrated 6.00  
Vario-Coupler mounted on formica panel complete with two switches & Dial . . . \$10.00  
Bulletin #10 sent on request.  
Dealers furnished with trade discounts.



**Simplex Radio Co. 1013-15 Ridge Ave. Phila. Pa.**

25c

25c

## THIS WONDERFUL DETECTOR

Are you interested enough in wireles to spend this small sum for something you cannot do without? Needs no adjusting—just snap it in your hook-up and receive—very convenient. Comes in four styles — GALENA — SILICON — IRON PYRITES and CARBORUNDUM. You

### BOYS!!!



### FOR 25c ONLY

Including Postage

can have five of them for half the cost of any one other detector, and you have the advantage of experimenting with four crystals and using the mineral most suited to your apparatus. FIVE WRIGHT DETECTORS—any selection \$1.00 or 25c each. Act Quickly—write at once before you forget.

THE WRIGHT RADIO CO.

P.O. BOX 534, CITY HALL STATION, NEW YORK, N. Y.

(No Stamps Accepted)

Enclosed is.....for which please send me:

.....Galena Detector

.....Silicon Detector


.....Iron Pyrites Detector

.....Carborundum Detector

Name ..... Address .....

25c

25c

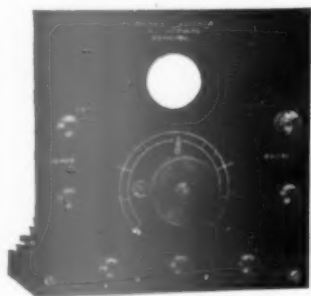

## THE RADIO ELECTRIC COMPANY AUDION CONTROL

Detector Panel .....\$9.50

Amplifier Panel .....\$13.50

Send for circular describing our audion apparatus.

THE RADIO ELECTRIC COMPANY  
3807 Fifth Ave., S. Pittsburgh, Pa.

## Summer Is The Time To Build!

Hot weather is here and it's not as much fun listening in as it is during winter. But don't let good weather find you unprepared to enjoy it—spend the "static" period in overhauling your station and making improvements for the coming of Fall. Get your C.W. set in operating shape, overhaul your aerial, finish that tuner, and build up that experimental tube equipment into a panel, so that when the air gets cold and clear again you will have a station that performs. We have on hand almost everything you could ask for, and what we haven't in stock we can get for you in a hurry. We're here to serve you, and we'll do our best to help you get your station the way you'd like it.

Stop in and see us, or drop us a line.

### SPAFFORD'S

209 TRUMBULL STREET,

HARTFORD, CONN.



---

---

# Hurry Up Fellows!

**WE DON'T WANT TO MISS THAT  
FIRST TRAIN TO THE  
FIRST NATIONAL A.R.R.L.  
CONVENTION & RADIO SHOW  
IN CHICAGO  
AUGUST 30th to SEPT. 3rd. 1921**

---

**I**T sure is going to be some affair and you don't want to miss meeting those fellows that you have heard so much about.

And the Radio Show with all the manufacturers and dealers with their latest apparatus will be on hand. The immense Broadway Armory will be just filled with apparatus and fellows you want to see.

And Oh Boy, that banquet will be one great affair!

Come along, fellows, and spend five of the happiest days of your life with a real live crowd at Chicago during convention week.

---

Banquet reservations should be made immediately with

**N. C. BOS.  
118 No. La Salle St., Chicago**

---


Manufacturers and dealers wishing exhibit space should write to

**N. E. WUNDERLICH**

**4533 No. Sawyer Ave.,**

**Chicago**



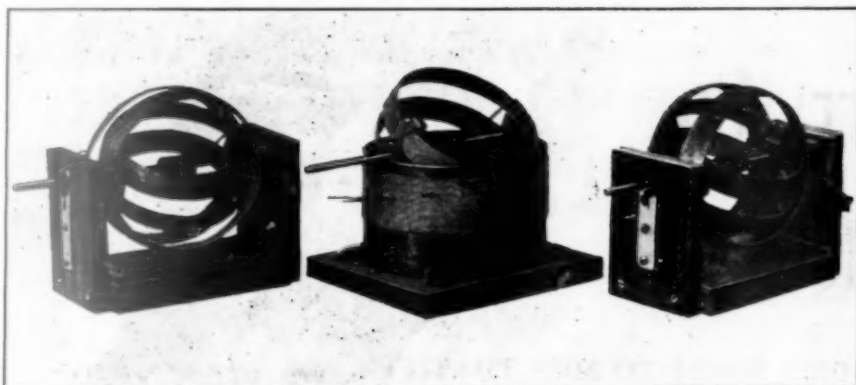

## YOU'VE TRIED THE REST, NOW BUY THE BEST.

The F. & F. variometer set will tune from 175 to 400 meters, and by inserting a variable condenser in the secondary circuit of the coupler, will tune as high as 650 meters. Complete set weighs only 21 ounces, just the thing for a portable receiver. We make the coils through a special process and are guaranteed not to split or crack from heat, cold or dampness. The set is strong and rigid in every respect. The old type wood forms are completely eliminated thereby reducing the distributed capacity to a very minimum. NO sliding connections, all contacts being soldered. Fitted with  $\frac{1}{4}$  in. shafts to take any standard  $\frac{1}{4}$  in. dials and knobs. These sets have stood the most rigid tests and have pulled through where other high priced sets have failed.

**LOOK AT THIS \$12.50 COMPLETE SET, POSTPAID**

If your dealer does not have them write us giving the name and address of your dealer.

We can deliver your order immediately.

**DEALERS—WE HAVE COMMUNICATIONS STATING THAT OUR PROPOSITION IS THE BEST THEY HAVE EVER RECEIVED. IT'S UP TO YOU.**

7803 SENATOR AVE.,

**F. & F. RADIO SHOP**

DETROIT, MICH.

## KEYSTONE WIRE

*Wire for every Wireless Purpose*

### MAGNET WIRE

We are prepared to furnish best grade magnet wire on  $\frac{1}{4}$  and  $\frac{1}{2}$  lb. spools at the following prices

#### PRICE PER $\frac{1}{4}$ LB. SPOOL

| Size<br>B & S Ga. | Single<br>Cotton | Double<br>Cotton | Single<br>Silk | Enameled |
|-------------------|------------------|------------------|----------------|----------|
| No. 22            | \$0.56           | \$0.68           | \$0.62         | \$0.45   |
| No. 24            | .60              | .77              | .67            | .47      |
| No. 26            | .65              | .88              | .71            | .49      |
| No. 28            | .75              | 1.10             | .85            | .52      |
| No. 30            | .85              | 1.24             | .97            | .53      |
| No. 32            |                  |                  | 1.15           | .55      |
| No. 34            |                  |                  | 1.52           | .59      |
| No. 36            |                  |                  | 1.77           | .69      |

Price of  $\frac{1}{2}$  lb. spools double above list.

All prices are net and include cost of spool and delivery charges via Parcel Post to any Post Office address in the United States; safe delivery guaranteed.

Send for Circular 21-A giving prices on other sizes, insulations and quantities of Magnet Wire. This circular lists "WIRE FOR EVERY WIRELESS PURPOSE."

**KEYSTONE WIRE COMPANY**

P.O. BOX 120



SCRANTON, PA.

# ACE

## Three New Ace Products

Type AVA Tuner . . . . . \$45.00

Type AVB Tuner . . . . . \$32.00

Type ATC Detector . . . . . \$12.00

Send 3c in stamps for SPECIAL

PRICE BULLETIN No. 102.


**The Precision Equipment Co., Inc.**

Mfrs. and Distributors of Radio Equipment

Dept. D., 2437-39 Gilbert Ave., Cincinnati, Ohio

"You May Pay More But You Can't Buy Better"

Member A.R.R.L. Radio Call "8XB"

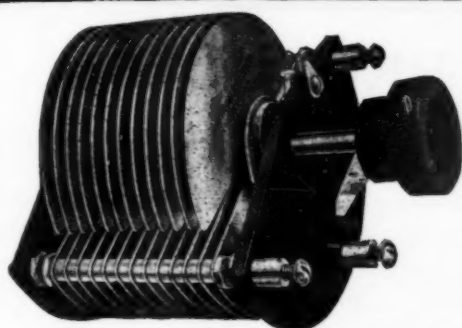

**WANTED--** The Name of Every Radio Man Who Has Had Trouble With His C.W. Condenser.

*This One Won't Give Trouble.*

**IF YOU ARE NOT ACQUAINTED WITH "WIRELESS SHOP" CONDENSERS—LET'S SHAKE.**

We want every amateur who uses a variable condenser to know our product. Our new bulletin showing our entire line of variables will be mailed for the asking. Where shall we send your copy?

We build 14 different sizes of condensers, in three different types, and several special ones to order. The prices range from \$2.00 to \$10.00 for the standard instruments. Can any other manufacturer offer you anything like this in variables?

The NEW WIRELESS SHOP C.W. VARIABLE CONDENSER is designed to be used on CW sets where the plate voltage runs up to from 200 to 1000 or higher. You won't have makeshifts now. Get a condenser which is built especially for your C.W. set. The plates are widely spaced and the construction is rigid. Only the best of materials and workmanship throughout. Fully guaranteed to give satisfaction or your money back.

**PRICES:**

No. 1500 15 plate, approximately 0.0004 mfd. Max. capacity.. \$6.00

No. 2500 25 plate, approximately 0.0006 mfd. max. capacity.. 7.50

No. 3500 35 plate, approximately 0.0008 mfd. max. capacity.. 9.00

Regularly equipped with knob and pointer and mounting screws. A metal dial will be supplied instead of the pointer at 75c extra, or a high grade moulded bakelite knob and dial with graduations filled in white, will be furnished at \$1.00 extra.

Postal charges and insurance must accompany your remittance. Insurance on any CW condenser is only 5c. Isn't it worth it?



511 West Washington St.,

Los Angeles, Cal.

**LONG LIFE—CLEAR RECEIVING**

are the features of

**BURGESS "B" BATTERIES**



All sizes from the Navy type down to the Baby "B." With and without taps

Send for catalogue

**BURGESS BATTERY COMPANY**

Harris Trust Bldg.

::

::

CHICAGO

## SAG-RE-CO- PRODUCTS



Back Mounted Rotary Switch. Used for master switch employing bakelite insulation.

Price \$4.00

Improved Spark Gap—entirely machined product. Provision made for interchangeable and renewable teeth. 9" O.D.—teeth 1/16" x 1" special aluminum alloy. XX grade bakelite insulation. See cut in June QST

Introductory price \$15.00.

Our mail order dept. can make immediate shipment on all standard radio tel. and tel. equipment with prompt service.

We handle the following and many other makes of equipment.


Clapp-Eastham  
Electrose Mfg.  
Chelsea  
Federal  
Remler  
Adams-Morgan  
Murdock

Acme  
Brandes  
John Firth  
General Radio  
DeForest  
Continental Fibre  
Radio Corp. of Am.

## Saginaw Radio & Electric Co.

118 SO. WATER STREET,

SAGINAW, MICHIGAN

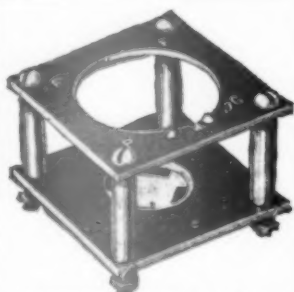

Type 126 Tube Socket  
PRICE 75c POSTPAID


### Something New

Made to please you and

Priced to please your pocketbook BY departing from conventional design in audion sockets we have combined the advantages of all, the disadvantages of none and a price lower than any. Think of it—a sturdy, easily mounted socket that is heat proof, has bakelite-dilecto insulation, handy binding post etc., all for 75c.

HERE'S a smooth running rheostat that takes panel space two inch in diameter, needs one hole to mount, has six ohm resistance, all off and all on positions and a brass panel bushing. Priced at 90c.

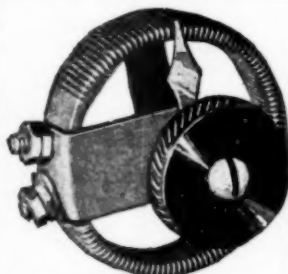THE WILCOX LABORATORIES  
LANSING, DEPT. H., MICHIGAN



Type 122 Rheostat  
PRICE 90c POSTPAID

## NEW ORLEANS RADIO

APPARATUS AND SUPPLIES

### ROSE RADIO SUPPLY

604 GRAVIER STREET

NEW ORLEANS, LA.

Send 10c for Latest Catalogue

### C. W. Transmission will be stronger this summer than ever before.

Send 10c in stamps or coin for our new catalogue together with set of Radio Corporation circulars dwelling on Radiotrons and their use. 10c to be returned as credit on first order of \$1.00 or more.

### THE ELECTRIC SHOP

306 George St. New Brunswick, N. J.



## More sensitive than the ear of an owl

Ernest Thomson Seton, the naturalist, says Owls have the most sensitive ears known.

Brandes Wireless Receivers are more sensitive—an improvement on Nature. The two telephones are perfectly matched in tone and this exclusive Brandes feature adds force to the supersensitive mechanical tympanums.

The minutest sound vibrations quivering through the air from out the far distances are caught and focussed into the clean, clear notes of the readable message—Brandes Headsets getting them all.



"Navy" type Headset. Price . . . \$14.00  
"Superior" type Headset. Price 8.00

Sold on 10 days trial. Money refunded if not satisfactory.

Send 5c for Catalog F  
DEALERS—Write for  
Special Proposition.

**C. BRANDES, Inc.**

Wireless Headset Specialists

Room 821, 32 Union Sq.

New York City

# BRANDES Matched-Tone HEADSETS

## Get a Copy of Our Wireless Manual H-12



It contains 200 pages, fully illustrating and describing the many instruments used in Radio service. Forty-five pages are devoted to general instructions, diagrams, station calls, tables, codes and other information identified with the art. The book is printed on highly finished paper with a two-color cover; size 9x5 1/4 inches.

We ask 25 cents for it, give a coupon receipt for the amount which coupon when returned with an order will be credited at 25 cents.


With a large and varied supply of wireless instruments and accessories carried in stock, we are in position to fill any order or meet any condition promptly and accurately.

We have experts in charge of our wireless departments, so do not hesitate to consult us about your wireless problems. Proper attention and accurate information is yours for the asking.

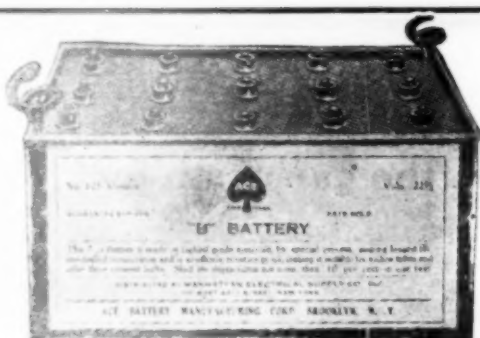**MANHATTAN ELECTRICAL SUPPLY CO., Inc.**

17 Park Place, New York; 114 So. Wells St., Chicago; 1106 Pine St., St. Louis; 604 Mission St., Frisco

ALWAYS MENTION Q S T WHEN WRITING TO ADVERTISERS



## Variable Plain ACE "B" BATTERIES

— Use the Best —

## Ace "B" Batteries

Dealers

Sell the "BEST" with our Special Inducements.

Write for Catalog No. 15

| Cat. No. |          | Size      | Voltage. | Hrs. Ser. | Taps | Lbs. | Price  |
|----------|----------|-----------|----------|-----------|------|------|--------|
| 623      | Plain    | 2½ x 2x3½ | 22½      | 400       | 1    | 1    | \$1.50 |
| 623      | Variable | 2½ x 2x3½ | 22½      | 400—5     | 1    | 1    | 1.75   |
| 625      | Plain    | 3 x 4x6½  | 22½      | 1400      | 5    | 5    | 2.50   |
| 625      | Variable | 3 x 4x6½  | 22½      | 1400—5    | 5    | 5    | 3.00   |
| 626      | Plain    | 3 x 8x6½  | 45       | 3000      | 10   | 10   | 5.00   |
| 626      | Variable | 3 x 8x6½  | 45       | 3000—6    | 10   | 10   | 6.00   |

ACE "B" BATTERIES are made according to government specifications, and are especially adapted for Plate Circuit, Detector and Amplifying Tubes.

*Guaranteed not to Depreciate more than 10% in one year when not in use. Absolutely Moisture proof.*

A few of the dealers handling Ace "B" Batteries

Am. Electro Tec. Appliance Co., New York.  
Continental Radio & Electric Co., New York.  
Dreyfuss Corporation, New York.  
W. B. Duck, Toledo, Ohio.  
Wilcox Laboratories Inc.—Lansing, Mich.

Dave Killoch, New York.  
Manhattan Elec. Supply Co., New York.  
M. Muller, Boston, Mass.  
Vimy Supply Co., Toronto, Canada.  
Whithall Elec. Co., Springfield, Mass.

### ACE BATTERY MFG. CORP.

44 COURT STREET

BROOKLYN, NEW YORK

Phone Main 8373  
Phone Main 7328

AGENTS WANTED

## 10c. Charges Your Battery AT HOME F-F Battery Booster

WITH AN

and your station will

never be closed because of

a discharged battery.

Is it not gratifying to feel

that your filament battery

will always be ready when

you want it and that you

will never have to give up

in disgust when working

a distant station?

F-F Battery Boosters are

automatic and operate un-

attended. Screw plug in

lamp socket, snap clips on

battery terminals and see

the gravity come up.

The ammeter shows you

Service Station Service just the amount of cur-

rent flowing. The full wave of current is recti-

fied thru adjustable and easily renewable carbon

electrodes which maintain a constant efficiency

and last for thousands of hours. Everything

complete on one compact, self-contained unit.

The F-F Booster is a Magnetic Rectifier for

105-125 Volt 60 Cycle Alternating Current.

Bantam Type 6 charges 6 Volt Battery at 6 Amps. \$15

Type 16 charges 6 Volt Battery at 6 Amperes \$24

Type 166 charges 6 Volt Battery at 12 Amperes \$32

Also Boosters for 12 Volt Batteries at same prices

Shipping weights 10, 12 and 15 lbs.

Order from your dealer or send check for prompt

Express Shipment. If via Parcel Post have remittance

include Postage and Insurance Charges.

Will also Ship C. O. D. Also F-F Battery Boost-

ers for charging batteries from Farm Lighting

Plants, Direct Current Circuits and D.C. Generators.

For Group Charging use the Full Wave Automatic

F-F Rotary Rectifiers of 100 Volt, 36 cell capacity.

Order now or write today for descriptive Bulletin No. 31 or Rotary 31A

The France Mfg. Co. CLEVELAND, OHIO

Canadian Representative: Battery Service & Sales Co. Hamilton, Ontario



## Did You Hear About the 18 Men from 18 Boylston Street ?

Up to April 28, 1921, the last 18 graduates from 18 Boylston Street averaged 81.5% out of a possible 90% on their GOVERNMENT EXAMINATIONS.

The unusually high average obtained by these 18 graduates, whose instruction averaged the short period of 5 months previous to their examination, shows conclusively the high merits of this school. Results count.

Send for free literature

### MASSACHUSETTS RADIO AND TELEGRAPH SCHOOL, INC.,


18 Boylston Street, Boston, Mass.

Tel Beach 7168

R. F. Trop

G. R. Entwistle
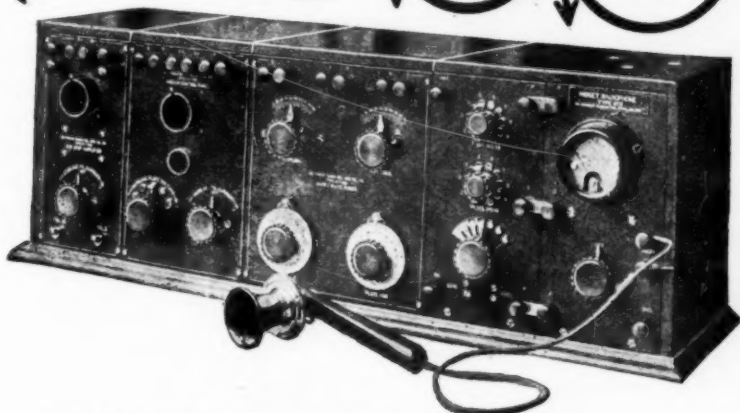
## If It's A Radiophone It's A DeForest Invention A New Idea In Radio—A C.W. Design



- Complete set of four units mounted vertically.
- (1) Complete radio "midget" transmitter. Phone sending range 30 miles (OT-3).
  - (2) Complete short wave tuner, 150 to 600 metres (MT-100).
  - (3) Complete audio amplifier (MP-200) for stand: rd gaseous tubes. (MT-100)
  - (4) Complete one-step amplifier (MP-200).
  - (5) Any additional step of amplification may be added.

### RADIOPHONE "INTERPANEL" SYSTEM

*For Commercial and Amateur Telephone and Telegraph Service*

The "Interpanel" System marks an advance in radio apparatus design equal in importance to C.W. for transmission.

The "Interpanel" System has all the convenience and expandability of sectional book cases.

Each panel is only 9 inches high. Each panel mounts a complete apparatus. Each panel gives a minimum amount of space to

the apparatus. Each panel gives all the space the apparatus requires. The panels lend themselves to stacking in any position and in any direction.

Two panels make a complete listening station.


The panels may be added one by one to increase the range of your station.

Get the "Interpanel Idea." Send for catalogue 79.

**De Forest Radio Tel. & Tel. Co., 1415 Sedgwick Ave., New York City.**

*Inventors, Licensers and Manufacturers of High Grade Radio Apparatus.*

### AT LAST—A REAL DISC!

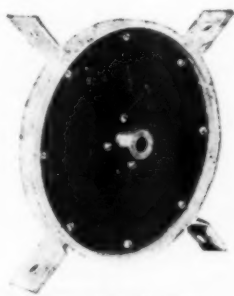

This rotor is designed to be scientifically correct and not merely to sell. It is better than any other gap on the market because of its large diameter, and consequent greater peripheral speed, combined with the spark-thru principle.

The better quenching and shorter leads resulting therefrom will go a long way toward putting your station among the leaders of the game.

#### SPECIFICATIONS:

Aluminum ring 12" in diameter 4 or 8 tooth.  $\frac{3}{16}$ " Bakelite center. Electrodes  $1\frac{1}{2}$ " wide. Price \$12.00. State size of shaft when ordering.

MADE BY

**The Twin City Radio Lab.**

Pat. applied for  
**SPARK-THRU TYPE**

**785 ALDINE STREET,**

**ST. PAUL, MINN.**

# OSCILLATION TRANSFORMER



Type TH-2

Built to put ALL of your condenser energy into the open circuit. No metal parts near the windings to absorb the energy. Formica insulation throughout. Woodwork natural finished walnut. Heavy brass ribbon. Secondary is 18" diameter and has 8 turns of 1 1/4" ribbon. Primary is 18" diameter and has 3 turns. TH-1 has 1 1/4" ribbon on primary. TH-2 has 3". Can be mounted in either vertical or horizontal position. Coupling easily variable.

TH-1 - - \$14.50

TH-2 - - \$18.50

Write for literature.

Interesting proposition to dealers.

*We have in stock at all times a complete line of spark and CW equipment.*

**T & H RADIO CO.**

**ANTHONY,  
KANSAS**

**RTS**

**★ AMATEURS ★**

**RTS**

**MANUFACTURERS—DEALERS & JOBBERS**

We are the originators of the RTS Condensers. We do not hesitate to say that our Condensers will surpass all other makes, regardless of price.

**SIMPLICITY IS THE SECRET OF THEIR SUCCESS COMBINED WITH THE BEST GRADE MATERIALS OBTAINABLE.**

IF YOU HAVE NOT PURCHASED YOUR CONDENSERS

**DO IT AT ONCE**

|   |      |        |
|---|------|--------|
| RTS—GRID CONDENSER .0005 M.F.               | Each | \$0.35 |
| RTS—GRID CONDENSER AND GRID LEAK .0005 M.F. | Each | .50    |
| RTS—FIXED PHONE CONDENSER .0013 M.F.        | Each | .40    |
| —NOW READY—                                 |      |        |
| RTS—CONDENSER FOR RADIOTRON TUBES           | Each | .40    |

SEND FOR CATALOGUE

**RADIO TESTING STATION,**

**BINGHAMTON 25, N. Y.**

## A SPECIAL MESSAGE

to  
**RADIO DEALERS AND MANUFACTURERS**

Have you seen "THE LEADER"—the post that has solved the Binding Post question.

Write us today for pamphlets and samples, also our attractive discounts and special sales proposition.

You cannot afford to be without these unique posts for your **FALL TRADE.**

**ORDER NOW—IMMEDIATE DELIVERIES**

**MADE RIGHT**

**STAY TIGHT**

**SELL ON SIGHT**

**THE H. H. EBY MANUFACTURING CO.**

**1302 Wallace St.,**

**Phila., Pa.**



"CAPTAIN"

(100 amp).


Made in five sizes.



"COMMANDER"  
1/2" size (Made in two sizes.)



# W H Y ?

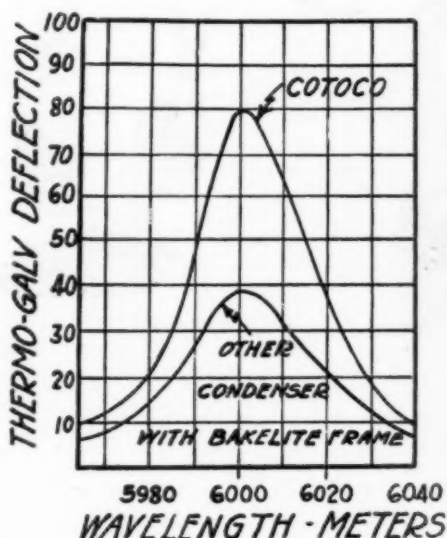

## W H Y

did we start building condensers?

should you investigate Cotoco condensers?

should you use a Cotoco condenser?

The curves above were made to compare the sharpness of resonance of our condenser with the usual type assembled between bakelite heads. It gives the essential reason WHY this condenser will produce results you want. If this is not sufficient reason, let us send you our descriptive bulletin, which will give you all the details.

Made in three sizes .0005 M.F.—.0007 M.F. and .001 M.F. in case as shown, or unmounted.

Get on our mailing list NOW

### COTO-COIL CO.

87 WILLARD AVE.,

PROVIDENCE, R. I.

## IT WILL COST LESS TO BUY THE BEST



6 Volt 60 Amp. Hour. Especially adapted for Radio work, and makes an ideal "A" Battery. Price \$18. Send shipping directions.

R. W. BLISS CO.

42 Davis St.

Wollaston, Mass.


## YOU CAN NOW BUY "CONNECTICUT" RADIO EQUIPMENT DIRECT FROM MANUFACTURER



### CONNECTICUT
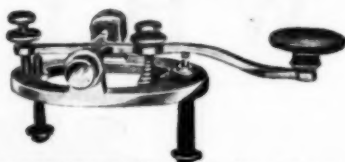
#### Variable Condenser

Compact. Simple. 360 degree adjustment. Unusual signal strength. Portable or Panel type .....\$6.50



#### CONNECTICUT Sending Keys

For low power stations  
10-W: as illustrated.....\$3.00  
11-W: without mounting screws 2.75



#### CONNECTICUT Toggle Switch

For receiving panel

75-Y: one gang.....35c.  
55-Y: two gang.....70c.



### CONNECTICUT

#### Head Receivers

U. S. Govt. Standard. Lightest, Strongest. Most easily adjusted.  
1856-A with 2000 ohm receivers and 6-ft. cord.....\$6.00  
1857-A: with 3000 ohm receivers and 6-ft. cord..... 6.50  
5014-W: head band only.... 2.00

Prices F. O. B. Meriden. Send for literature descriptive of our complete line of Radio Apparatus and Supplies. Amateur inquiries especially invited.

## CONNECTICUT TELEPHONE & ELECTRIC COMPANY

Meriden Connecticut

### G.E. Kenotron

|                        |        |
|------------------------|--------|
| UV—216 20 W. Rectifier | \$7.50 |
| UV—200 Radiotron       | 5.00   |
| UV—201 " Amplifier     | 6.50   |
| UV—202 5W. Oscillator  | 8.00   |
| UV—203 50W. "          | 30.00  |
| 550—VT Sockets         | 1.00   |
| Paragon rheostats      | 1.75   |

Prepaid in U. S.

### Wireless Supply Co.

Springfield, Ohio, Box 59

### ATTENTION you SUNKIST moonhugged RADIATORS

(Especially moonhugged)

If it is inconvenient for you to come to my store for your radio apparatus, I will pay transportation charges from the factory on anything you want. If I have it in stock, you pay only the transportation from here. If not, it comes prepaid direct from the factory. The latter anyhow if you prefer.

#### Altadena Radio Laboratory

PAUL F. JOHNSON, Owner.

ALTADENA,

CALIFORNIA

### Emblems—now \$1




A new supply of A.R.R.L. Emblems has been secured at a figure which permits a reduction in the price. Now every A.R.R.L. member can have one and be recognized as a booster of Citizen Radio. A.R.R.L. Emblems are made of heavy rolled 14 k. gold with black enamel background, and are available in either lapel button or pin mounting—specify which is desired when ordering. Price \$1 postpaid.

A.R.R.L. 1045 MAIN ST., HARTFORD, CT.

ACCURACY

DEPENDABILITY

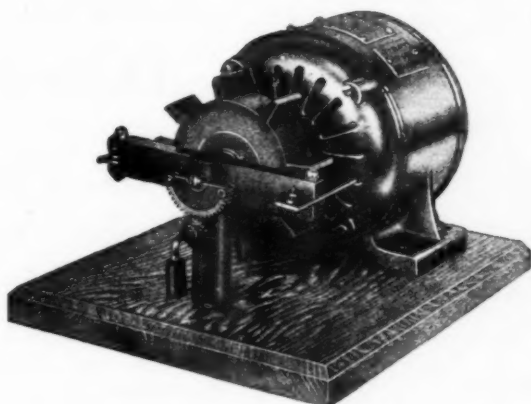

QUALITY

PERFECTION

## J-RAY SYNCHRONOUS ROTARY GAP

We take pleasure in announcing our latest product a real synchronous rotary at a price within the reach of all. You can now prepare your station for the coming fall season by installing the ultimate in Amateur rotary gaps. Synchronous rotaries are already being used by the country's leading stations. The advantages of such a gap are too well known to be discussed.

As per the cut the stationary electrodes are adjusted to the point of synchronism by an excellent gear arrangement, very simple but exceedingly effective. While the gap is in operation the adjustable arm can be rotated with perfect safety to the operator. Once the desired point is found the arm is locked in place precluding any possibility of the slightest movement. Owing to the excellent motor used and our Machine Cut Disc, the gap runs vibrationless in the full sense of the word. The fixed electrodes can therefore be adjusted exceedingly close to the disc.

The motor is a  $\frac{1}{8}$  H.P. 1800 RPM, 60 cycle, 110 (or 220) volt, single phase synchronous motor, very large for its rated H.P., made for us by a nationally known concern. The disc is our 8 or 4 point (Aluminum or Bronze) the former giving the well known characteristic 120 spark synchronous tone, the 4 point a 60 cycle note. Insulation is Bakelite, base is of heavy Oak, fixed electrodes of copper.

The strongest construction and most accurate workmanship possible are found in this gap. Its sturdy and rugged build insures its giving the greatest satisfaction under the longest and most severe usage.

**Synchronous Rotary as described, 4 or 8 point disc, \$75.00.  
Motor only \$45.00. F. O. B. St. Louis, Mo.**

Any of our gaps in conjunction with this motor can be run synchronously by our improved method. Write for details.

**Next Month—The J-RAY Non-Metallic Enclosed Gap—A Big Surprise**

**J-RAY MFG. CO. 2131 De Kalb St. St. Louis, Mo.**

## NEW- THE FINEST DIAL ON THE MARKET



4" dia. 16 gauge Brass silver plated, and lacquered to prevent tarnishing. Clock wise Rotation. Two Calibration scales permit Rapid Adjustment. Polished Bakelite knob, 1 1/4" dia. and 2 1/4" at flange is just the right size. Has hole for 3/4" shaft and screw set.

SOMERVILLE DIAL INDICATOR.....\$2.00  
SOMERVILLE FLANGED KNOB......90

Used for coupling or tickler control and also on Rheostats, where the Non-Melting feature is invaluable. Somerville Switch Lever, to match, \$0.65. 1 1/4" Dia. Bakelite Knob, N.P. Bronze Blade, one piece Brass shaft, Brass Bushing and Lock nuts. Metal Parts Polished Nickel.

Anticapacity Contacts, 4c,  
45c. per Dozen

Threaded shank and 1/8" Nut.  
G-R Switch Stops 5c. each.  
Insulated Binding Posts, Medium, 12c. each. 1 doz. \$1.25.  
Large, 16c. each. 1 doz. \$1.65.  
Empire Cloth Tubing, 10c. ft.



Northeastern Headquarters for Phone and C. W.

Accessories; Pioneers and still in the lead

Discovered: A cheap substitute for Mica Dielectric. Let us quote you on your 2000V. Test C.W. Condenser. 1800 V Grid Condenser .0005 MFD. \$1.00. \$2.25 Ward Leonard 5000 ohm Grid Leak \$1.85

C.W. Inductance S-50  
\$8.50 Postpaid.

31 turns #9 copper wire, 5 ins. dia. on Slotted Bakelite Form. 3 insulated clips furnished. Sorala Threaded Bakelite inductance Form, 6" long 3 3/4" D. \$3.00



New Catalog and Treatise on Practical C. W. and Phone Sets. Edition Limited, order now. 20c. postpaid

PARAGON RA-TEN TUNER, SPECIAL.....\$78.00

GREBE CR-5 RECEIVER..... 80.00  
CR-3 RELAY TUNER..... 65.00  
WESTINGHOUSE COMPLETE RECEIVER..... 125.00  
WESTINGHOUSE TUNER..... 65.00  
DETECTOR AMPLIFIER..... 65.00

**SOMERVILLE RADIO LAB.**

102 Heath Street, Winter Hill, 45, Mass.

As The Sole Philadelphia

## Distributors

for the

## DE FOREST Radio Apparatus

we have in stock for immediate delivery practically every need in

**Complete Radio Telephone Transmitting and Receiving Sets for the Amateur.**

See the New Interpanel Sets  
Receiving 125 to 25000 meters

Free On Request Catalog E.

**CENTRAL ELECTRIC**

AND LOCK COMPANY

1309 Arch St., Philadelphia

1/4 H. P., 110 volts,  
A. C., 60 cycle,  
single phase,  
1750 R. P. M.

**MOTORS**

LARGE QUANTITIES NEW WASHING MACHINE MOTORS

These are of standard manufacture and carry the full factory guarantee. Shipped in original boxes. Complete as cut. Suitable for operating Coffee Grinders, Cream Separators, Bottle Washers, Air Compressors, Small Lathes, Etc.

Mail \$2.00 and a Money order We will send C.O.D. subject to full examination. Money Back Guarantee.

Burgess Small Motors and Compressors Write for Catalogues Special Quantity Prices-Values \$15.00

**\$22.75 Each**

MANUFACTURER'S DISTRIBUTOR

CHAS. H. JOHNSTON - Box 19 W. E., Pittsburgh, Pa.

## MINNESOTA RADIO AMATEURS

AND OUR NEIGHBORS

We have a complete line of radio apparatus and represent over thirty radio manufacturers. Write us for prices.

POSTAGE PAID

Duluth's Oldest Electrical Store


**BURGESS ELECTRIC CO.**

310 W. FIRST ST., DULUTH, MINN.



## Federal Standard Radio Accessories

Are Recommended and Endorsed by the Leading Radio Engineers and Amateur Experimenters of the Country.

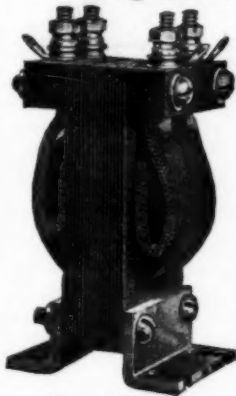


No. 226-W  
Audio-Frequency  
Transformer

Federal No. 226-W Audio Frequency Transformer gives the **Maximum** Amplification with all types of Standard Tubes now on the market.

Federal No. 300-W Filter coil for smoothing out the Pulsations in the D.C. Plate Voltage Supply in Radiophone Circuits.

It is unquestionably the most effective filter coil on the market.

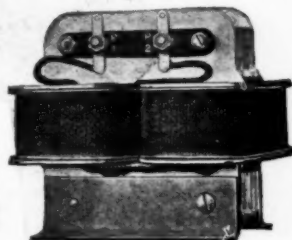

No. 300-W  
800 M. A. Filter Coil

Ask your dealer for Federal products. If he does not have them, tell us his name.

## Federal Telephone and Telegraph Co.

Buffalo, N. Y.

Manufacturers of Standard Radio Accessories. Send for Bulletin 102-W.B. & C. Circular.


## SWITCHES, All High Polished Nickel



S #2—75c.



S #1—50c.

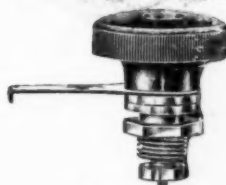

S #3—75c.



SP #1—80c.



B #2—12c.



B #3—15c.




B #1—10c.



CP #1—18c. Doz.



C #1—30c.

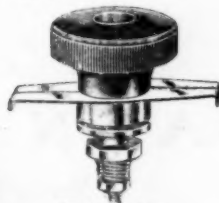

SP #2—80c.

SEND FOR  
DEALERS  
PROPOSITION  
STATE QUANTITY

ALL RADIO PARTS  
IN STOCK  
10% DISCOUNT  
JULY & AUGUST

AMERICAN ELECTRO TECHNICAL APPLIANCE COMPANY

BIGGEST STOCK IN N. Y. CITY. THE WHOLE BLD. FULL OF RADIO PARTS AND APPARATUS

Dept. Q,

235 Fulton Street

New York City



## The Radio Magnavox For \$45

This Magnavox will allow every one to listen in. It will reproduce radiophone speech or music so that it can be heard all over the house when sufficiently amplified. It can be operated with dry cells or a storage battery. It is indispensable for every outfit. Send for Bulletin 30 and get details.

# MAGNAVOX

J. O. Morris Co., Inc.


1270 Broadway

New York

I enclose \$45.00 money order for which you will send the Radio Magnavox by express prepaid.

Name .....

Address .....

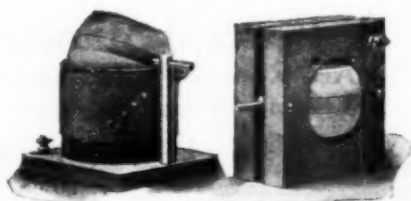

## Variometers Couplers \$3.75

These instruments embody finest workmanship and best materials, all wooden parts genuine mahogany, coupler primary wound on formica tubing. Metal parts of brass. Wound for maximum results on short wave work. Money back if they fail. With Chelsea Dial \$1 Extra. Send for bulletin describing unwired regenerators.

FREDERICK WINKLER, Jr.

304 COLUMBUS AVENUE

New York City, N. Y.

## A Full Line of Radio Apparatus

We have everything you need. Below are a few items from our large stock. Watch this space for a complete stock list.

## POWER TUBES

|                                  |        |
|----------------------------------|--------|
| A-P 5 watt.....                  | \$7.50 |
| Cunningham C302 5 watt.....      | 8.00   |
| Cunningham C303 50 watt.....     | 30.00  |
| Cunningham C304 250 watt.....    | 110.00 |
| DeForest Singer Type 37 watt.... | 24.00  |
| DeForest Oscillion 250 watt..... | 60.00  |
| DeForest Oscillion 500 watt..... | 75.00  |
| DeForest Oscillion 1000 watt.... | 150.00 |

We have all the necessary material for CW outfits.

|                                   |         |
|-----------------------------------|---------|
| 350 volt generators.....          | \$20.00 |
| 6" diam. 3/8" wall Formica Tubing |         |
| Per ft. ....                      | 2.75    |

Send for bargain list.

The above prices are F.O.B. St. Paul.

PIONEER ELECTRIC CO.

137 East Fifth St.,

St. Paul, Minn.

## Canadian Radio Experimenters — Special

|                                  |         |
|----------------------------------|---------|
| Radio Storage Batteries          |         |
| 40 Ampere hours.....             | \$22.00 |
| 60 Ampere hour.....              | 25.00   |
| Baldwin Telephones Type C.....   | 24.75   |
| Brandes Telephones Superior..... | 12.00   |
| Transatlantic Telephones.....    | 18.00   |
| Navy Telephones.....             | 21.00   |
| Murdocks Telephones 2000 ohm.... | 6.00    |
| " " 3000 ohm....                 | 7.20    |

|   |         |
|---|---------|
| Lateral Coils to order                            |         |
| Inductances for Wireless Telephone                |         |
| Milliammeter and Hot Wire Meters                  |         |
| Vario-Couplers & Variometers.....                 | \$4.25  |
| Transmitters for Radio purposes....               | 3.50    |
| LOOK! LOOK!! LOOK!!!                              |         |
| 1/4 H.P. 110 Volt 25 cycle Menominee Motors.....  | \$30.00 |
| 1/5 H.P. 110 volt 25 cycle Menominee Motors.....  | 25.00   |
| 1/10 H.P. 110 volt 25 cycle Menominee Motors..... | 20.00   |

Send 5c for 30 page catalogue

J. M. PAQUIN

The Electrical Shop, 787 Queen St., W. Toronto, Ont.

## A Brand New Storage Battery. More Capacity for Less Money

A battery with twice as many plates per cell as the standard battery. The most powerful and longest life battery ever built. Guaranteed 2 years.

Price, F.O.B. Cleveland:—

|                            |         |
|----------------------------|---------|
| 6 Volt 80 Ampere hour..... | \$28.00 |
| 8 Volt 80 Ampere hour..... | 36.00   |

**Colebrook - Hamilton Battery Co.**  
1940 E 82nd. 1941 E 81st  
CLEVELAND, OHIO.

## Second Introductory Offer of the Bronx Radio Equipment Company

Real two step amplifiers—Size of panel 11½" x 7½". Old English Oak Cabinet. Shipping weight—packed—15 lbs.

|   |         |
|---|---------|
| Price each .....                              | \$50.00 |
| Regular stock size amplifiers 5½" x 8" panel. |         |
| Price each .....                              | \$40.00 |

Containing:

Federal transformer, plugs and jacks. Paragon rheostats. XX Bakelite.

Special 6 Volt—60 Ampere Storage Batteries. Price, each .....

Estimates furnished on receiving, transmitting and phone sets built to your specifications.

Dealers write for proposition.

**Bronx Radio Equipment Company**  
687 Courtlandt Ave. New York City

## Second Transatlantic Tests


Late October or November

Get your sets in shape and watch QST

ALWAYS MENTION QST WHEN WRITING TO ADVERTISERS

## ANNOUNCING
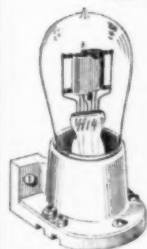
## The Crosley V-T Socket 60c "BETTER—COSTS LESS"



This Socket is made of porcelain—the ideal material for the purpose. Our own special design makes possible the use of this material. Has many advantages over other types of sockets, in addition to moderate price. Suitable for either panel or base mounting. If your dealer does not handle them, order direct and send us his name.

Watch for our announcement of new \$1.00 Variable Condenser. We are also manufacturers of cabinets, CROSLEY MAGFON, and other radio apparatus. Write for circular matter.

DEALERS: it will pay you to handle our line. Write for full particulars.

**Crosley Manufacturing Co.**

Dept. Q.S.T. #2,

Cincinnati, Ohio



BATTERIES FOR PLATE  
CIRCUIT OF VACUUM TUBES.

**NOVO MANUFACTURING CO.**

424 W. 33d ST.  
NEW YORK

531 So. Dearborn St.  
CHICAGO

## BUILD YOUR OWN SET

High quality, seamless paper tubing, in just the right sizes for constructing

Variometer 3⅞" x 2" 25c  
4⅞" x 2½"

Vario-Coupler 3⅞" x 2" 35c  
4⅞" x 4½"

3500 Meter Loose Coupler 45c  
3¼" x 7" 3⅞" x 7"

6000 Meter Loose Coupler 65c  
3⅞" x 7" 4⅞" x 7"

Postpaid to you—order to-day.

**THE TAYLOR COMPANY**

Box 1043C

Lowell, Mass.

## CLASSIFIED ADVERTISEMENTS

Five cents per word per insertion, in advance. Name and address must be counted. Copy must be received by the 10th of month for succeeding month's issue.

**FOR SALE:** 900 volt direct current generator, \$30; one Campbell, Model E, X-Ray outfit in oak cabinet with oak stand, tube, applicators, and all accessories, \$40.00; One K.W. panel type transmitter as described August 1920 Everyday Engineering, comprising Acme type H1 transformer, plate glass in oil condenser, oscillation transformer, enclosed rotary gap with Emerson high speed motor, Weston thermo-couple ammeter, United Wireless 2 K.W. key, special bakelite antenna switch, and mica protective condensers. Absolutely complete; suitable for school or college, \$185.00; Fleming, laboratory type, DC milli-ammeter, three range-10, 100 and 1000, \$10; B battery box with potentiometer and switch mounted with two nearly new Burgess batteries, \$5; Send for list of other items and parts. J. A. Hall, 1016 Iglehart Ave., St. Paul, Minn.

**GENERATORS** 10, 450 Volt 1-10 K.W. Westinghouse externally excited generators. New \$20.00 each. Money back guarantee. Frank Crosswell, 920 West 55th St., Los Angeles, Cal.

**AUTO MOTORS SUPPLIES:** Buick—Michigan—Stoddard-Dayton—E. M. F.—Cadillac—Overland—Continental and Buda Motors. All types, \$50.00 each and up. New Dixie Magnets \$20.00. Splittorf High Tension Magnets \$10.00. Kellogg Pumps \$3.50. Auto-Lite generators, new \$10.00. Air gauges \$0.65. Remy Ignition Coils, new \$3.00. Electric and gas headlamps, coils, distributor heads, air compressors, etc. Write for catalog. Motor Sales Dept. 19, West End, Pittsburgh, Pa.

**SELL:** Variometer short wave regenerative. \$12.00 Gordon Rideout, Everett, Mass.

**DX MEN,** Variometer tuned receiver variometers have 4" dials with 2" knob, in cabinet with bakelite panel. These are wonderful receivers. Sold unwired \$40. We are agents for Chelsea, Tuska, Coto-Coil, Porox A-Batteries, Ace B-Batteries, Radio-craft. Send for bulletins. Stratfield Radio Laboratory, R. F. D. 1, 9 Flushing Ave., Bridgeport, Conn.

**FOR SALE:** "Z-Nith" Regenerator and "Z-Nith" two-stage Amplifier. First class condition. Price each \$35.00. Arthur Haake, West Norwood, New Jersey.

**SELL:** DeForest 1 to 1 Amplifying Transformer \$2.50. 92L.

**FOR SALE:** 1/2 K.W. Telefunken transmitter including motor-generator and accessories. Lester A. Pulley, Melrose, Mass.

**NOW** is the time to buy—New and Used Apparatus at special prices. Tell me what you need. W. Free-lan 34 Baldwin Ave., Newark, N. J.

**FOR SALE:** Complete regenerative audion panel with batteries, phones, etc. Works perfectly. Worth \$60. Will sell \$35. Write for full description. Donald Meyer, 9714 Lamont, Cleveland, Ohio.

**BARGAINS!** Few unused A. P. Tubes. Relays \$5.25, Amplifiers \$6.25, postpaid. Also two each Cunningham Tubes, unused, Detectors \$4.25, Amplifiers \$5.75, postpaid. Radio Sales Co. 251 Duboce Ave., San Francisco, Cal.

**ALKALINE** Storage "B" batteries give years of service without expert attention. Thirty two volts \$8; fifty volts \$10; sixty-eight volts \$12. Pictures and further information upon request. Kimley Electric Co., 290 Winslow Ave., Buffalo, N. Y.

**FOR SALE:** Murdock 1/2 K.W. Rotary \$10.25; Amrad 1/2 K.W. Quenched Gap \$12.25. Lawrence Kidd, 289 Broadway, Lawrence, Mass.

**WANTED:** 6 volt Amrad induction coil. Have Acme 500 watt and amp. transformer, C. W. generator, 0-5 H. W. Ammeter, all new. Geo. Neff, Jr., 68 N. Gore Ave., Webster Groves, Mo.

**SPECIAL GARAGE MOTORS:** Manufactured by the General Electric Co. 1 H.P. \$78.50—2 H.P. \$110.00—3 H.P. \$128.50—5 H.P. \$166.50. All sizes both single and Polyphase Motors for immediate delivery. Special charging generators all voltages. Write for catalog. Motor Sales Dept. 19, West End, Pittsburgh, Pa.

**SELL:** Complete 1/2 K.W. transmitter \$35. Regenerative cabinet \$10. Detector and 2 step with jacks controlling both A & B batteries, complete with bulbs and B batteries \$45. Two large automobile batteries fine condition \$15 each. Gap motor \$4. Also great lot miscellaneous parts. Printed list for 2c stamp. Hanes, Stroh, Ind.

**SPECIAL GREBE OFFER.** For a limited time we are supplying free of charge with each Grebe Type CR-3, Short Wave Regenerative Receiver the recognized standard among most all professional amateurs, your choice of a Paragon Vacuum Tube Control, a pair of 2000 ohm Murdock phones, a Radiotron UV-200, VT Detector, or a Moorhead A-P VT Detector. Type CR-3, \$65.00. Only new and high-grade apparatus carried in stock. Orders filled within twelve hours. Unsatisfactory goods subject to return in five days. The Kehler Radio Laboratories, Department 3, Abilene, Kansas.

**LOOK!** Variometer-regenerative, \$19; 2-step amplifier, \$23; Western Electric phones, \$11; VT-1, \$6; VT-2's, \$8; 2mf. paper condensers, \$0.75; phone transmitters, \$0.90; tubular trons, \$5; Other stuff. Want camera. L. Peacock, 41 S. E., 7th St., Miami, Fla.

**WANTED:** C.W. apparatus. Sell 1/2 K.W. Transformer with preventers \$12.00. E. O'Neill, Downers Grove, Illinois.

**FOR SALE:** One K.W. 500 cycle self-excited generator; \$75.00. H. M. Warner, Great Notch, N. J.

**SELL:** or Swap 1/4 K. W. Thordarson \$9.00, O. T. \$3.00, C.W. apparatus. Write for list. Henry Kulikowski, 483 Main St., Ansonia, Conn.

**FOR SALE:** 1 Grebe Audion Control Cabinet with tickler connections \$12. With bulb \$15. Hewey Jackson, Bower Springs, Kansas.

**SELL:** Vol. 5-6-7 I.R.E. Proceedings. Also back numbers of all Radio magazines.. W. A. Parks, Brookland, D. C.

**SAY OM:** Can save you money on apparatus and supplies. Handle all makes good apparatus. Prompt shipment. Radio orders given preferred attention. Send 2c stamp for printed list and prices. Hanes, Stroh, Ind. 9DBQ.

**DeForest Radiophones** A. C. Type O.T. with 3 Rect. tubes and 4 Radiotrons, \$1.50. J. C. Cox, 5130 Enright Ave., St. Louis, Mo.

**FOR SALE:** 1/4 K.W. Thordarson transformer, \$13.00; Thordarson oil immersed condenser, \$13.00; both, \$25. Also heavy O.T. and 2 K.W. United Wireless change-over switch. R. French, 1675 Pilgrim Pl., Akron, O.

**DO WE? "Yes"** We supply free of charge with each Radiotron UV 202 5 watt power tube (\$8.00) a special 5000 ohm size "M" grid leak (\$1.10), with midtap at 3500 ohms, and with each 50 watt Radiotron UV 203 power tube (\$30.00), a special 5000 ohm size "B" grid leak (\$1.65) with midtap at 2500 ohms. These grid leaks are designed and manufactured by the General Electric Co., for use with the Radiotron Power Tubes. Only new and high-grade apparatus carried in stock. Unsatisfactory tubes subject to return in five days. Orders are filled within twelve hours, and are shipped postpaid and insured. "Remember us." The Kehler Radio Laboratories, Department 3, Abilene, Kansas.

**CABINET** long distance set, battery, tube \$25. Navy transformer \$9. Large transformer \$10. Switches, Phones, Condensers, Write James B. Rich, Hobart, N. Y.

**FOR SALE:** One complete 15 unit DeForest receiving panel; includes crystal and audion detectors and 1 step. One complete set of Hawkins Electrical Guides. For full information Write Cramer La Pierre, Jackson, Mo.

**FOR SALE:** 1/4 K.W. type Thordarson Wound for 220 V 60 cycle \$20, Aluminum Enclosed Benwood \$25, (14 point), 220 V Westinghouse Induction motor 1/6 H.P. nearly new \$25. All letters answered R. E. Linthicum, 2013 Benning Rd., Washington, D. C. Radio 3KM.

**TRIPLE HONEYCOMB COIL** receiving cabinet 175-20,000 meters, including twelve coils and audion \$70.00. John Smith, 3650 Marvine, Philadelphia.

10/38 Litz wire, 3 feet \$0.01; \$1.10 per lb. Bridges for measuring resistance and capacity, 38 coils 10-4000 ohms, hard rubber top, mahogany cabinet; blue printed instructions, \$6.50. Galvanometers \$11.00. New and used D.C. meters. Western Instrument Repair, 314 N. Fairfield, Chicago, Ill.

**VARIOCOUPERS WOUND** on Bakelite tubes \$5.25. Variometers inside windings \$4.25. No. 22 DCC. Magnet wire \$0.30, 1/4 pound, all sizes. Choke coils ideal for Radiophone. Oak Cabinets all sizes. Bakelite tubes and panels. Meade Bakelite and Radio Apparatus, 522 Central Ave., Brooklyn N. Y.

**FOR SALE:** closing down station. All parts and apparatus of telephone and spark sets also receiving set. Including variables, transformers, rotary converter, tubes, storage battery, etc. W. S. Willis, 347 W. 14 Street, New York City. 2QM.



**WIRELESS:** The new Crosley V-T Socket, suitable for either base or panel mounting. Price only 60c.

(Continued on next page)


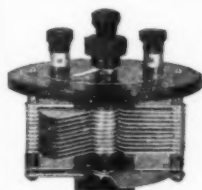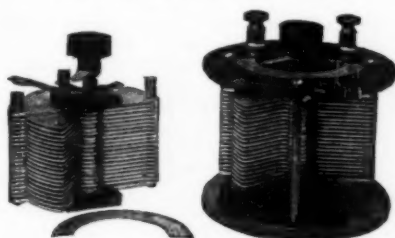
## THE "ILLINOIS" VARIABLE CONDENSER

The Condenser with "Star Spring" Tension  
MADE RIGHT - STAYS RIGHT  
Hard Rolled Aluminum Plates



Style No. 1 No. 2 No. 3

|            |        |        |        |
|------------|--------|--------|--------|
| 67 Plates, | \$7.00 | \$8.00 | \$8.50 |
| 43 Plates, | 3.50   | 4.50   | 4.75   |
| 23 Plates, | 2.75   | 3.75   | 4.00   |
| 13 Plates, | 2.25   | 3.25   | 3.50   |

Money back if not satisfied. Just return condenser within 10 days by insured Parcel Post.

### VERNIER

Three Styles; No. 1, Panel; No. 2, Open Type as shown; No. 3, Fully Encased. Anti Profitteer. Less than pre-war prices. Fully assembled and tested. With Style No. 1, we will, if desired, furnish 3 inch metal Dial with large knob, instead of Scale and Pointer. Extra Price 75 cents. Or we will send Condenser with smooth  $\frac{1}{8}$ " center staff, without Scale Knob and Pointer, at 15 cents off list, for those who prefer to furnish their own dial. Vernier with single movable plate applied to 13, —23, and 43, plate Condensers, \$3.00 extra.

Sent Prepaid on Receipt of Price.

Except: Pacific States, Alaska, Hawaii, Philippines and Canal Zone, add 10c. Canada add 25c.

G. F. JOHNSON, 625 Black Ave., Springfield, Ill.

## SIX Stages of audio frequency amplification!

See John Firth & Co.'s August advertisement.

(Classified Ads., Concluded)

Also new variable condenser, .0005 capacity, \$1.00 without dial, \$1.75 with dial. Also stock cabinets for radio apparatus and other specialties. Circulars on request. Crosley Manufacturing Company, Dept. Q.S.T., Cincinnati, Ohio.

FOR SALE: Acme Transformer, Oil Condenser, Benwood Gaps and large Oscillation transformer \$32.00. 8AAT.

25 Cycle  $\frac{1}{4}$  and 60 cycle  $\frac{1}{4}$  K.W. transformers, O.T. oil condenser, key. For sale by Alex. Darragh, Beaver, Pa.

BUILD YOUR OWN RADIOPHONE TRANSMITTER, 5-50 miles on B-Battery. Also radiophone receiver (instantaneous Oscillator) no interference from spark transmitter, easily built at small expense. Detailed instruction and Diagram for Radio-Phone Transmitter \$1.00 for Radio-Phone Receiver \$1.00. Ernest C. Mignon, R. E. 366 Hudson St., Buffalo, N. Y.

FOR SALE: 2" Spark Coil A1 condition \$8.00. A. Grosshohlin, 126 Humboldt St., East Rutherford, N. J.

ALWAYS MENTION Q S T WHEN WRITING TO ADVERTISERS

## LEARN WIRELESS AT HOME


The Demand for Good Wireless Operators Far Exceeds the Supply

The New York Wireless Institute will make you an operator—AT HOME—in your spare time—quickly, easily and thoroughly. No previous training or experience required. Our Home Study Course has been prepared by our Radio Expert, I. R. Krumm, formerly Chief Radio Inspector, Bureau Navigation, N. Y. Experts able to impart their practical and technical knowledge to YOU in an easy to understand way. The graded lessons mailed you will prove so fascinating that you will be eager for the next one. The instruments furnished free, will make it as easy to learn the Code as it was to learn to talk. All you will have to do, is to listen.

**Travel the World Over** A Wireless Operator can visit all parts of the world and receive fine pay and maintenance at the same time. Do you prefer a steady position without travel? There are many opportunities at the numerous land stations or with the Commercial Wireless or Steamship Companies.
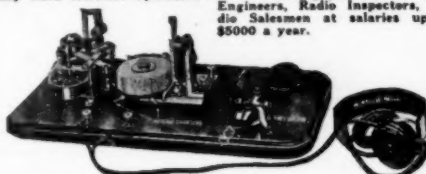
### BIG SALARIES

Wireless operators receive salaries from \$125 to \$200 a month and it is only a stepping stone to better positions. There is practically no limit to your earning power. Men who but yesterday were Wireless Operators are now holding positions as Radio Engineers, Radio Inspectors, Radio Sailmen at salaries up to \$5000 a year.



This wonderful Set for learning the code furnished free with our

### FREE

Instruments and Text Books

We furnish free to all students, during the course, the wonderful receiving and sending set exactly as reproduced in the illustration. This set is not loaned but GIVEN to all students completing the course.

The Transmitter shown is the celebrated Omnigraph used by several Departments of the U. S. Government and by the leading Universities, Colleges, Technical and Telegraph Schools throughout the U. S. and Canada. Still, the Omnigraph, place the phone to your ear and this remarkable invention will send you Wireless Messages the same as though you were receiving them, through the air, from a Wireless Station hundreds of miles away. When you apply for your license, the U. S. Government will test you with the Omnigraph—the same model Omnigraph as we furnish to our students. Ask any U. S. Radio Inspector to verify this.

### FREE Post-Graduate Course

A one month's Post-Graduate Course, if you so desire at one of the largest Wireless Schools in N. Y. City, New York—the Wonder City—the largest port in the World and the Headquarters of every leading Wireless and Steamship Co.

### NEW YORK WIRELESS INSTITUTE

Dept. 262 258 Broadway New York City

### NEW YORK WIRELESS INSTITUTE

Dept. 262 258 Broadway New York City

Send me, free of charge, your booklet "How to Become an Expert Wireless Operator," containing full particulars of your course, including your Free Instrument Offer.

Name .....

Address .....

City or Town ..... State .....

# ? No. 7600 ?

### QST de 8AFO all NRH and Vicinity

We sell RADIO CORP. BULBS, etc., also De Forest RADIO, Acme Apparatus, Burgess B Batteries, Brandes Phones. Order from catalogs. We pay postage. Information and Bulletins gladly sent.

### KRAUS BATTERY CO.

3425 W. 25.

CLEVELAND, O.



# A COLOSSAL EVENT

The new RASCO catalog just off the press is one of the greatest events in amateur radio. There are many radio catalogs, but the RASCO catalog is an event by itself for the simple reason that it

## Contains 50 Vacuum Tube Hook-Ups

This is the one and only radio catalog containing such wonderful free information. Complete hook-ups of all important vacuum tube circuits are given in clear diagrams with complete explanation. Just to name a few — The V.T. as a detector, detector and one-step amplifier; regenerative circuit; De Forest ultra-translation; V.T. to receive undamped and spark signals; Armstrong circuits; one step radio frequency amplifier and detector; three stage audio-frequency amplifier; short wave regenerative circuits; V.T. radio telephone; 4-stage radio frequency amplifier; radio and audio frequency amplifier; inductively coupled amplifier; Armstrong superheterodyne; radio frequency amplifier and crystal detector; C.W. transmitters; self-exciting 2 tube C.W. transmitter; V.T. transmitter with 6 volt battery; radiophone using plate and grid modulation; one tube radio transmitter and receiver; experimental radiophone; radiophone using Colpit oscillator circuit.

This list is only a partial one. You must positively see this wonderful book to appreciate it. It is made to fit the pocket—has heavy covers to withstand the wear and tear which it is sure to have at your hands because it will be your constant companion.

And Oh yes! Before we forget it. If you are in need of the following, remember "Rasco has it." These are only a few things contained in this catalog: Lugs, Nuts, Bolts, Washers, Crystals, Litz Wire, Selenium, Cord Taps, Cap Nuts, Tin Foils, Name Plates, Spring Pans, Switch Parts, Metal Ribbon, Carbon Balls, Binding Posts, Switch Points, Switch Levers, Farnes Grains, Metal Punctures, Contact Points, Low Melting Metal, Carbon Diaphragms, Screws, Copper Strip, "Spacchetti," Name Plates, Sliders, Mick, Switches, Resistance Wire, Varocoupler Rotors, Test Clips, Condenser Plates, Condensers, Antenna Connectors, Threaded Brass Rod, Ground Clamps, Etc. Etc.

The catalog contains 185 illustrations. On account of its great cost, this catalog cannot be distributed free of charge. It will only be mailed upon receipt of

15c in stamps.



185 illustrations


### The Rasco "Baby"

Here it is boys! The smallest and most efficient detector in the world—as well as the cheapest. Our illustration is full size, and while the various details can be seen at a glance, we feel so enthusiastically about it that we must tell you all of its good points. First, there is a solid hard rubber composition base, 4 1/2" x 1 1/2". We have not forgotten two holes to screw down the detector.

Then we have the nickel holder and binding post combined which holds the sliding, knurled, hard rubber composition knob. As you see, this knob not only revolves in its holder, but can also be moved back and forward in order to explore each point of the detector crystal.

Next we see the patent nickel detector cup and binding post combined. This is a little marvel all by itself and will not fail to awake your admiration. No clamps, no soft metal to fuse with. You

## THE RASCO "BABY"

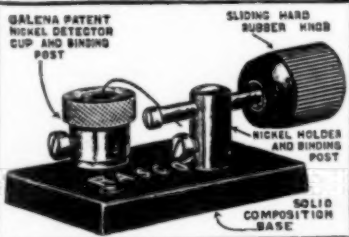

simply unscrew the knurled cap and insert your crystal into the stand, screw home the cap which leaves a goodly portion of the galena exposed. The contact is perfect, while the crystal can be exchanged quickly in less than three seconds. By slightly unscrewing the cap, the crystal can be changed in position, in order to explore other sensitive spots. The catwhisker is of phosphor bronze and is attached to the horizontal bar by means of a blitzer head screw. Can be readily exchanged in less than two seconds. Wires can be connected to the binding post in a jiffy. All metal parts are nickel plated, and you will be proud of this little masterpiece.

No. 1928 Rasco Baby Detector complete with galena crystal, prepaid.....

50c

No. 1929 The same but furnished with an additional piece of tested radiocite crystal, prepaid.....

75c

Ready for distribution June 30th.



800



804




802



801



803

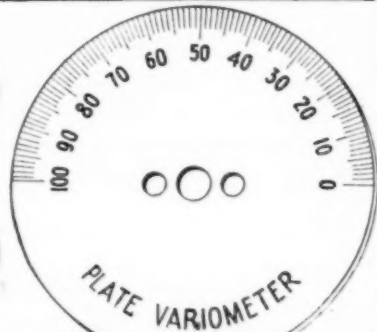

## RASCO DIALS

Again Rasco is setting the pace. Here are our new Rasco Dials. A revelation in every respect. These dials measure 2 1/2" diameter and are made in heavy brass. They have two extra holes to fit our No. 128A Bl Knobs (see last month's advertisement.) The finish is silver white. Lettering in black enamel, inside. There is nothing on the market like it for finish. Consider the very low price of these dials. Note particularly that we make six different types with following denominations: "Plate Variometer," "Primary Condenser," "Secondary Condenser," "Filament Rheostat," "Coupling," "Grid Variometer."

No longer do you have to guess what each dial on your set stands for, as each one is now plainly marked. Order by number. Large Dial 3/4 size. The smaller illustrations are only given to show style.

DEALERS' GET OUR SPECIAL PROPOSITION

Prices all styles . . . . . prepaid ea. 30c

A series of 6 dials complete prepaid, \$1.70

Do not compare these dials with some other makes as there is positively no comparison between them. Must be seen to be appreciated. Money back if not satisfied.

800 Designs Copyright 1921 by R. S. Co.

Did you see our full page ad in the May issue? We expected a good deal of business but we were actually snowed under! It shows that Rasco goods are wanted. In one week we filled over 100 orders and each and every order was shipped within 24 hours! Surely a record. We own filled orders for articles not listed. Our prices are low—our service the quickest—and your small order is never side-tracked as all our orders are small. One trial order will make you a life customer. Try us with a 50c order. We can only "stick" you once!



98-100 PARK PLACE, NEW YORK CITY

Factories: Brooklyn, N. Y.—Elkridge, Md.

WE GUARANTEE EVERY ORDER SHIPPED WITHIN 24 HOURS.

—FOR YOUR CONVENIENCE—

# QST'S INDEX OF ADVERTISERS

## IN THIS ISSUE


|  |              |  |       |
|--|--------------|--|-------|
| A.R.R.L. National Convention.....            | 101          | Magnavox Co., The.....                   | 92    |
| Ace Battery Mfg. Corp.....                   | 106          | Manhattan Elec'l Supply Co., Inc.....    | 105   |
| Acme Apparatus Co.....                       | 120          | Marshall-Gerken Co., The.....            | 80    |
| Ajax Electric Co.....                        | 86           | Massachusetts Radio & Tel. School.....   | 106   |
| All-American Elec'l Mfrs.....                | 66           | McTighe Battery Co.....                  | 72    |
| American Electric & Wireless Supply Co.....  | 78           | Midwest Radio Co.....                    | 94    |
| American Electro Technical Appliance Co..... | 113          | Morris Co., The J. O.....                | 114   |
| American Radio & Research Corpn.....         | Fourth Cover | Murdock Co., Wm. J.....                  | 69    |
| American Radio Sales & Service Co.....       | 68           | Mutual Purchasers Assn.....              | 82    |
| Andrea, F. A. D.....                         | 70           |  |       |
| Atlantic Radio Co.....                       | Second Cover |  |       |
| Atlantic Radio Supplies Co.....              | 85           |  |       |
|  |              | New York Wireless Institute.....         | 117   |
| Beekay Motor Service.....                    | 90           | Newman-Stern Co.....                     | 89    |
| Benwood Co., The.....                        | 99           | Novo Mfg. Co.....                        | 115   |
| Bliss Co., R. W.....                         | 109          |  |       |
| Brandes, C., Inc.....                        | 105          | Pacent Electric Co., Inc.....            | 4     |
| Bronx Radio Equipment Co.....                | 115          | Pacific Radio Pub. Co.....               | 84    |
| Bunnell & Co., J. H.....                     | 82           | Pacific Radio Supplies Co.....           | 85    |
| Burgess Battery Co.....                      | 103          | Paquin, J. M.....                        | 115   |
| Burgess Electric Co.....                     | 112          | Parkin Mfg. Co.....                      | 98    |
|  |              | Philadelphia School of Wireless Tel..... | 75    |
| California Elec. Supply Co.....              | 98           | Pitts Co., F. D.....                     | 93    |
| Central Electric & Lock Co.....              | 112          | Pioneer Elec. Co.....                    | 114   |
| Chelsea Radio Co.....                        | 80           | Precision Equipment Co., The.....        | 102   |
| Chicago Radio Apparatus Co.....              | 77           |  |       |
| Chicago Radio Laboratory.....                | 77           | Quaker Light Supply Co.....              | 94    |
| Cino Radio Mfg. Co.....                      | 96           |  |       |
| Clapp-Eastham Co.....                        | 64           | Radio Audion Co.....                     | 97    |
| Clark, C. B. & Son.....                      | 88           | Radio Corporation of America.....        | 86-91 |
| Colebrook-Hamilton Battery Co.....           | 115          | Radio Distributing Co.....               | 1     |
| Connecticut Tel. & Elec. Co.....             | 110          | Radio Electric Co.....                   | 100   |
| Continental Radio & Elec. Corpn.....         | Third Cover  | Radio Equipment Co., Boston.....         | 81    |
| Corwin & Co., A. H.....                      | 65           | Radio Specialty Co., N. Y. C.....        | 118   |
| Coto-Coil Co.....                            | 109          | Radio Testing Station.....               | 108   |
| Crosley Mfg. Co.....                         | 115          | Ray-Di-Co.....                           | 68    |
|  |              | Rose Radio Supply.....                   | 104   |
| DeForest Radio Tel. & Tel. Co.....           | 107          |  |       |
| Doubleday-Hill Electric Co.....              | 82           | Saginaw Radio Elec. Co.....              | 104   |
| Dreyfuss Sales Corp.....                     | 98           | Ship Owners Radio Service, Inc.....      | 76    |
|  |              | Shotton Radio Mfg. Co., The.....         | 63    |
| Eastern Radio Institute.....                 | 95           | Simplex Radio Co.....                    | 99    |
| Eastern V.T. Laboratories.....               | 96           | Somerville Radio Laboratory.....         | 112   |
| Eby Mfg. Co., The H. H.....                  | 108          | Spafford's.....                          | 100   |
| Electric Machine Co.....                     | 76           | Stockwell, P. J.....                     | 96    |
| Electric Shop, The.....                      | 104          | Stuart Products Corp.....                | 90    |
| Electric Specialty Co.....                   | 64           |  |       |
| Electrical Specialty Co.....                 | 70           | T & H Radio Co.....                      | 108   |
| Empyrean Radio Co.....                       | 86           | Taylor Co., The.....                     | 115   |
|  |              | Thordarson Elec. Mfg. Co.....            | 73    |
| F. & F. Radio Shop.....                      | 102          | Tresco.....                              | 78    |
| Federal Tel. & Tel. Co.....                  | 113          | Tuska Co., The C. D.....                 | 72    |
| Firth & Co., John.....                       | 67-72-86-117 | Twin City Radio Lab.....                 | 107   |
| Formica Insulation Co.....                   | 66           |  |       |
| France Mfg. Co., The.....                    | 106          | Vimy Supply Co., The.....                | 82    |
|  |              |  |       |
| General Radio Co.....                        | 84           | Westinghouse Elec. & Mfg. Co.....        | 71    |
| Glenhurst Research Laboratories.....         | 84           | Western Radio Electric Co.....           | 80    |
| Grebe & Co., A. H.....                       | 87           | Weston Elec'l Instrument Co.....         | 82    |
|  |              | Whitall Electric Co.....                 | 88    |
| J-Ray Mfg. Co.....                           | 111          | Winkler, Frederick Jr.....               | 114   |
| Johnson, G. F.....                           | 117          | Wilcox Laboratories, Inc., The.....      | 104   |
| Johnston, Charles H.....                     | 112          | Wireless Equipment Co.....               | 2-3   |
| Johnson, Paul F.....                         | 110          | Wireless Improvement Co.....             | 90    |
|  |              | Wireless Press, Inc.....                 | 94    |
| Karlowa Radio Corpn., The.....               | 79           | Wireless Mfg. Co., The.....              | 74    |
| Kelly & Phillips.....                        | 92           | Wireless Shop, The.....                  | 103   |
| Kennedy Co., The Colin B.....                | 83           | Wireless Supply Co.....                  | 110   |
| Keystone Wire Co.....                        | 102          | Wright Radio Co., The.....               | 100   |
| Kraus Battery Co.....                        | 117          |  |       |

ALWAYS MENTION QST WHEN WRITING TO ADVERTISERS


# ACME APPARATUS



**C.W. Power Transformer**

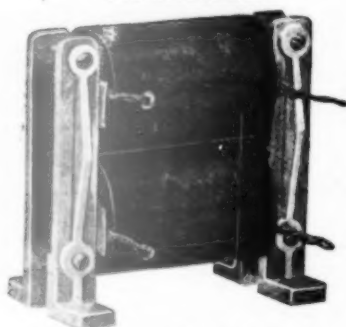

**1 1/2 Henry Choke Coil**

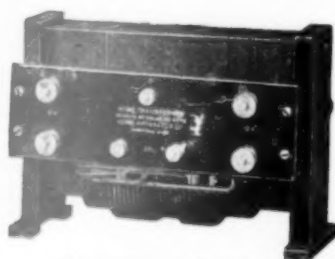

**Filament Heating Transformer**

**The Apparatus with a Guarantee.**

## **C. W. Power Transformers**

For use with rectifying devices or for A.C. directly on the plates of power tubes.

### **Specifications 110 Volts 60 Cycles**

| Output                | Filament voltage | Filament current | Plate voltage | Plate current |
|-----------------------|------------------|------------------|---------------|---------------|
| 50                    | 10               | 2.5              | 350           | 100           |
| Two filament windings |                  |                  |               |               |
| 200                   | 12               | 5                | 250-550       | 200           |
| Two filament windings |                  |                  |               |               |
| 500                   | 0                | 0                | 1000-1500     | 400           |
| No filament windings  |                  |                  |               |               |
| 600                   | 12               | 13               | 1000-1500     | 400           |
| One filament winding  |                  |                  |               |               |

## **1 1-2 Henry Choke Coils**

For use in ironing out pulsations and for modulating single and double 150 MA capacity.

## **Filament Heating Transformers**

allow the use of A.C. for power tube filament heating

### **Specifications 110 Volts 60 Cycles**

| Output | Secondary voltage | Secondary current |
|--------|-------------------|-------------------|
| 75     | 8-10              | 7                 |
| 150    | 10-12             | 13                |
| 300    | 10-12             | 26                |

## **Modulation Transformers**

give maximum modulation without distortion.

*Your Dealer will be Glad to Show These.  
Ask for Bulletins.*

**THE ACME APPARATUS COMPANY**

**194 MASSACHUSETTS AVENUE, CAMBRIDGE 39, MASS.**

*Transformer and Radio Engineers and Manufacturers*



# CONTINENTAL NEWS

JULY, 1921

Published occasionally in QST by Continental Radio and Electric Corporation

As long as a Packard is worth more than a Ford, so long will a PARAGON R. A. TEN Receiver be worth more than other receiving sets. PARAGON is built to last a life time, and absolutely guaranteed for two full years. Spread over its years of service, the cost of a PARAGON will be lower than any similar piece of apparatus. And all during that time, you get PARAGON's marvellous selectivity and amplification, never duplicated. As one amateur said, "nothing like it ever heard before, especially for strength of signals on detector alone."

The best is always cheapest, regardless of initial cost. Order a PARAGON now, or send for free descriptive booklet.

For use with the PHONETRON these long-lived 6 volt storage batteries are specially recommended:

|       |              |         |
|-------|--------------|---------|
| 10003 | 20-40 amps.  | \$14.60 |
| 10004 | 40-60 amps.  | 18.00   |
| 10005 | 60-80 amps.  | 23.60   |
| 10006 | 80-100 amps. | 29.30   |

We have a generous supply of all sizes on hand, ready to ship the day you order. Please include postage, and make remittance by bank draft or P.O. Money Order to avoid delay.

Are you interested in C.W.? If not, get interested. It's the coming method of radio transmission. Continental makes a specialty of continuous wave apparatus. Send 25c for 112 page Creco catalogue. It's well worth the money, and anyway, your quarter is credited to your first \$5.00 order.



## The PHONETRON

*Electric Sound Converter*

More than a  
loud speaker:

Designed for both reception and wireless telephone transmission in place of a microphone transmitter.

PRICE - - \$45.00

PHONETRON is distinguished from an ordinary loud speaker by the wide, rigid, cone diaphragm, in place of a horn shaped megaphone. It re-creates voice and music by wireless telephone, with a full, rich, natural tone. You will be surprised and delighted with the complete absence of any "horn tone" or reverberation. The sound waves emitted from the PHONETRON are fully rounded and retain all the original sound values.

PHONETRON is more than a loud speaker,—it is a converter of electric energy into sound, or of sound into electric energy.

The illustration shows magnet block suspended in the center of the diaphragm by three rigid supports. Thumb nut at the apex of the conical diaphragm provides an easy way for critical adjustment. PHONETRON is rigidly constructed and mounted on heavy metal base. Size 17" high by 9" wide. One 6 volt storage battery will supply sufficient current. For best results use at least one stage of amplification. With two or three stages, signals can be read distinctly several hundred feet distant.

Send for illustrated leaflet, showing construction.

## CONTINENTAL RADIO AND ELECTRIC CORP.

J. DiBlasi, Sec.

J. Stantley, Treas.

Dept. B26, 6 Warren Street, New York City

# AMRAD

*The Recognized Symbol of Superior Performance*



NEW HOME OF AMRAD—MEDFORD HILLSIDE, MASS.

THE distinguishing characteristic of AMRAD Radio Equipment—high quality workmanship—is made possible by this new, modern factory with its new machinery and the precision methods of production.

Users of AMRAD equipment secure all the advantages and benefits of our experience and skill in designing and manufacturing government-specification radio sets, fractional horsepower motors, automatic switches, ignition coils and other electrical specialties. Our achievements in these fields have won for AMRAD an enviable reputation for quality and high standards of performance.

Radio men are always welcome at the AMRAD plant. There they may see at first hand the painstaking care ever exercised in maintaining AMRAD high standards in the finished product.

If you are unable to pay us a visit, we suggest that you send for the complete catalogue, enclosing the postage, 10 cents.

**AMERICAN RADIO AND RESEARCH CORPORATION**

205 COLLEGE AVENUE,

MEDFORD HILLSIDE, 57, MASS.

(4 miles north of Boston)

